



Helwan University - Faculty of Engineering (Helwan)
Electronics and Communications Engineering Department



Lec-3 Diodes: Applications

Presented By:

Azza Mohamed Anis

Diode Applications

Diodes are used in many types of circuits such as:

- ❑ Digital Circuits (**Logic Gates**).




- ❑ Clipping Circuits.

- ❑ Clamping Circuits.

- ❑ Rectifier Circuits.

❑ Digital Circuits

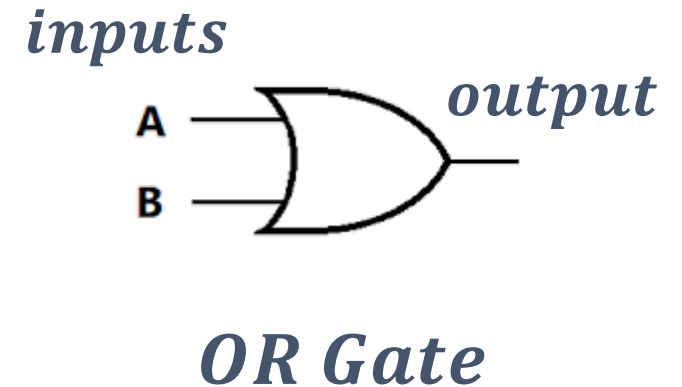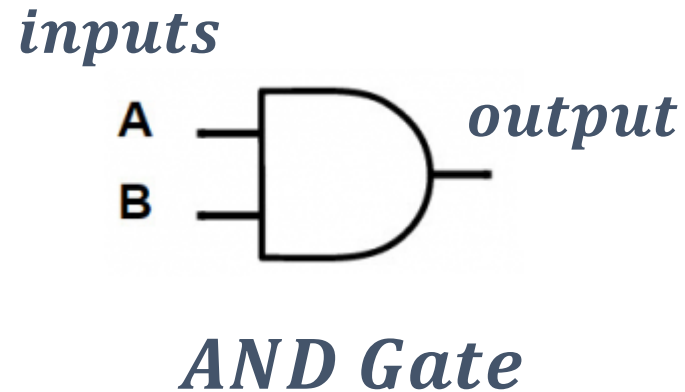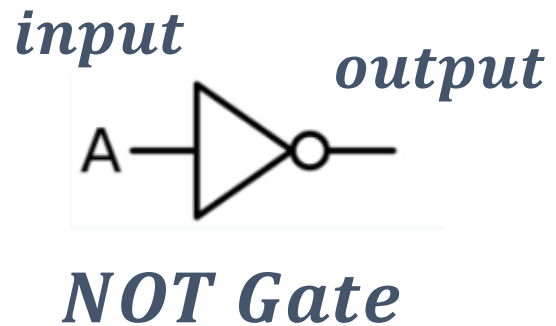All digital circuits (such as microprocessor, memory, ...) contain hardware elements called **logic gates** that perform the logical operations on binary numbers (0 and 1).




In digital circuits, binary 0 and 1 are represented by two voltage levels.


For example, zero volts (0V) represents binary 0, and +5V represents binary 1.

In actuality, because of circuit variations, binary 0 and 1 are represented by voltage ranges.

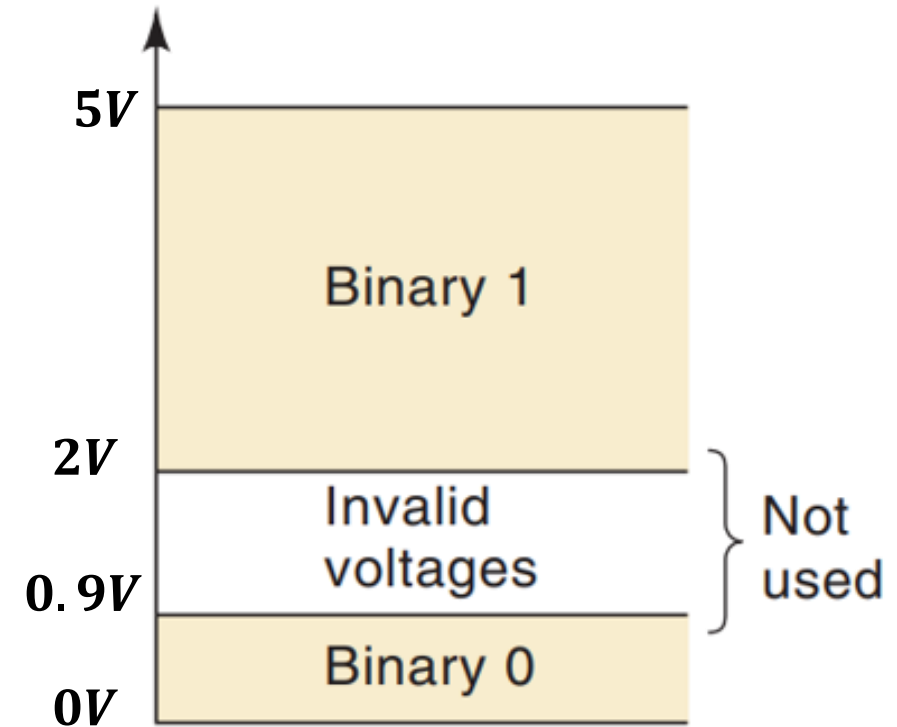
For example, any voltage between 0 and 0.9V represents binary 0 and any voltage between 2 and 5V represents binary 1.



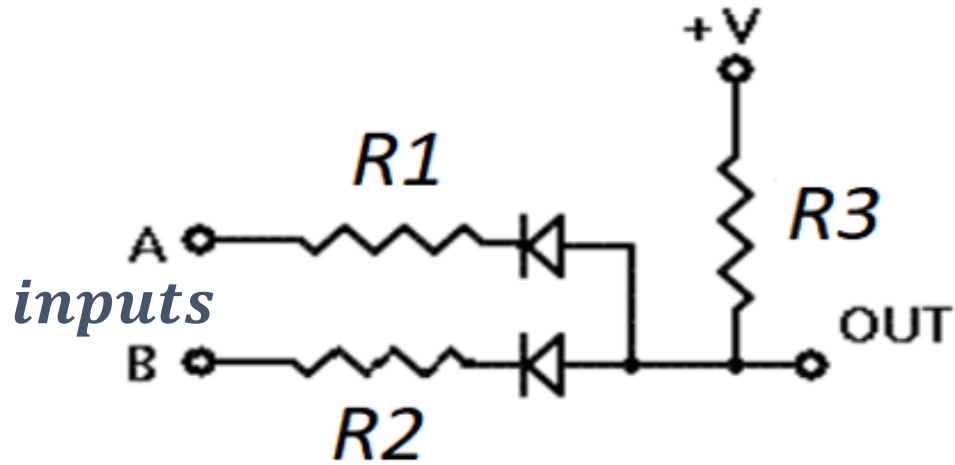Logic gates (AND, OR) can be made by combining diodes and resistors.



Two – Inputs AND Gate

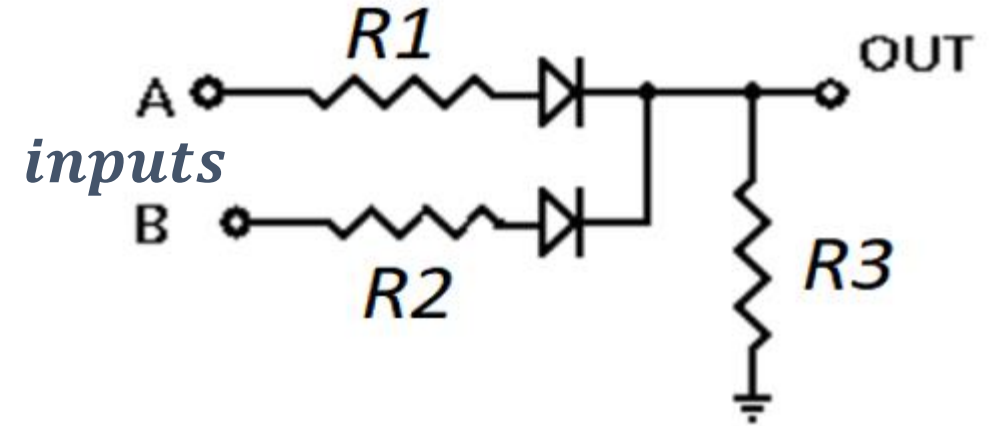

Two – Inputs OR Gate


AND gate performs AND function, its output is 1 if both inputs are 1 and its output is 0 otherwise.



A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

Truth Table of AND Gate

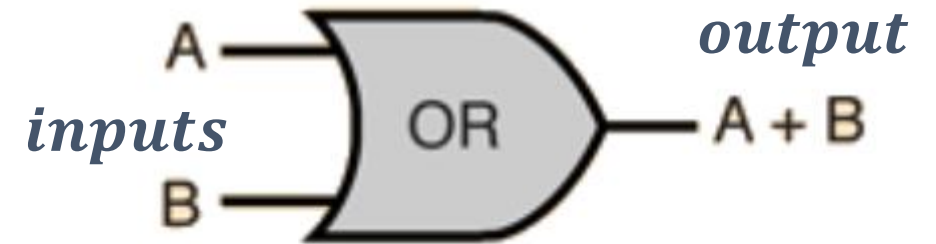OR gate performs OR function, its output is 1 if either or both inputs is 1 and its output is 0 otherwise.



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

Truth Table of OR Gate

Example-1


For the circuit shown, the cut in voltage of a diode is $0.6V$ and the voltage drop across a conducting (forward) diode is $0.7V$.

Calculate V_o for the following input voltages:

(a) $V_1 = 5V$ and $V_2 = 5V$

(b) $V_1 = 5V$ and $V_2 = 0V$

(c) $V_1 = 0V$ and $V_2 = 0V$

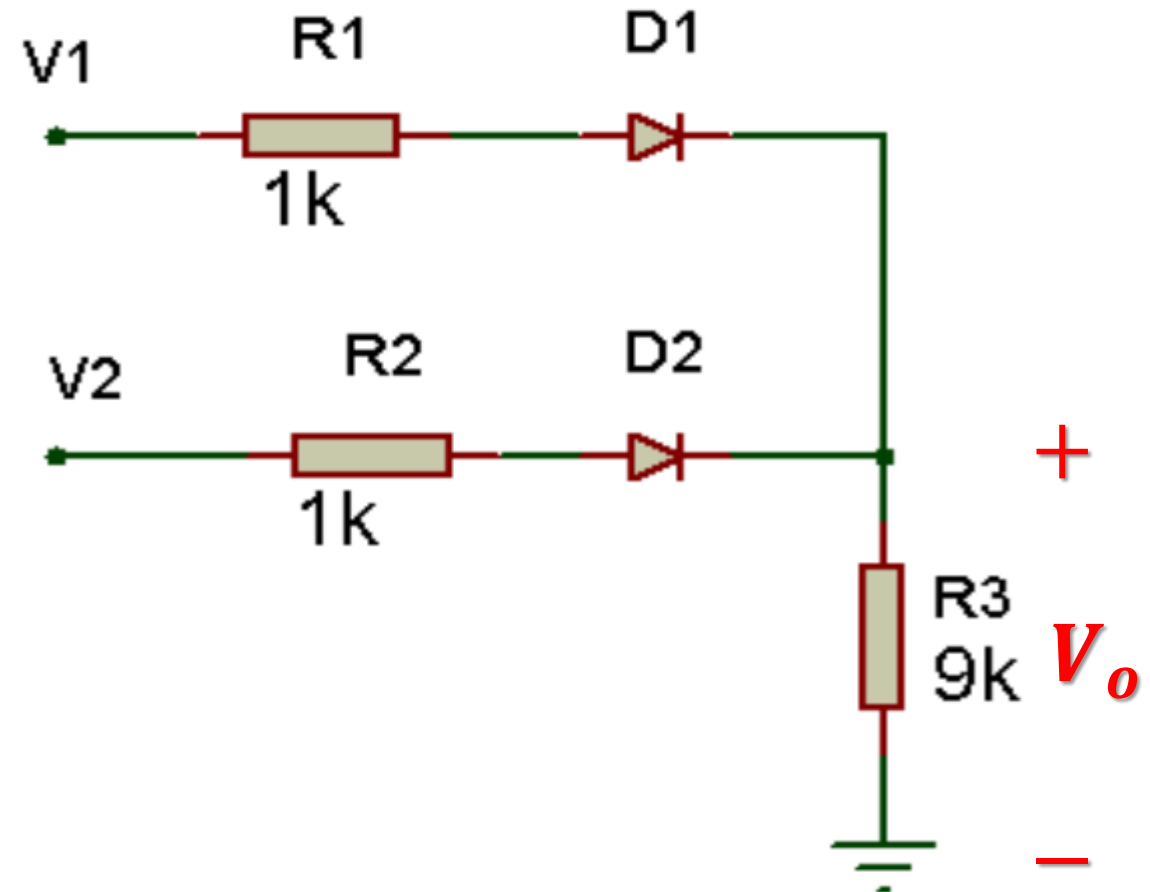

Solution:


Cut in voltage = barrier voltage = $V_B = 0.6V$

Voltage drop across
conducting (forward) diode
is $0.7V$.

means



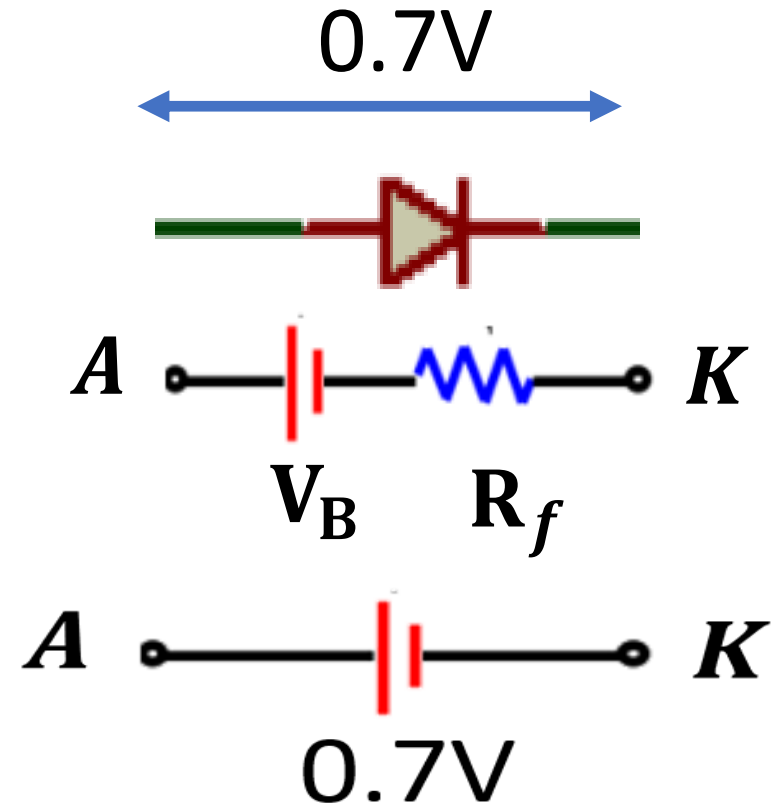Voltage across forward resistance
plus barrier voltage is $0.7V$.




(a) $V_1=5V$ and $V_2=5V$

Assume:

$$(V_{A1} = 4) > (V_{K1} = 0) + (V_B = 0.6)$$

$$(V_{A2} = 4) > (V_{K2} = 0) + (V_B = 0.6)$$

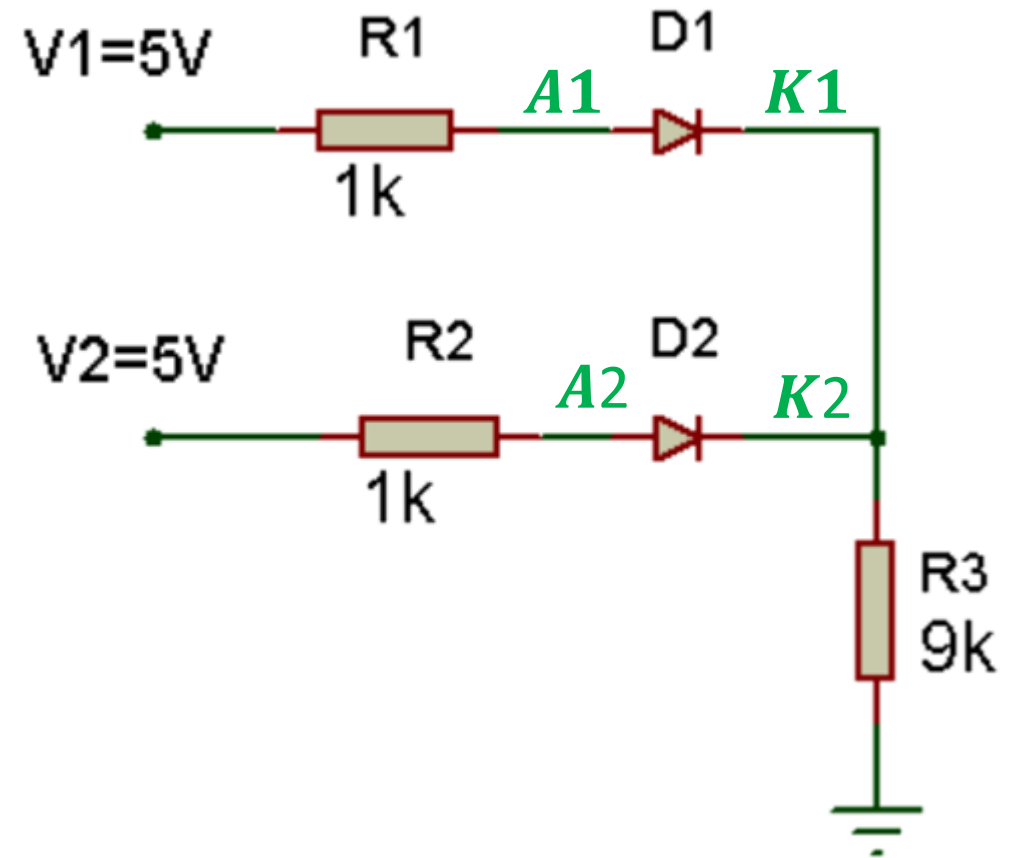\therefore Assume D_1 and D_2 are forward



$$\sum V \text{ in any closed loop} = 0$$

$$5 - (1k)I_1 - 0.7 - (9k)(I_1 + I_2) = 0$$

$$5 - (1k)I_2 - 0.7 - (9k)(I_1 + I_2) = 0$$

$$I_1 = 0.23mA$$


$$I_2 = 0.23mA$$

$\therefore I_1 = I_{D1} = \text{positive value}$

$\therefore I_2 = I_{D2} = \text{positive value}$

$\therefore I_{D1}$ and I_{D2} are in the correct direction

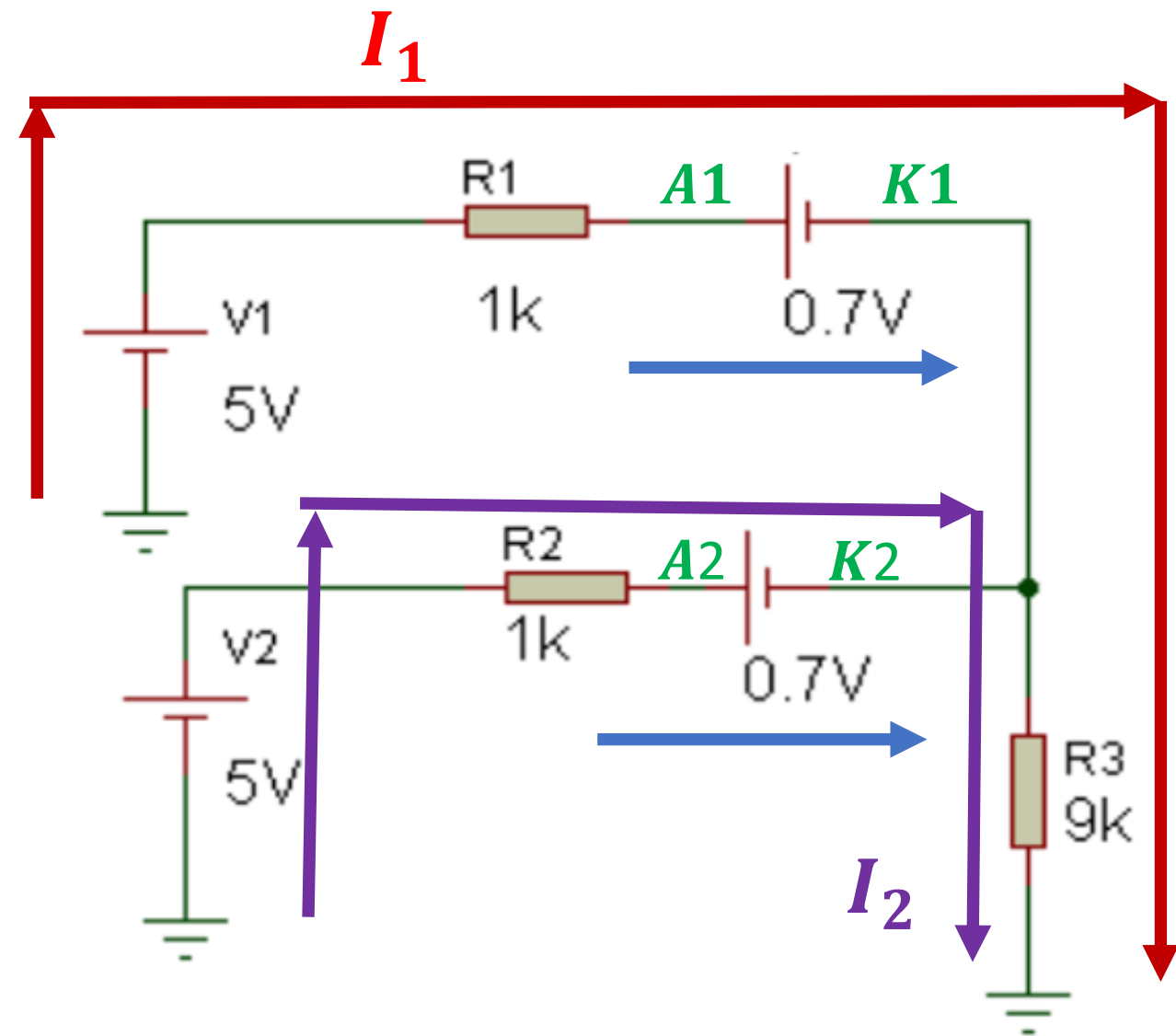\therefore our assumption is true (D_1 and D_2 are forward)




To find $\mathbf{V_o}$, write KVL between $\mathbf{V_o}$ and **the branch** (that you calculate on it the voltage drop):

$$V_o - (9k)(I_1 + I_2) = 0$$

$$V_o = (9k)(I_1 + I_2)$$

$$V_o = 4.07V$$

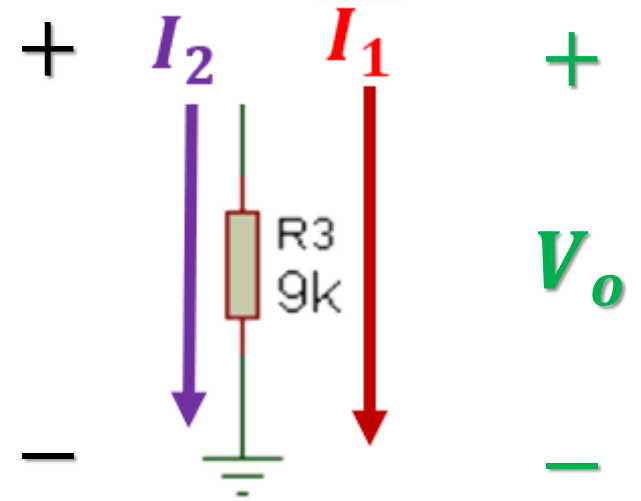


(b) $V_1=5V$ and $V_2=0V$

Assume:

$$(V_{A1} = 4) > (V_{K1} = 0) + (V_B = 0.6)$$

$$(V_{A2} = 0) < (V_{K2} = 0) + (V_B = 0.6)$$

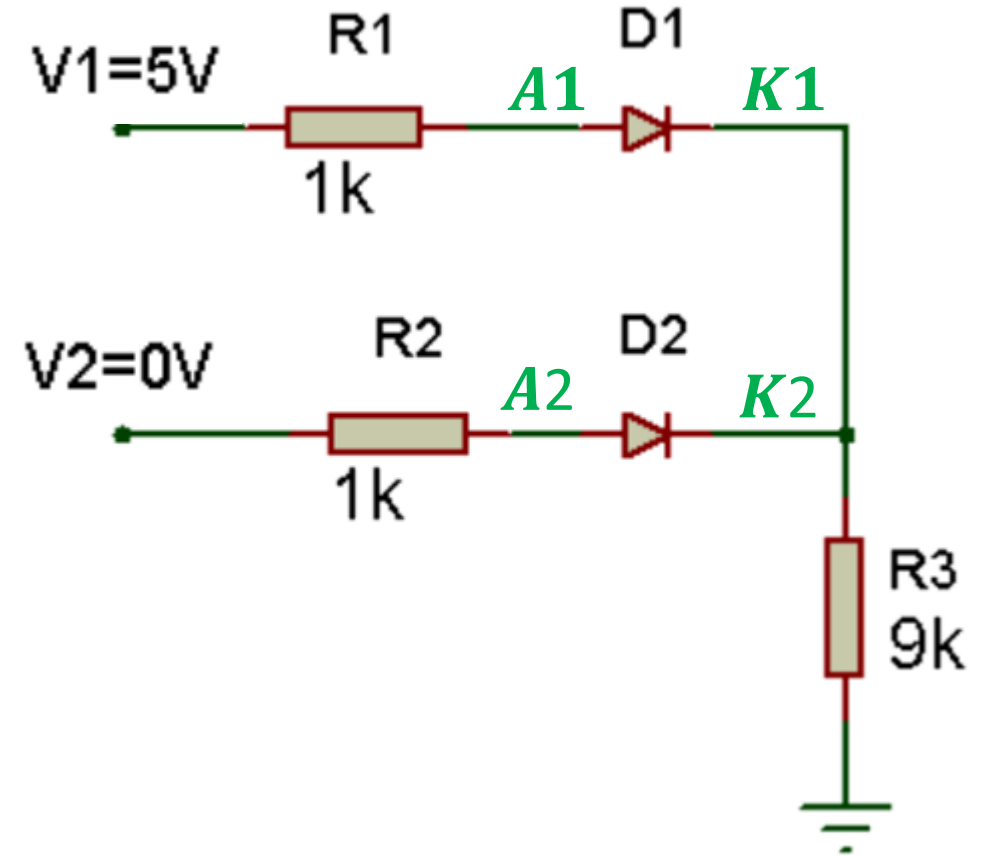\therefore Assume D_1 is forward and D_2 is reverse



$$\sum V \text{ in closed loop} = 0$$


$$5 - (1k)I_1 - 0.7 - (9k)I_1 = 0$$

$$I_1 = 0.43mA$$

$\therefore I_1 = I_{D1} = \text{positive value}$

$\therefore I_{D1}$ in correct direction

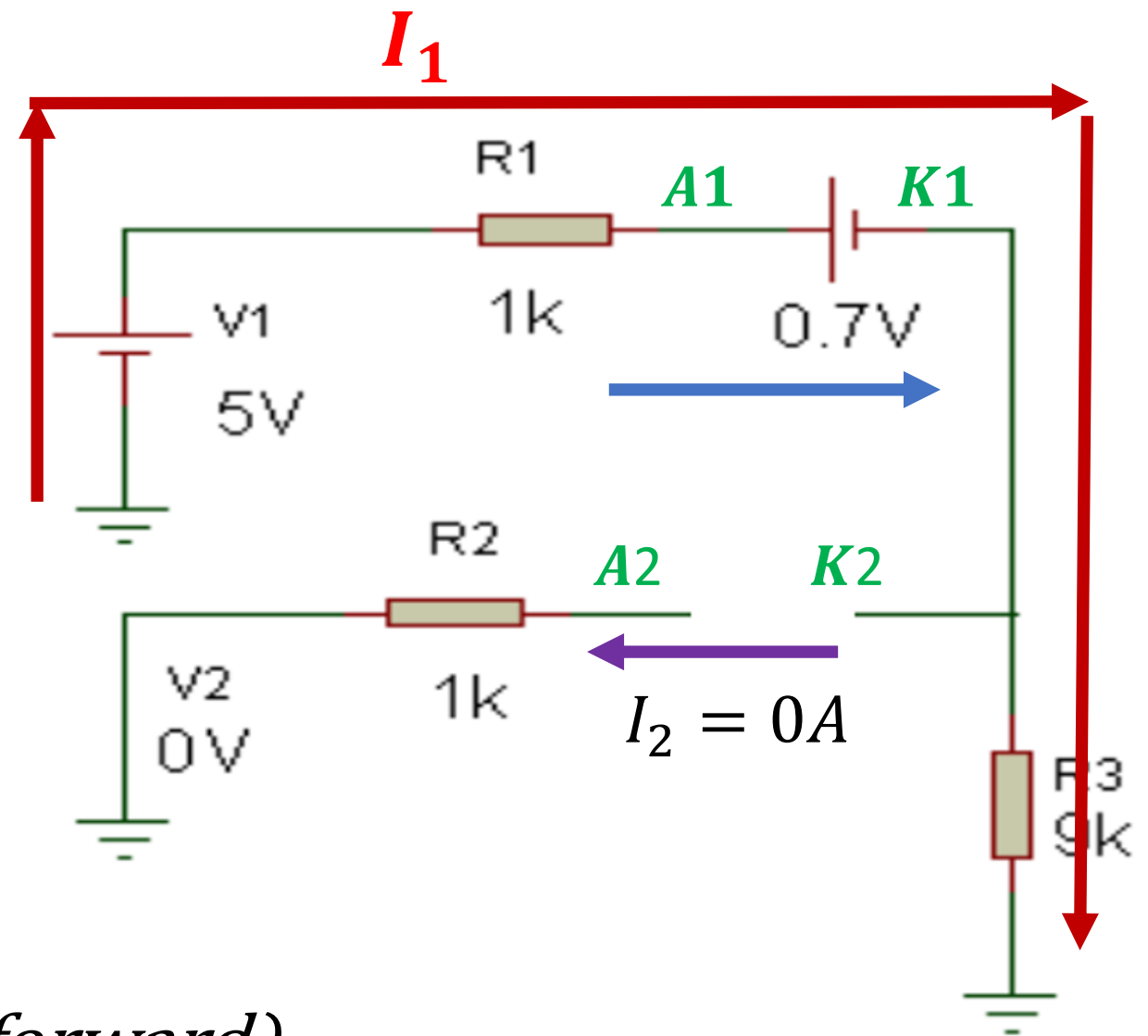\therefore our assumption is true (D_1 is forward)




To find $\mathbf{V_o}$, write KVL between $\mathbf{V_o}$ and **the branch** (that you calculate on it the voltage drop):

$$V_o - (9k)I_1 = 0$$

$$V_o = (9k)I_1$$

$$V_o = 3.87V$$

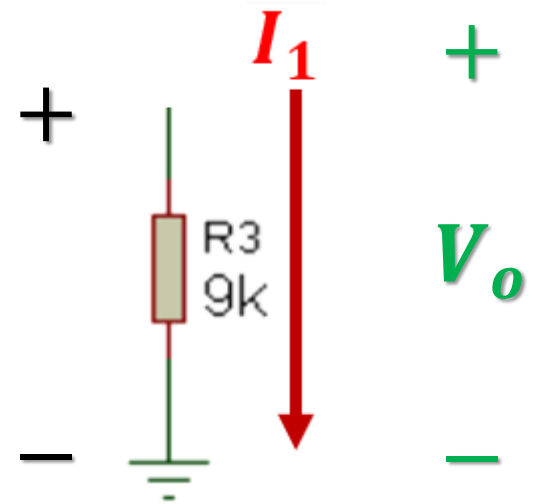


(c) $V_1 = 0V$ and $V_2 = 0V$

Assume:


$$(V_{A1} = 0) < (V_{K1} = 0) + (V_B = 0.6)$$

$$(V_{A2} = 0) < (V_{K2} = 0) + (V_B = 0.6)$$

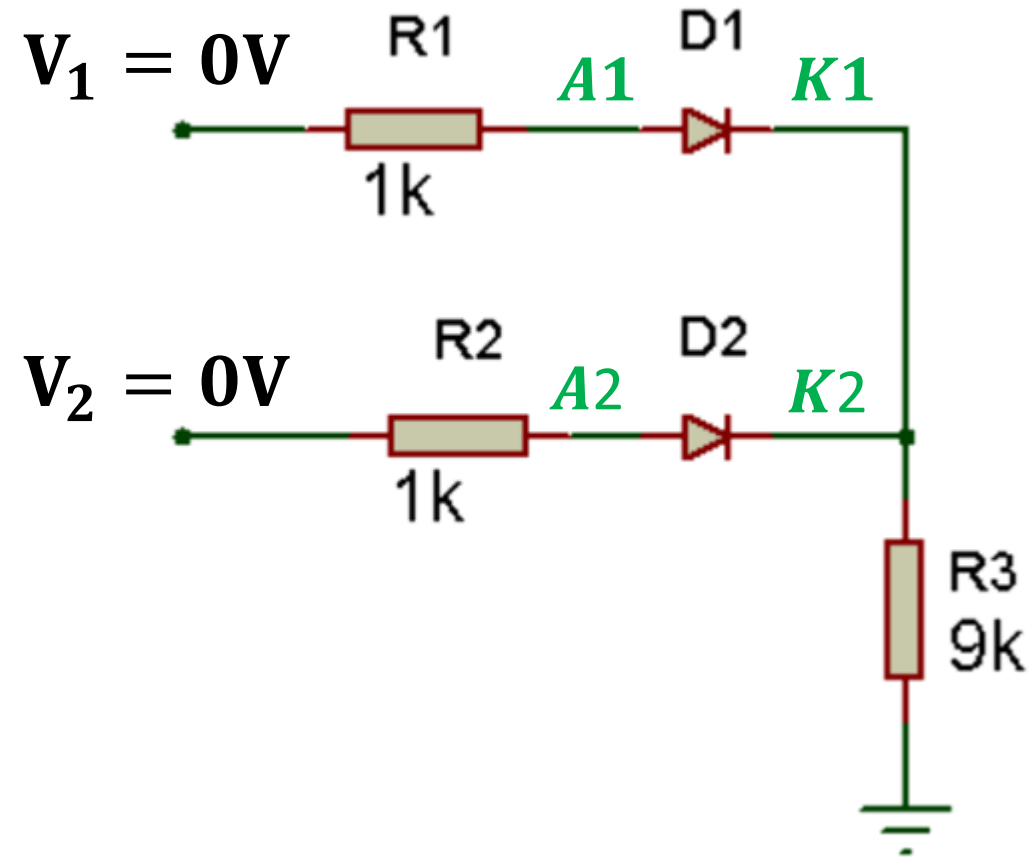\therefore Assume D_1 and D_2 are reverse




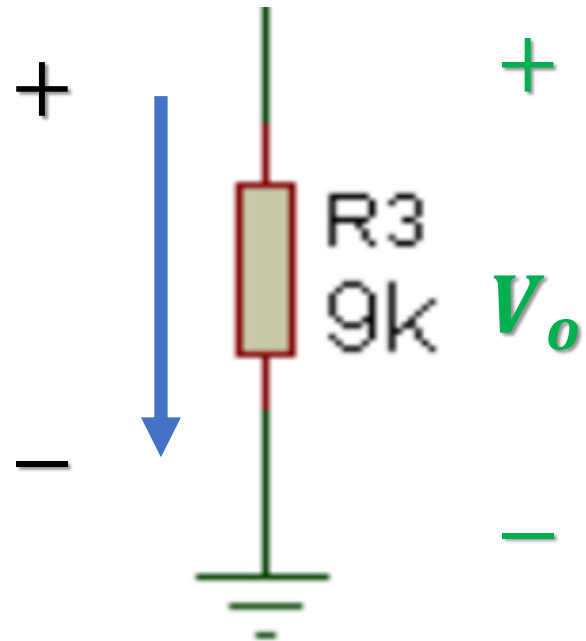To find V_o , write KVL between V_o and **the branch** (that you calculate on it the voltage drop):




$$V_o - (9k)(0A) = 0$$

$$V_o = (9k)(0A) = 0V$$

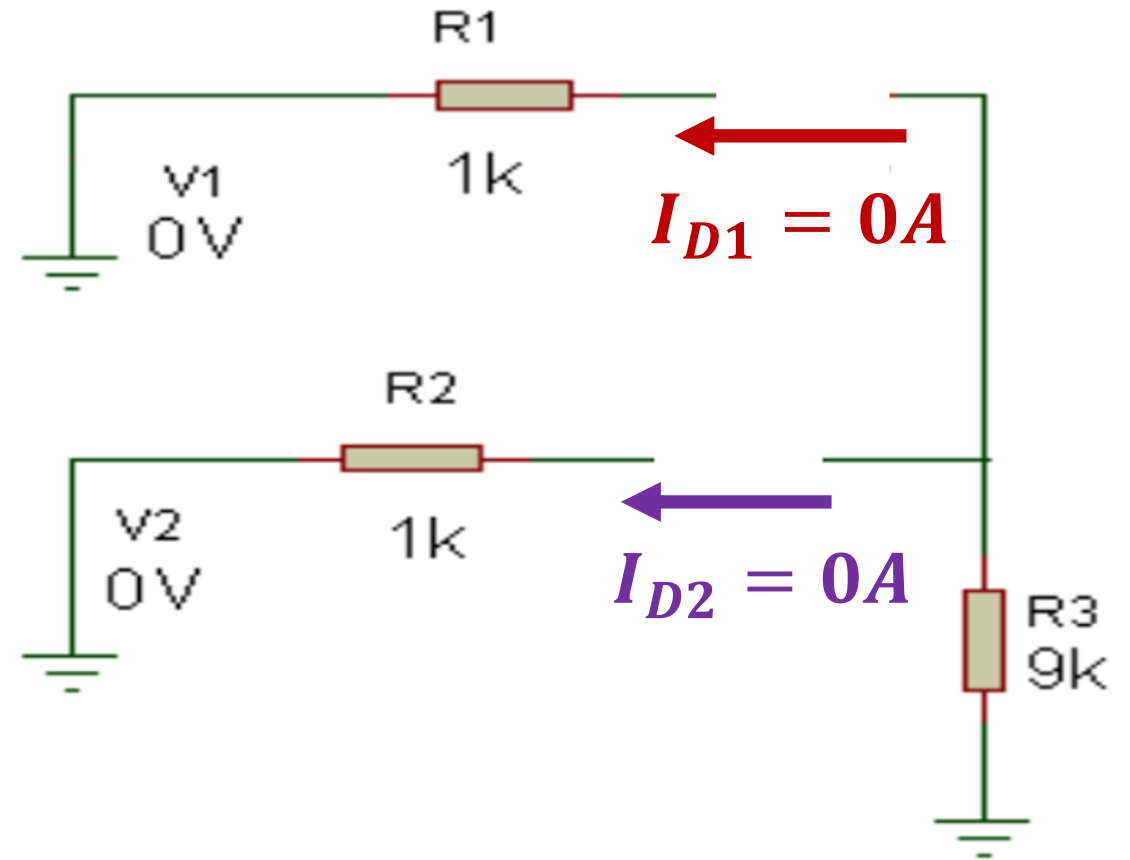

Truth Table of OR Gate

<i>Input</i>		<i>Output</i>
V_1	V_2	V_o
$0V \equiv \text{Binary } 0$	$0V \equiv \text{Binary } 0$	$0V \equiv \text{Binary } 0$
$5V \equiv \text{Binary } 1$	$0V \equiv \text{Binary } 0$	$3.87V \equiv \text{Binary } 1$
$0V \equiv \text{Binary } 0$	$5V \equiv \text{Binary } 1$	$3.87V \equiv \text{Binary } 1$
$5V \equiv \text{Binary } 1$	$5V \equiv \text{Binary } 1$	$4.07V \equiv \text{Binary } 1$

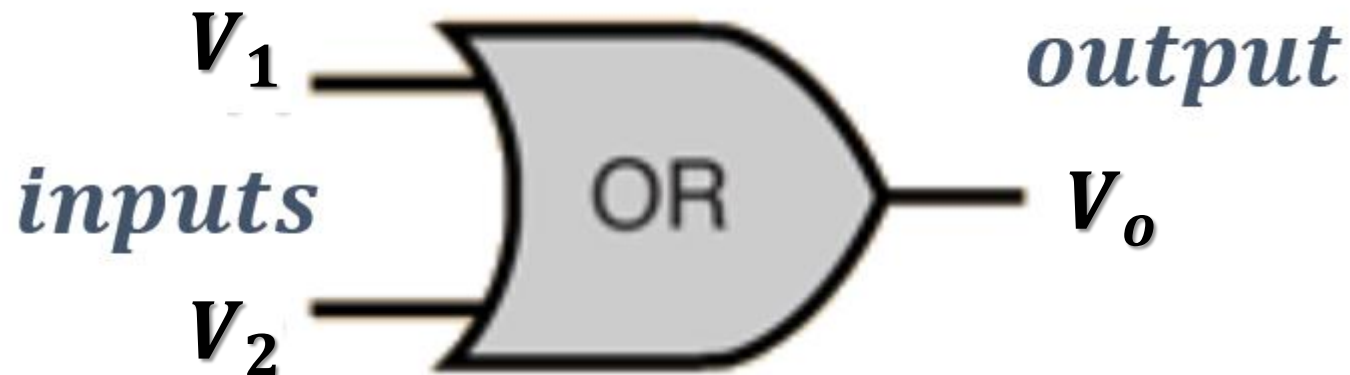

Example-2


For the circuit shown, assume identical diodes with barrier potential (V_B) of $0.6V$ and forward resistance (R_f) of 30Ω

Calculate the output voltage (V_o) for the following input voltages:

(a) $V_1=0V$ and $V_2=0V$.

(b) $V_1=5V$ and $V_2=0V$.

(c) $V_1=5V$ and $V_2=5V$.

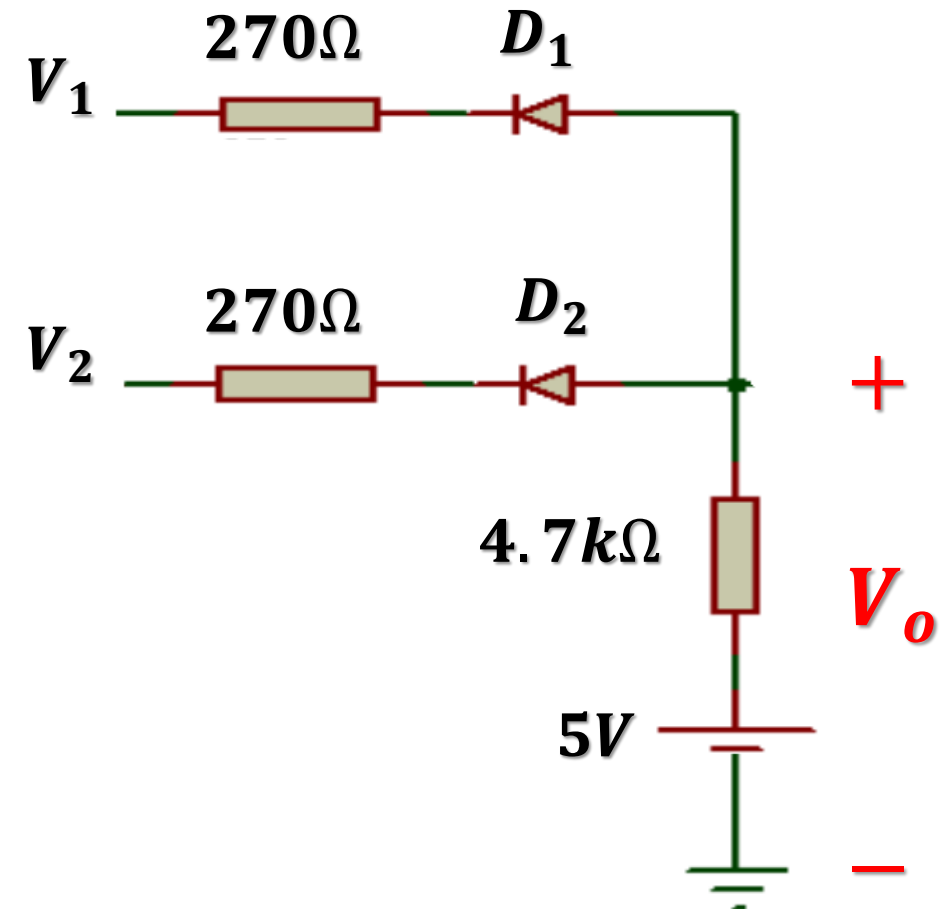

Solution:


(a) $V_1 = 0V$ and $V_2 = 0V$

Assume:

$$(V_{A1} = 4) > (V_{K1} = 0) + (V_B = 0.6)$$

$$(V_{A2} = 4) > (V_{K2} = 0) + (V_B = 0.6)$$

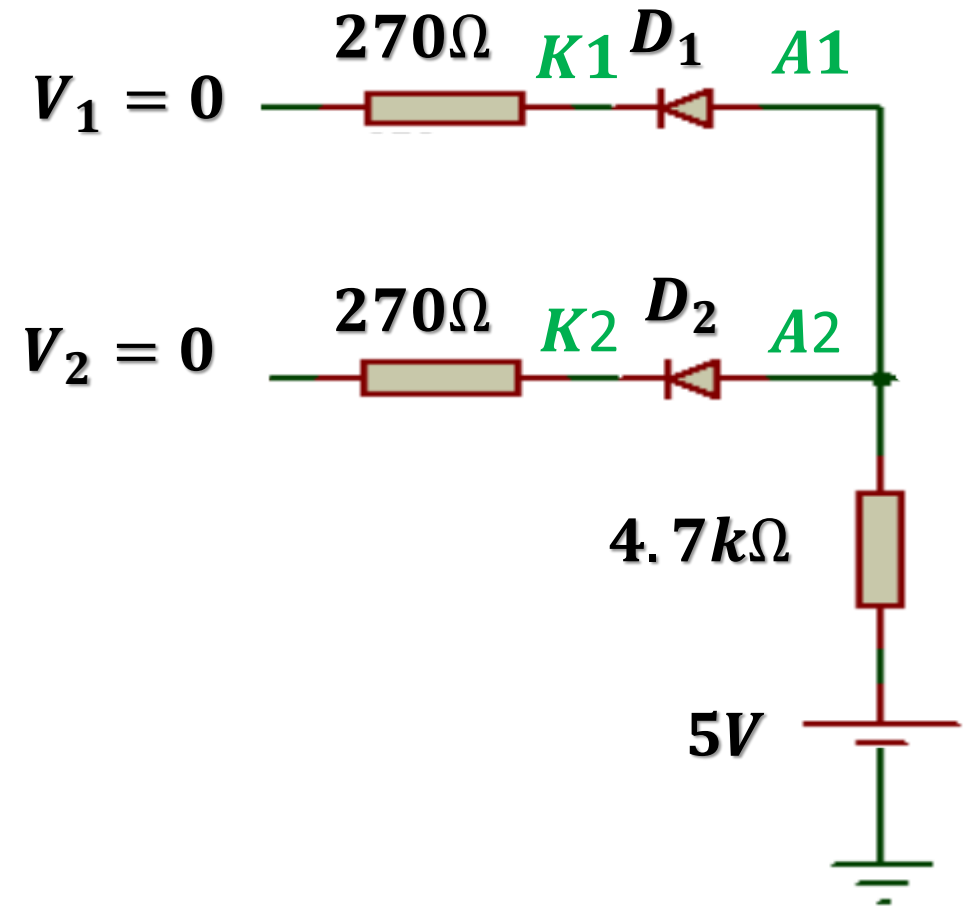\therefore Assume D_1 and D_2 are forward




$$\sum V \text{ in closed loop} = 0$$

$$5 - (4700)(I_1 + I_2) - 0.6 - (30 + 270) I_1 = 0$$

$$5 - (4700)(I_1 + I_2) - 0.6 - (30 + 270)I_2 = 0$$

$$I_1 = 0.454 \text{mA}$$

$$I_2 = 0.454 \text{mA}$$

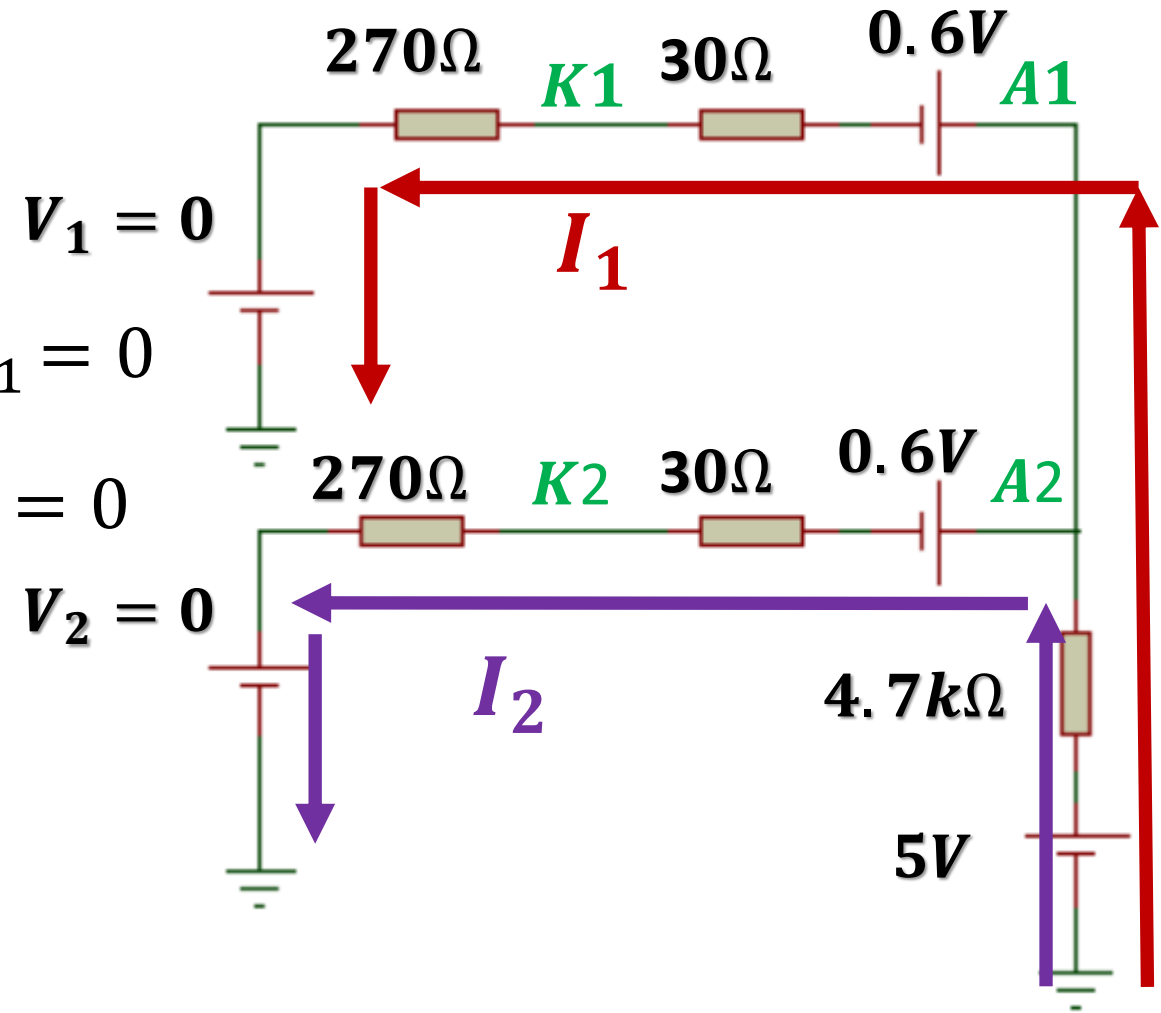

The positive value of currents indicates our assumption is true (D_1 and D_2 are forward).


To find $\mathbf{V_o}$, write KVL between $\mathbf{V_o}$ and **the branch** (that you calculate on it the voltage drop):

$$5 - 4.7k (I_1 + I_2) - V_o = 0$$

$$5 - 4.7k (0.454mA + 0.454mA) = V_o$$

$$5 - 4.3 = V_o$$

$$V_o = 0.7V$$

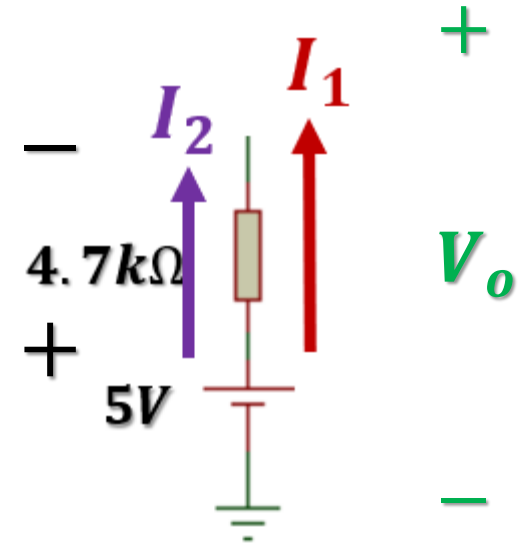


(b) $V_1 = 5V$ and $V_2 = 0V$

Assume:

$$(V_{A1} = 4) < (V_{K1} = 4.5) + (V_B = 0.6)$$

$$(V_{A2} = 4) > (V_{K2} = 0) + (V_B = 0.6)$$

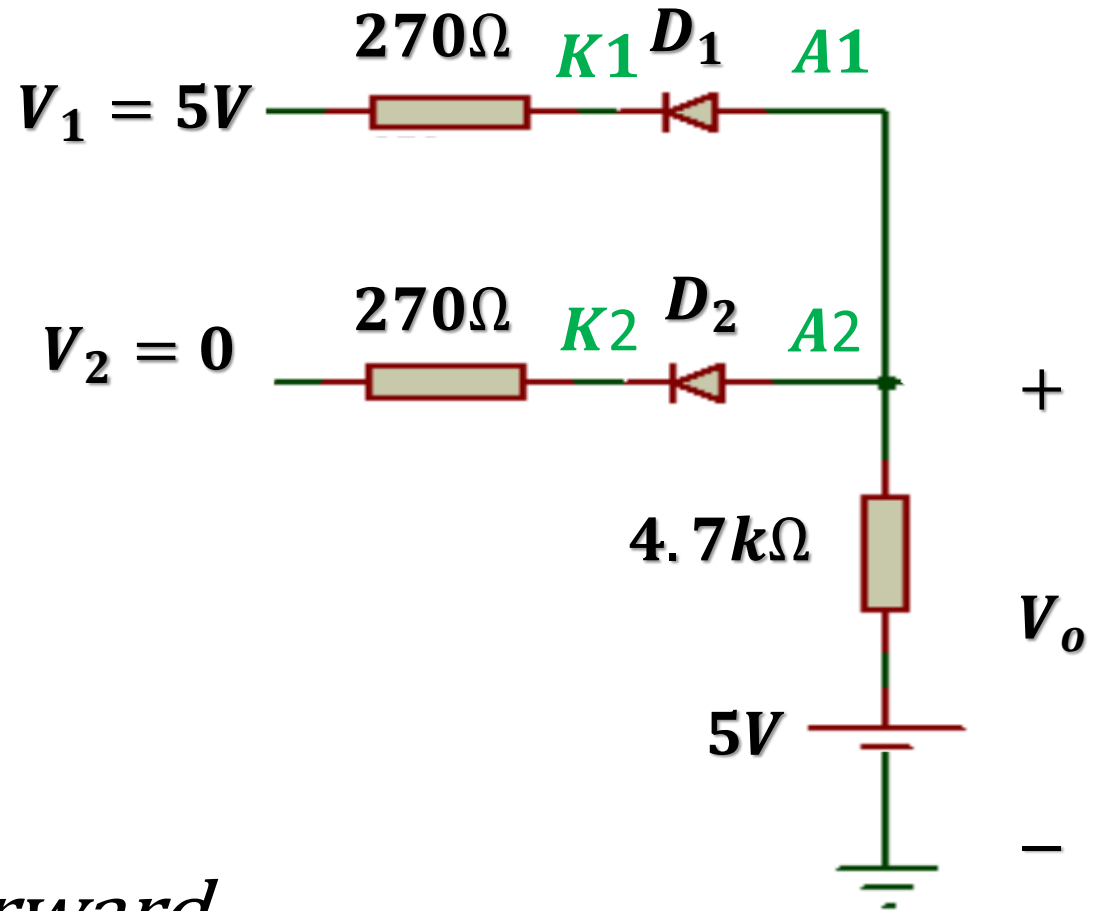\therefore Assume D_1 is reverse and D_2 is forward




$$\sum V \text{ in closed loop} = 0$$

$$5 - 4700 I_2 - 0.6 - (30 + 270)I_2 = 0$$

$$4.4 - 5000I_2 = 0$$

$$4.4 = 5000I_2$$

$$\frac{4.4}{5000} = I_2 = 0.88mA$$

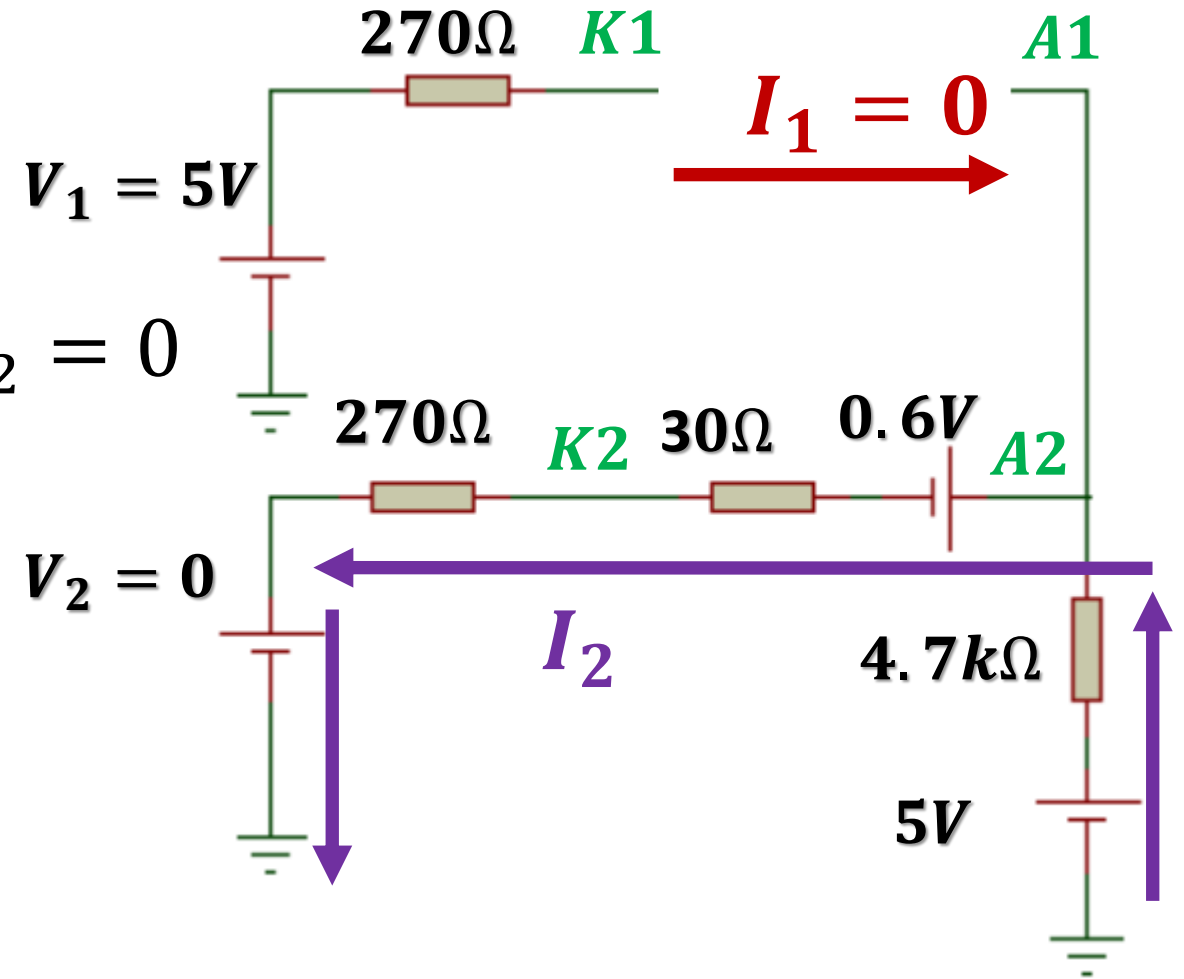

The positive value of current indicates our assumption is true (D_2 is forward).


To find $\mathbf{V_o}$, write KVL between $\mathbf{V_o}$ and **the branch** (that you calculate on it the voltage drop):

$$5 - 4.7k \times I_2 - V_o = 0$$

$$5 - 4.7k \times 0.88mA = V_o$$

$$5 - 4.1 = V_o$$

$$V_o = 0.9V$$

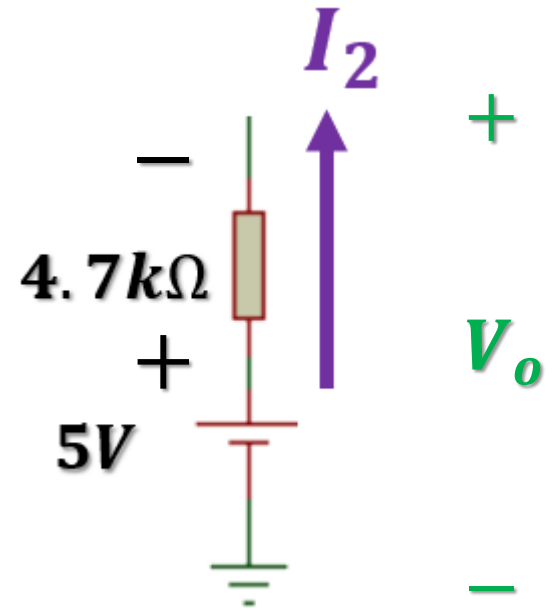


(c) $V_1 = 5V$ and $V_2 = 5V$

Assume:


$$(V_{A1} = 4) < (V_{K1} = 4.5) + (V_B = 0.6)$$

$$(V_{A2} = 4) < (V_{K2} = 4.5) + (V_B = 0.6)$$

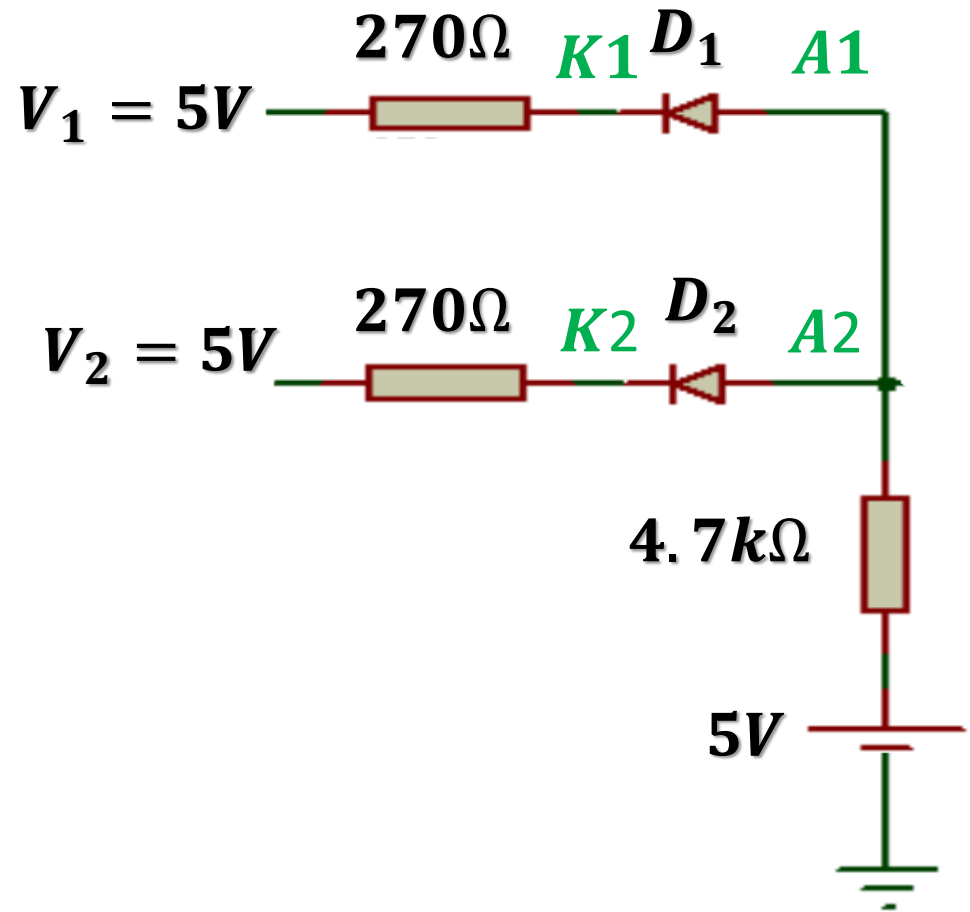\therefore Assume D_1 and D_2 are reverse




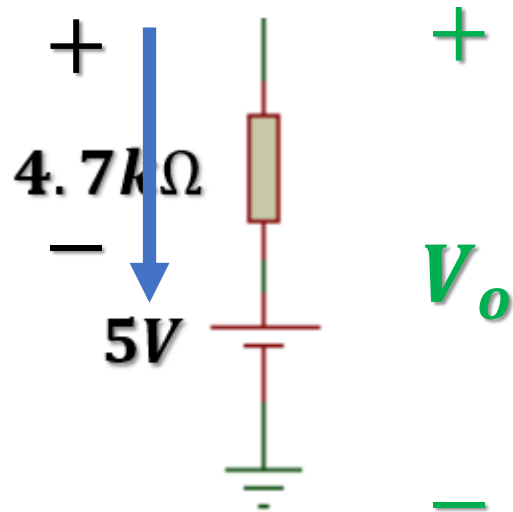To find V_o , write KVL between V_o and **the branch** (that you calculate on it the voltage drop):



$$5 + 4.7k \times (0A) - V_o = 0$$

$$V_o = 5V$$

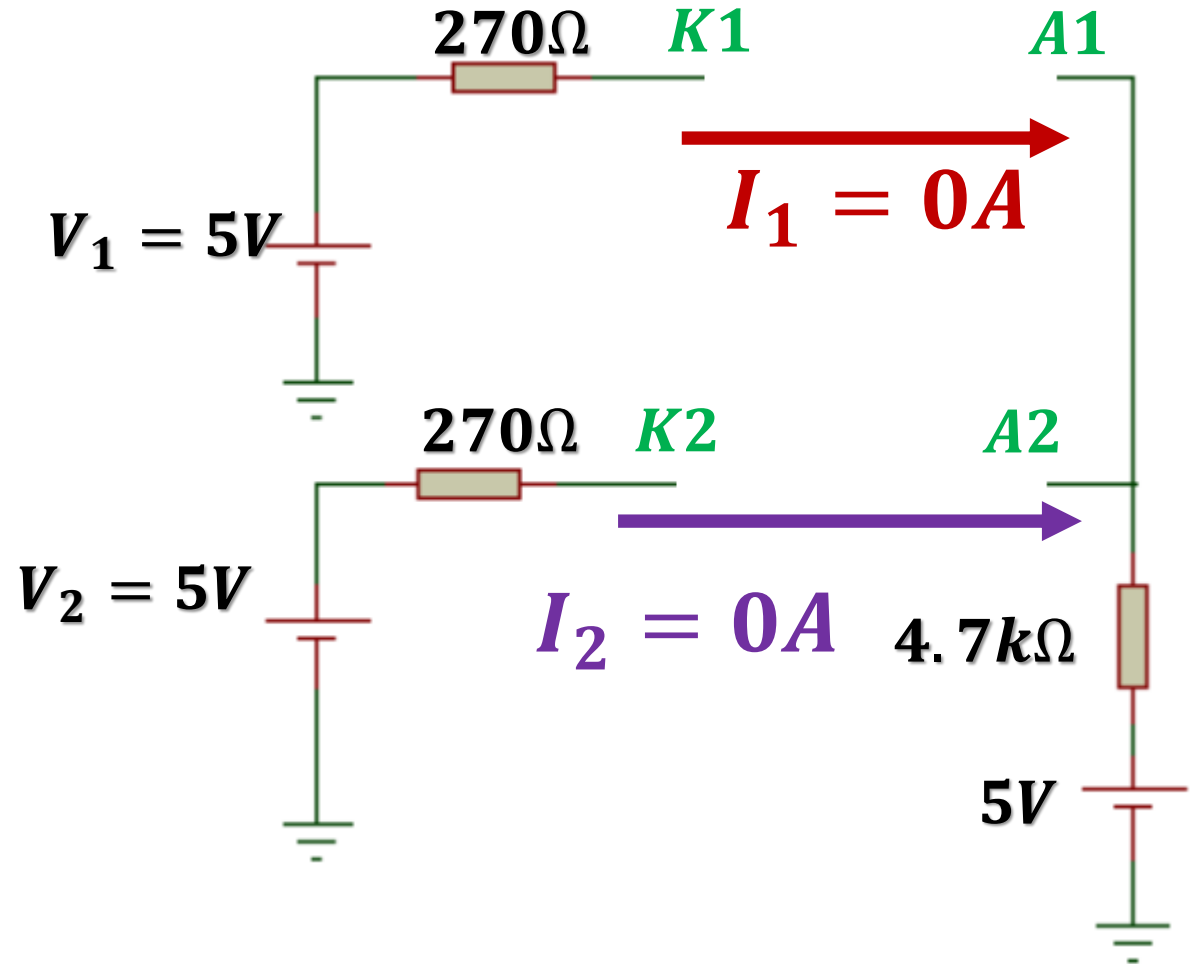


Truth Table of AND Gate

<i>Input</i>		<i>Output</i>
V_1	V_2	V_o
$0V \equiv \text{Binary } 0$	$0V \equiv \text{Binary } 0$	$0.7V \equiv \text{Binary } 0$
$5V \equiv \text{Binary } 1$	$0V \equiv \text{Binary } 0$	$0.9V \equiv \text{Binary } 0$
$0V \equiv \text{Binary } 0$	$5V \equiv \text{Binary } 1$	$0.9V \equiv \text{Binary } 0$
$5V \equiv \text{Binary } 1$	$5V \equiv \text{Binary } 1$	$5V \equiv \text{Binary } 1$




❑ Clipping Circuits

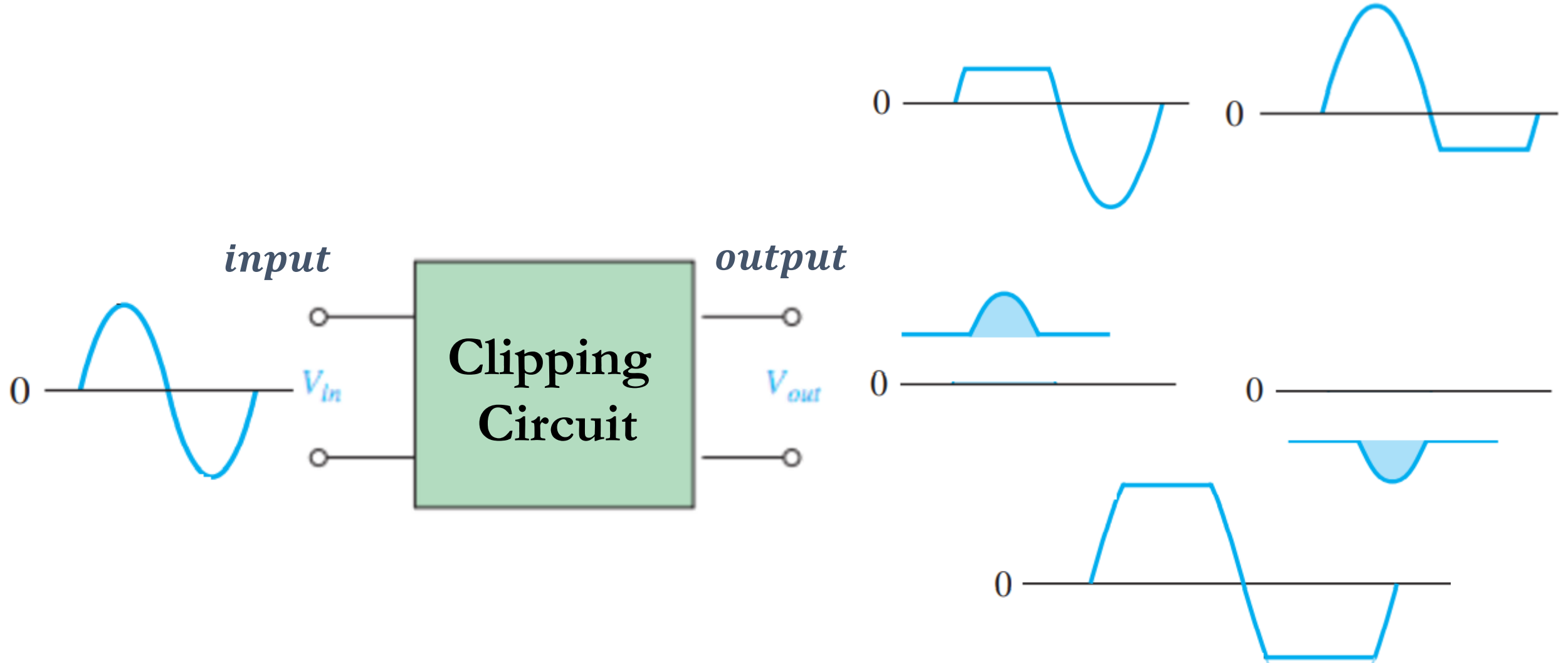Used to clip off (cut) parts of input signal above or below certain levels.



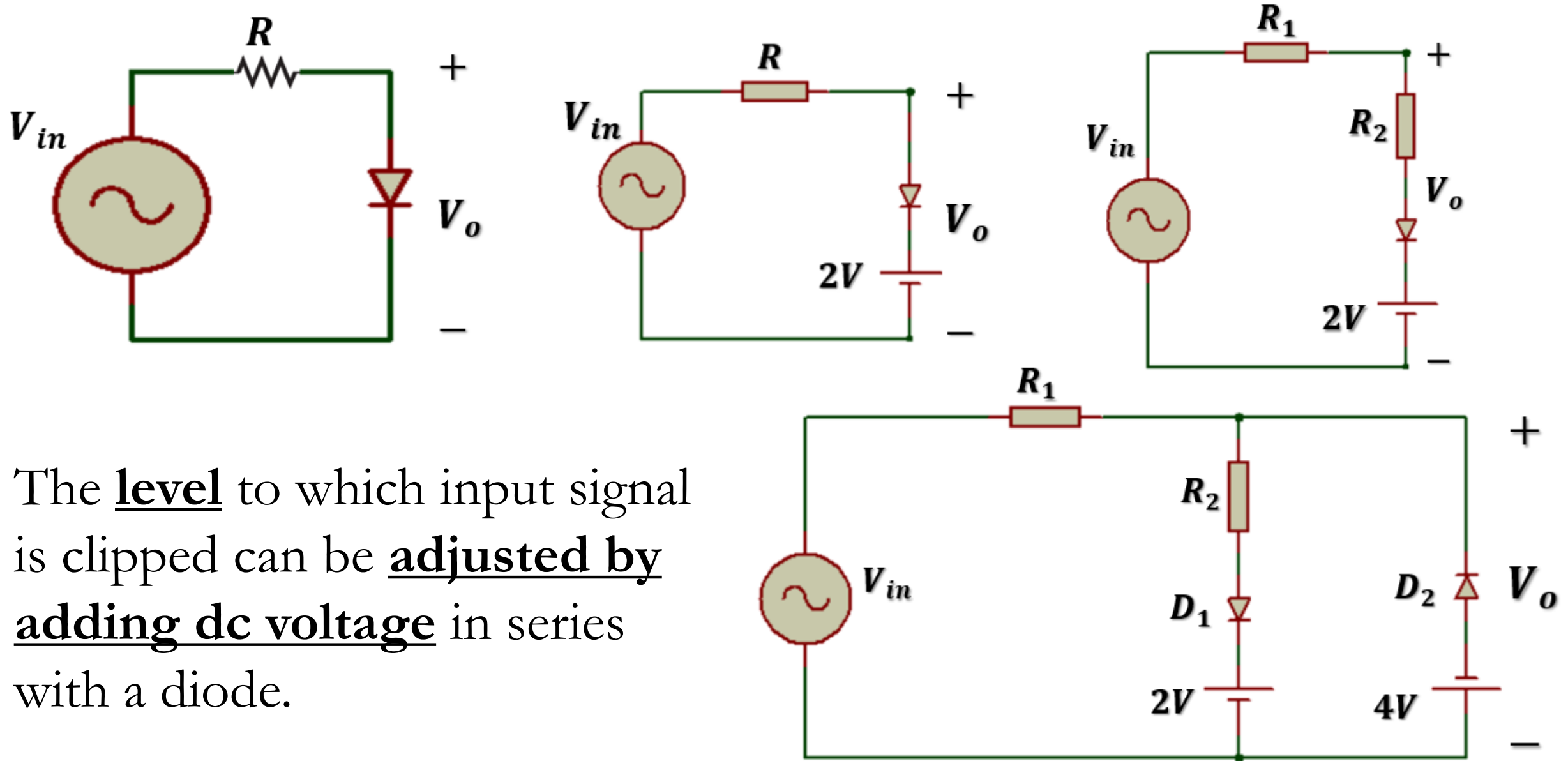Clipping circuits can be made by combining diodes and resistors.




The level to which input signal is clipped can be adjusted by adding dc voltage in series with a diode.

Sketch the output voltage waveform (V_o versus time), assuming ideal diode and $V_{in} = 5 \sin \omega t$.


Diode is reverse and appears as open switch (ideal diode) when:


$$V_A \leq V_K + V_B$$

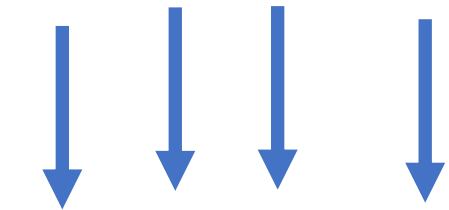

$$V_{in} \leq 0 + 0$$


$$V_{in} \leq 0$$

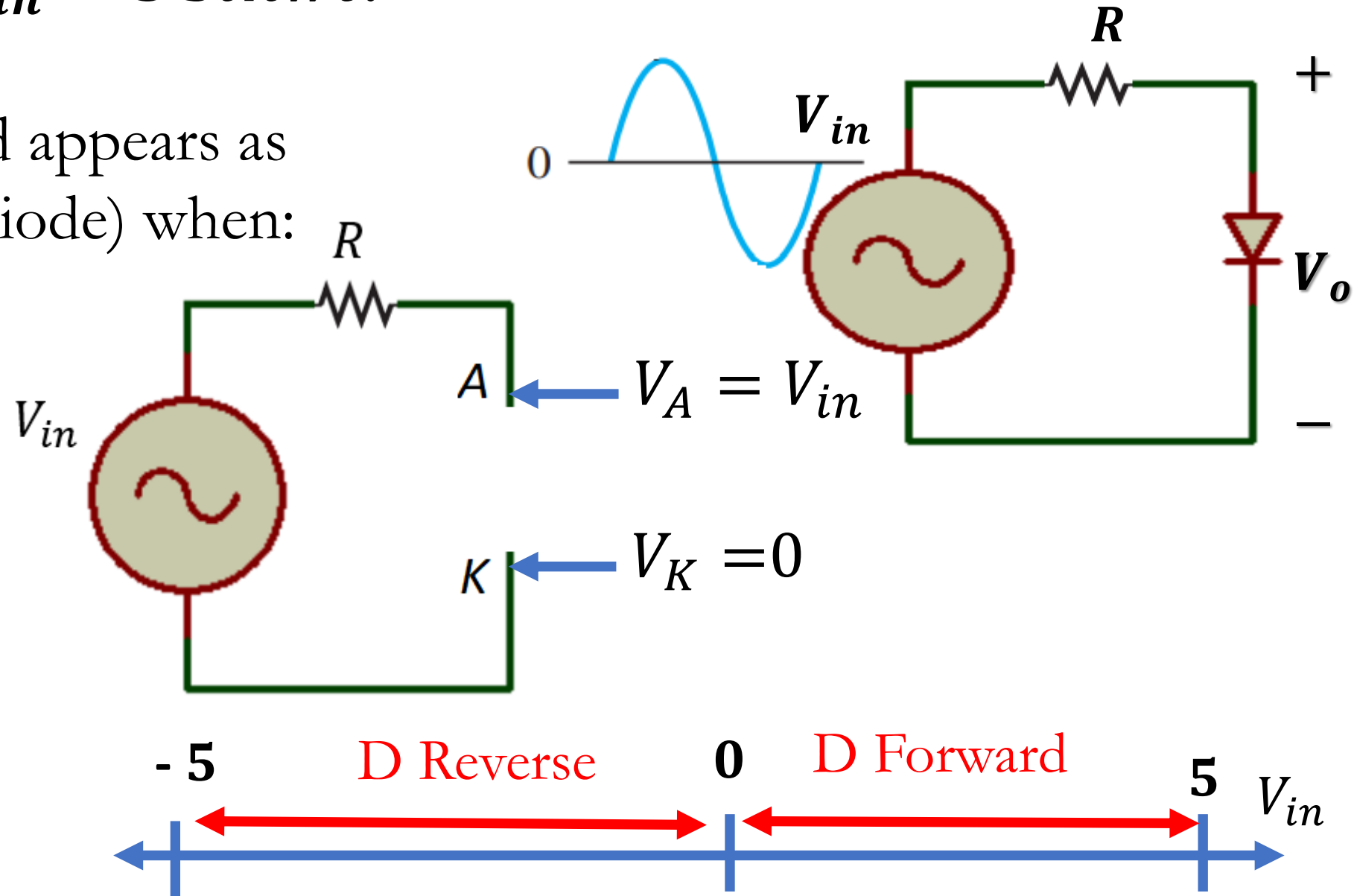

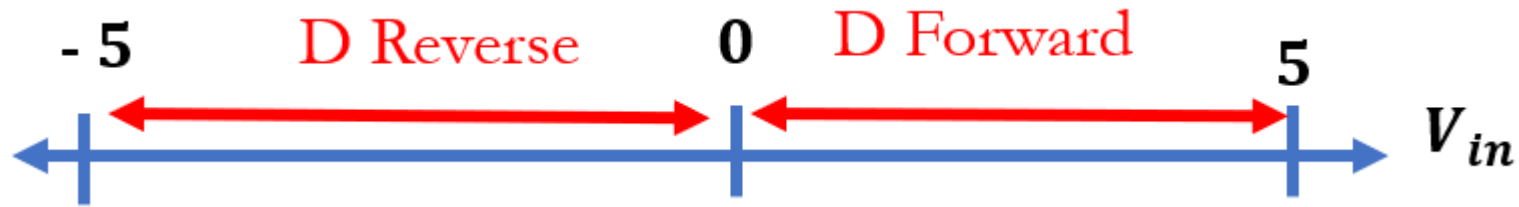

[1] $-5 \leq V_{in} \leq 0$

D is reverse

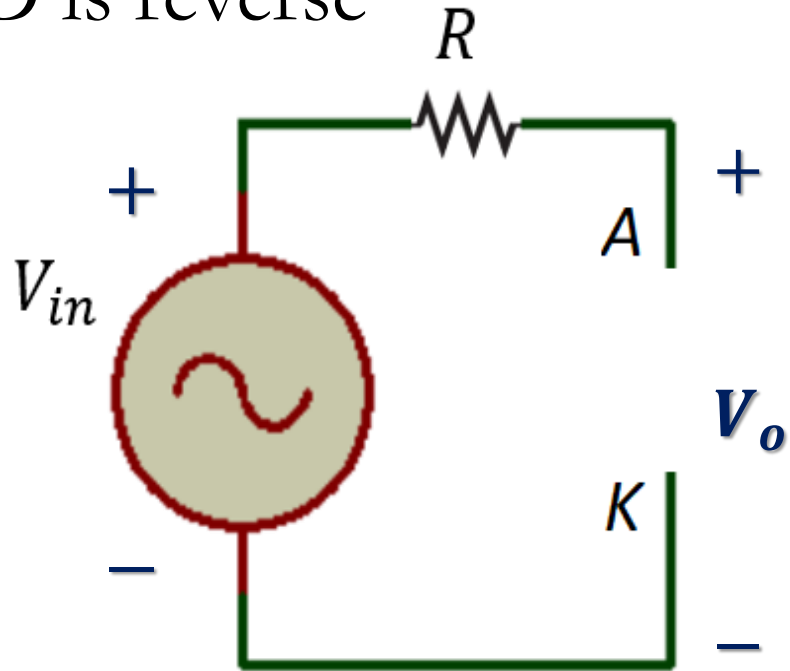


$$V_o - V_{in} = 0$$


$$V_o = V_{in}$$

[2] $0 < V_{in} \leq 5$


D is forward

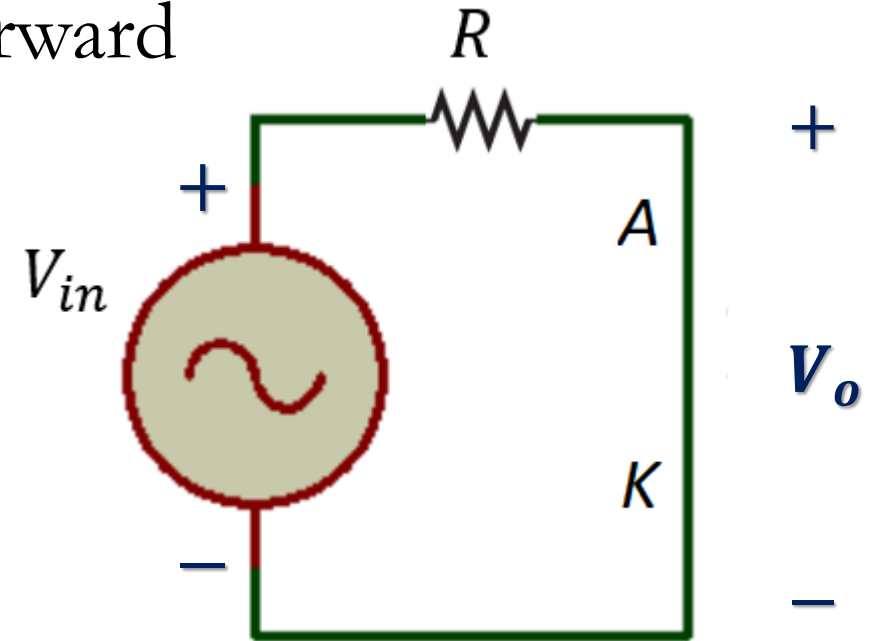

$$V_o = 0V$$

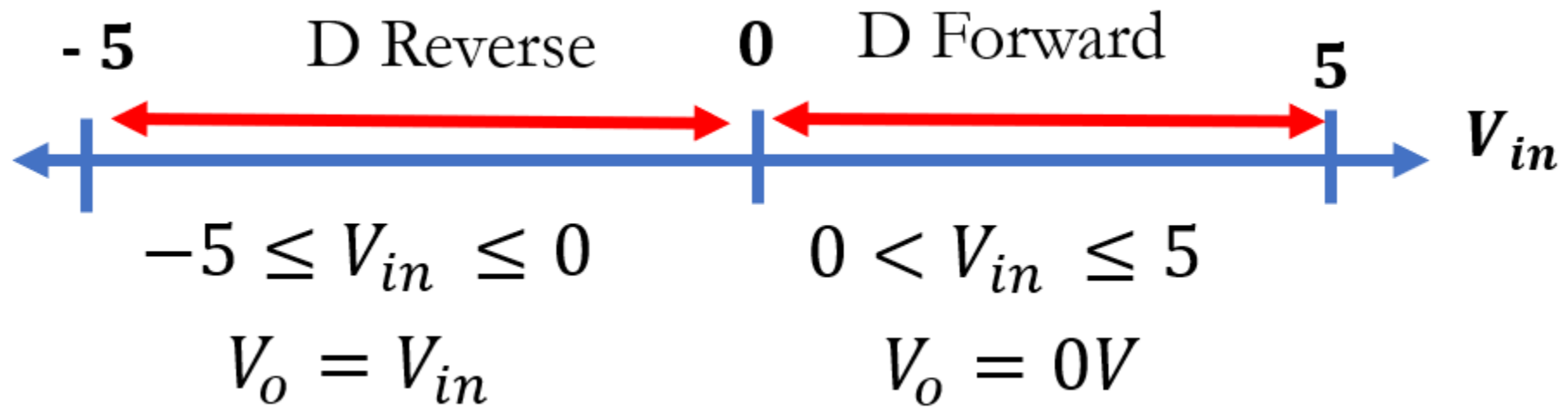


The output voltage waveform:

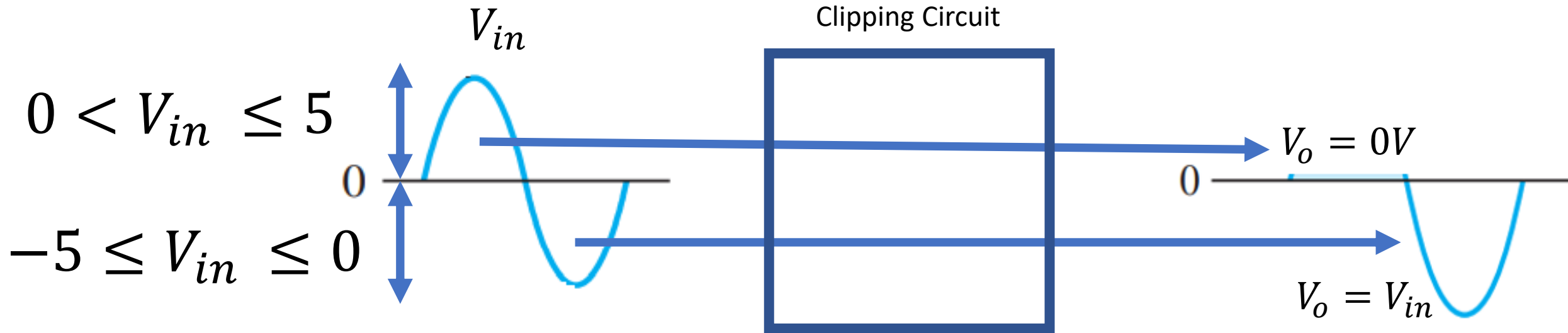

Sketch the output voltage waveform, assuming practical diode with barrier potential $V_B = 0.7V$ and $V_{in} = 5 \sin \omega t$


Diode is reverse and appears as open switch ($R_r = \infty$) when:


$$V_A \leq V_K + V_B$$

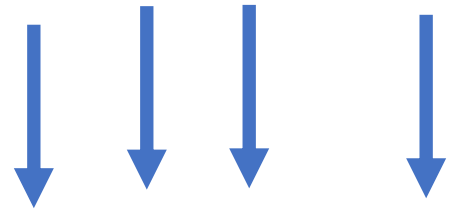

$$V_{in} \leq 0 + 0.7$$


$$V_{in} \leq 0.7$$

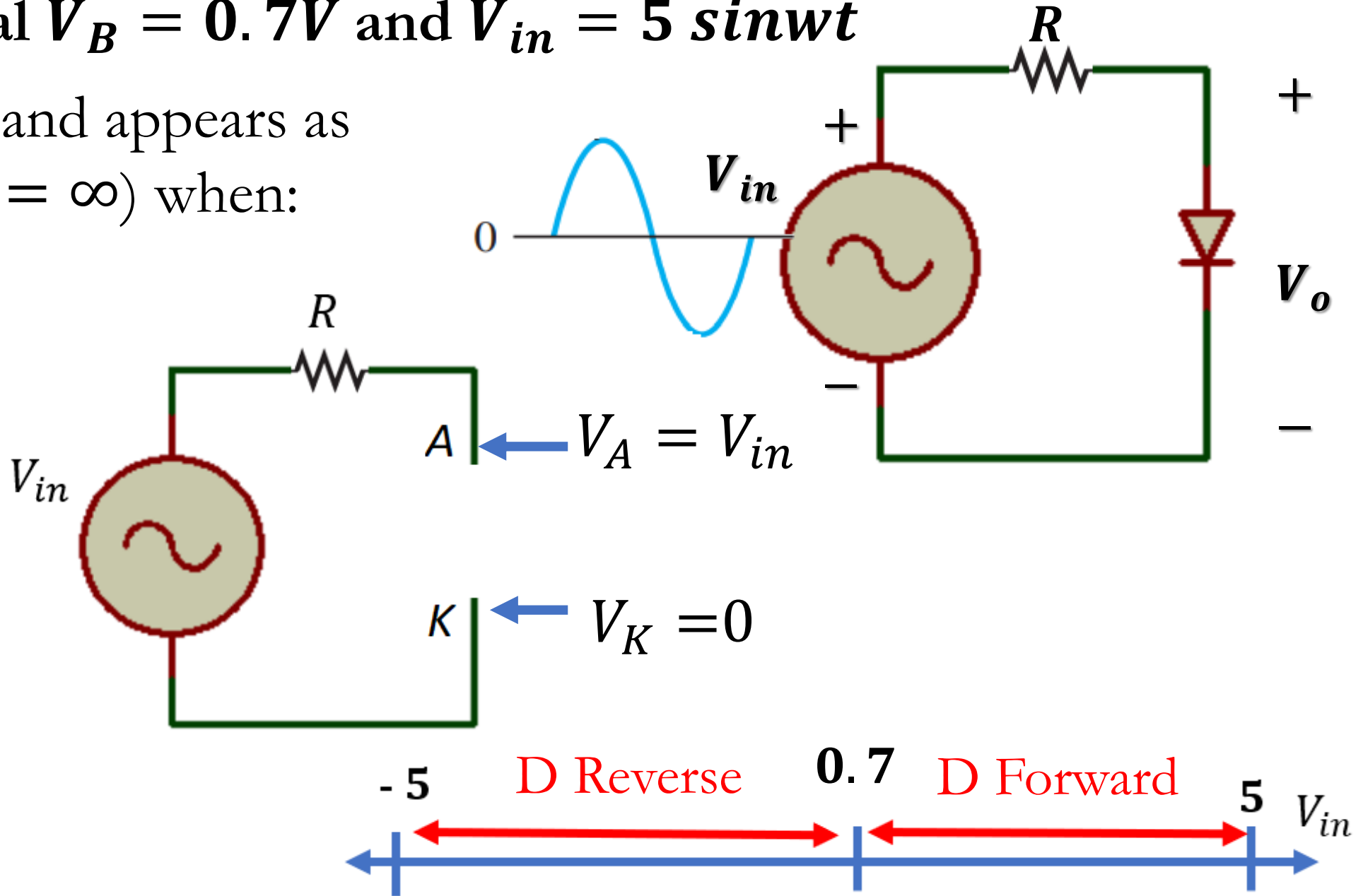

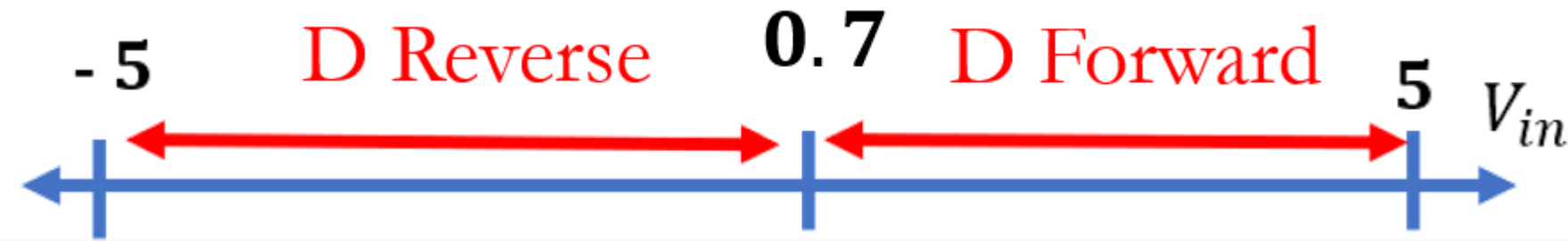

[1] $-5 \leq V_{in} \leq 0.7$

D is reverse

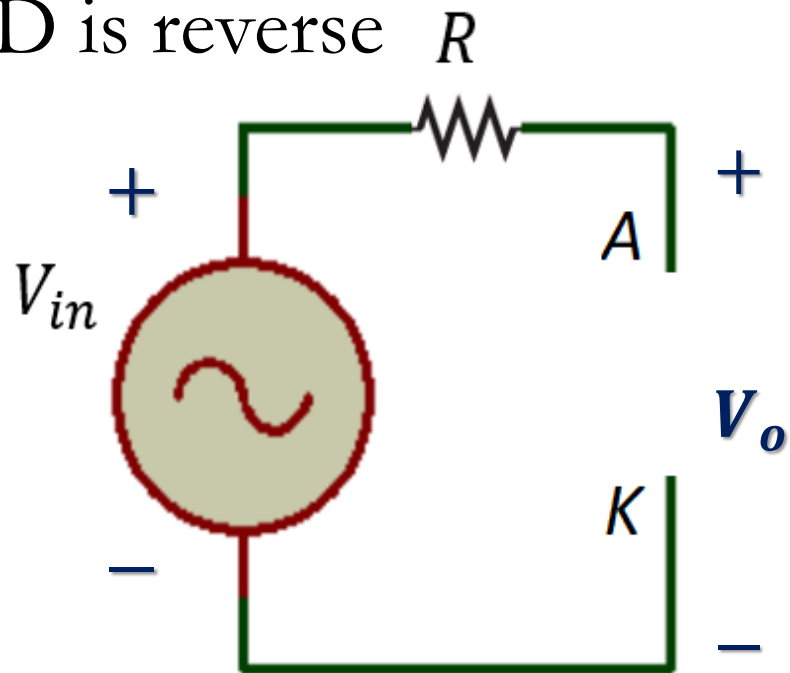


$$V_o - V_{in} = 0$$

$$V_o = V_{in}$$


[2] $0.7 < V_{in} \leq 5$

D is forward

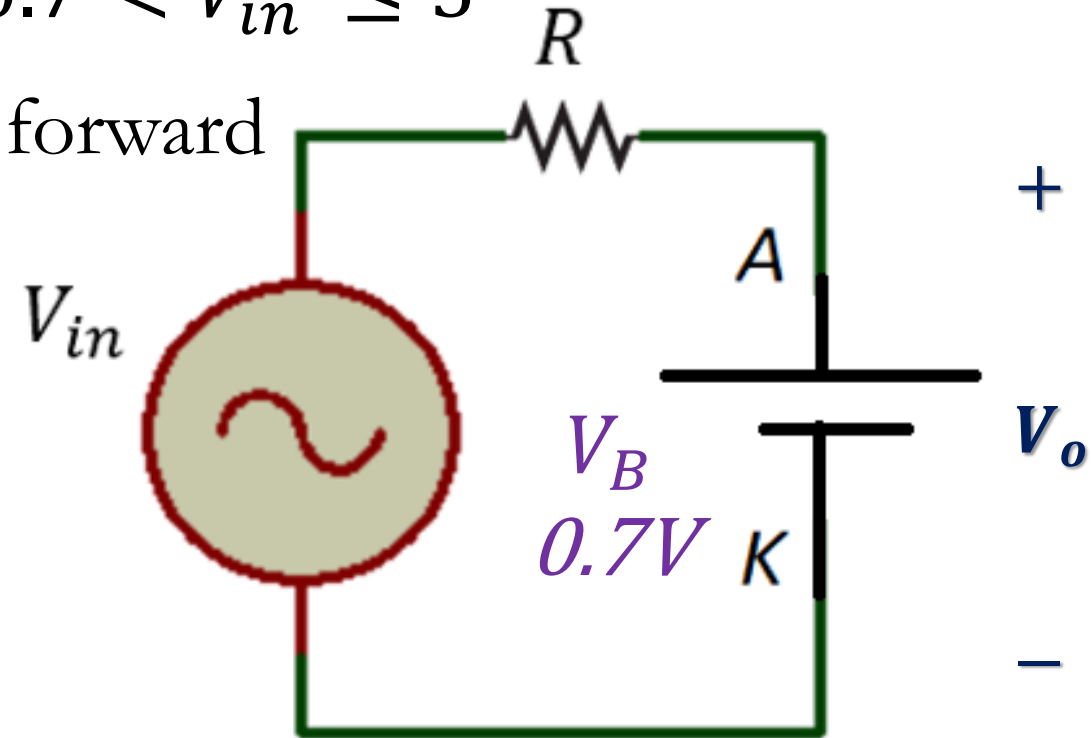


$$V_o - 0.7 = 0$$

$$V_o = 0.7V$$

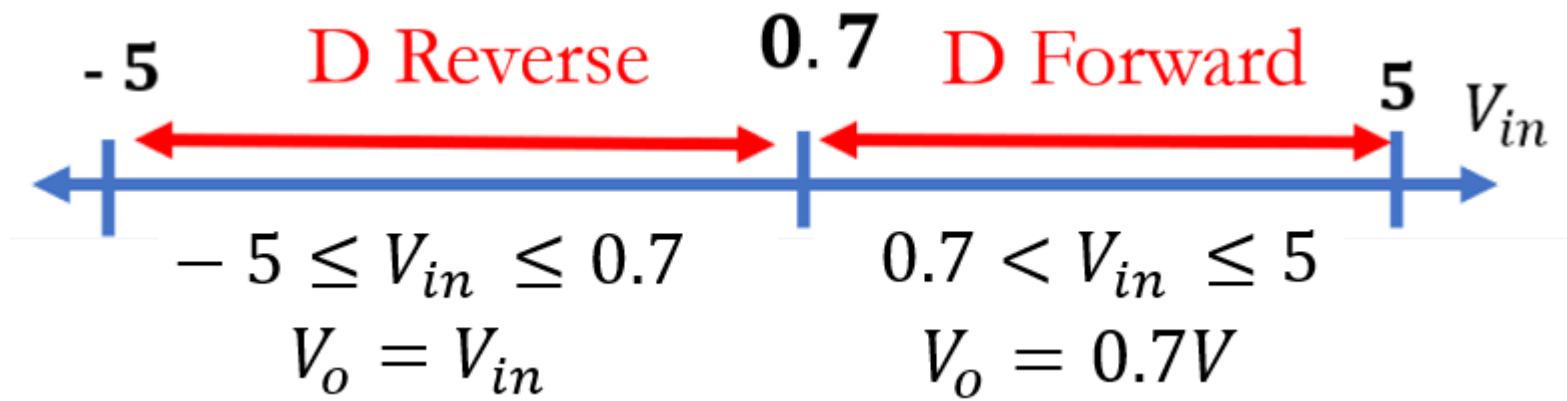


The output voltage waveform:

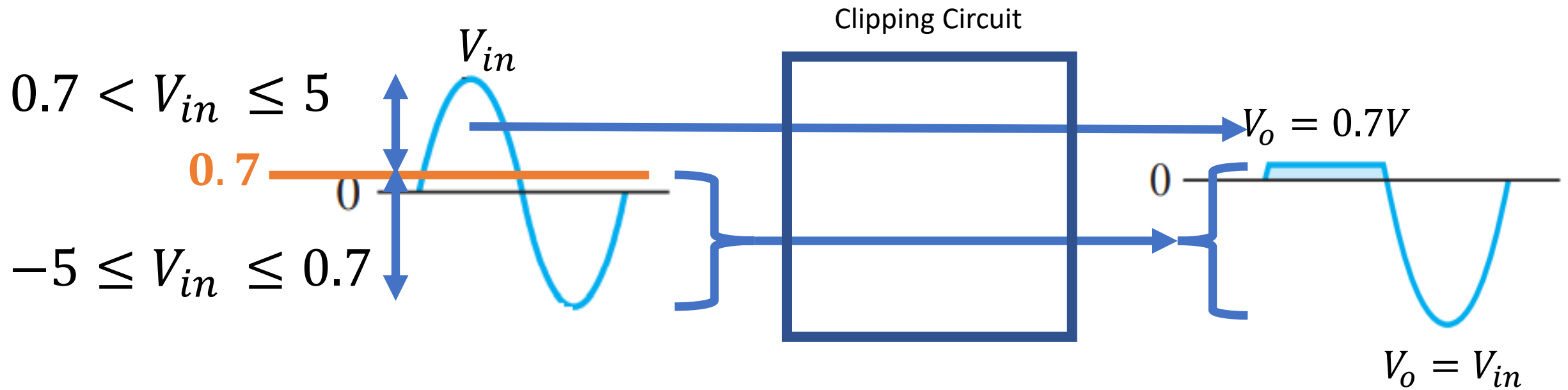

Sketch the output voltage waveform, assuming practical diode with barrier potential $V_B = 0.7V$ and $V_{in} = 5 \sin \omega t$


Diode is reverse and appears as open switch ($R_r = \infty$) when:


$$V_A \leq V_K + V_B$$

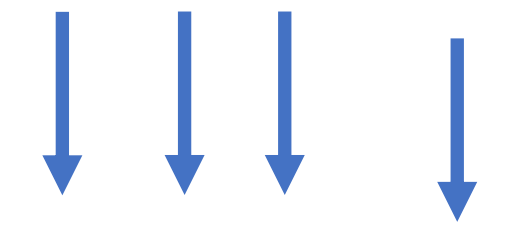

$$V_{in} \leq 2 + 0.7$$


$$V_{in} \leq 2.7$$

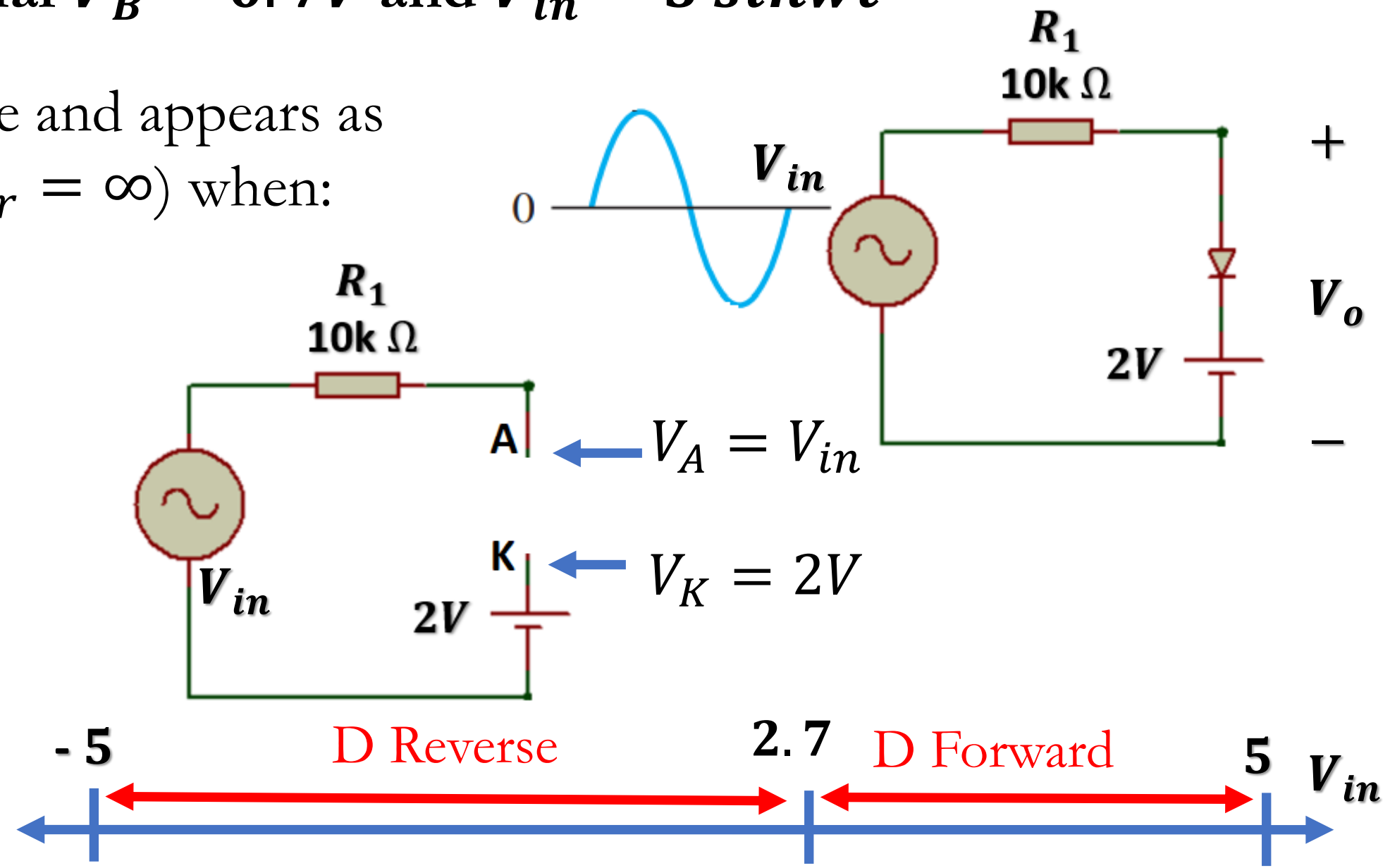

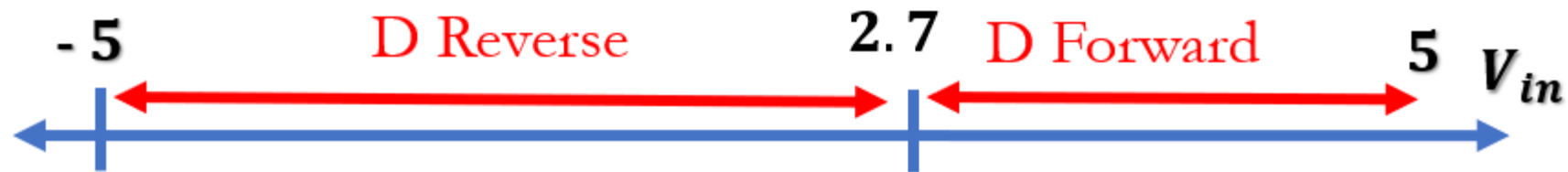

$$[1] -5 \leq V_{in} \leq 2.7$$

D is reverse

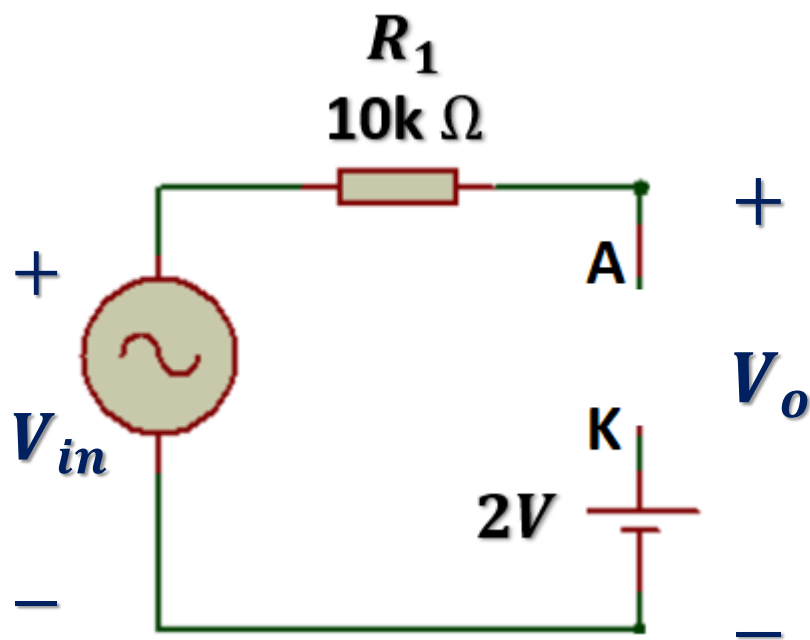


$$V_o - V_{in} = 0$$

$$V_o = V_{in}$$


$$[2] 2.7 < V_{in} \leq 5$$

D is forward

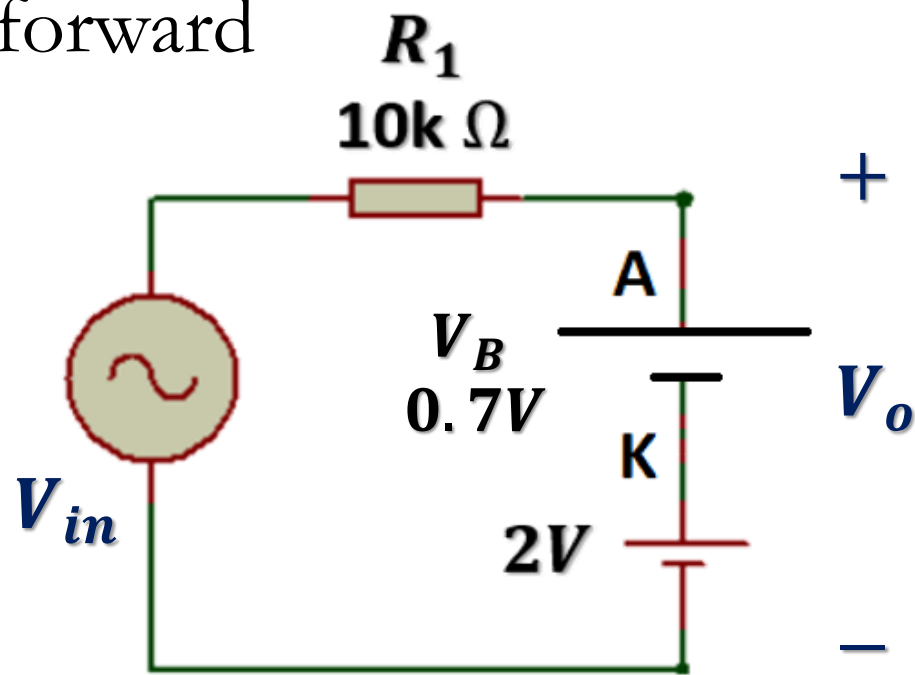


$$V_o - 0.7 - 2 = 0$$

$$V_o = 2.7V$$

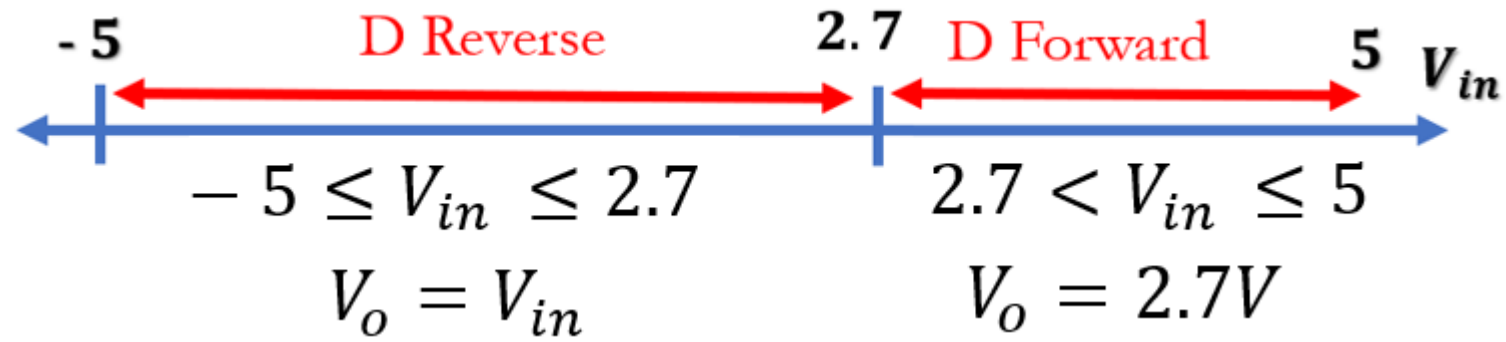


The output voltage waveform:

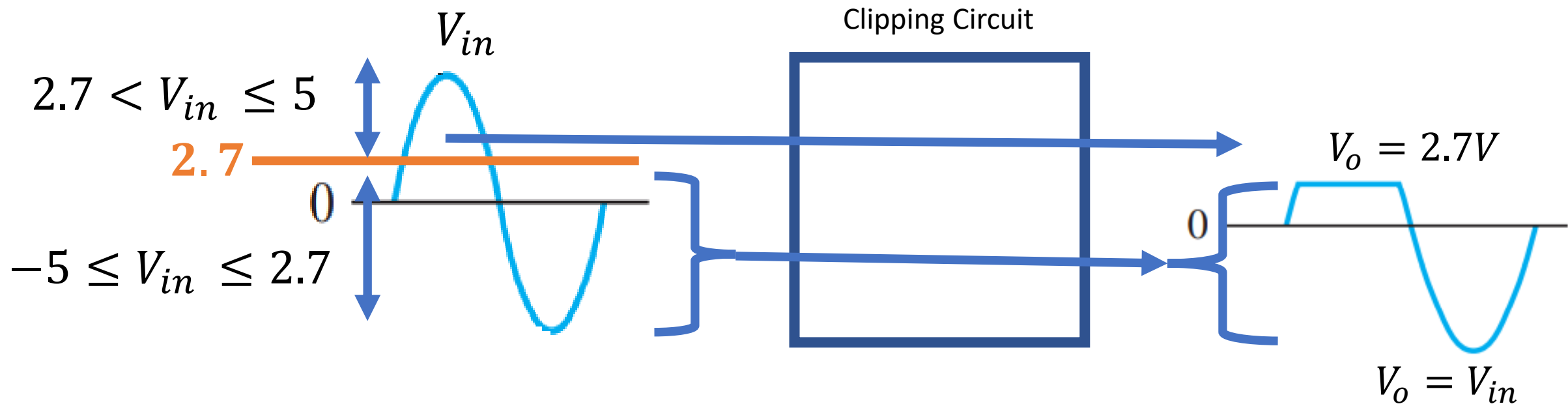

Sketch the output voltage waveform, assuming a practical diode with barrier potential $V_B = 0.6V$ and $V_{in} = 5 \sin \omega t$.




Diode is reverse and appears as open switch ($R_r = \infty$) when:

$$V_A \leq V_K + V_B$$

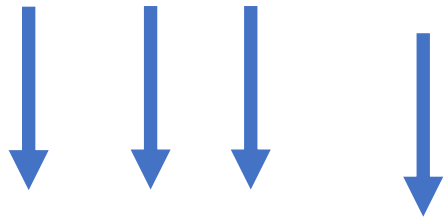

$$V_{in} \leq 2 + 0.6$$


$$V_{in} \leq 2.6$$

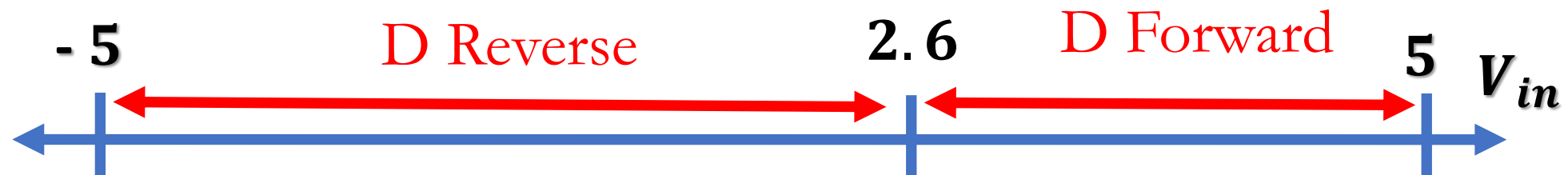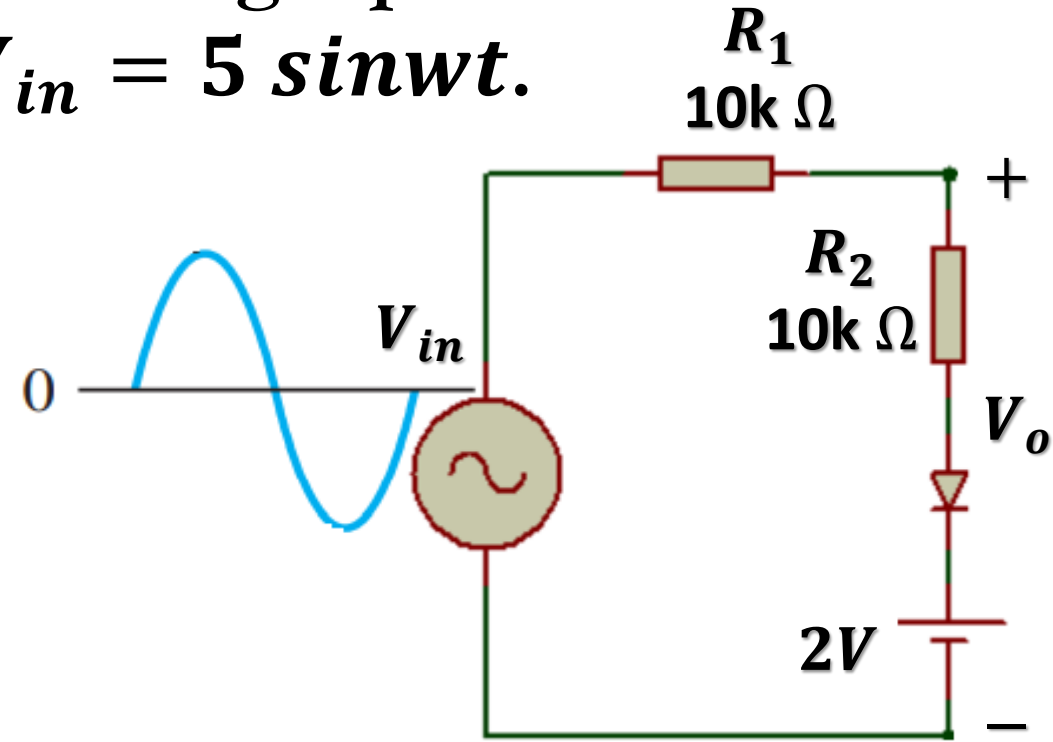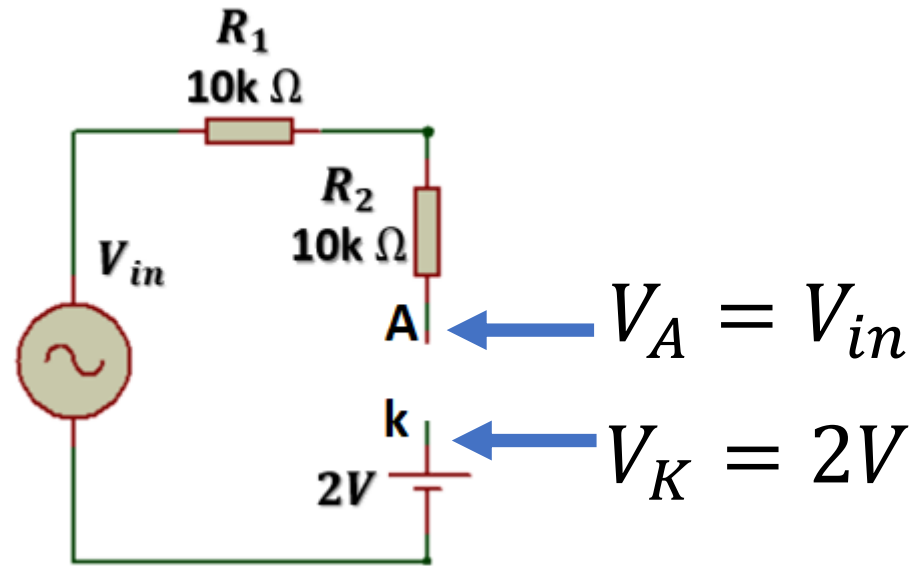



$$[1] -5 \leq V_{in} \leq 2.6$$

D is reverse

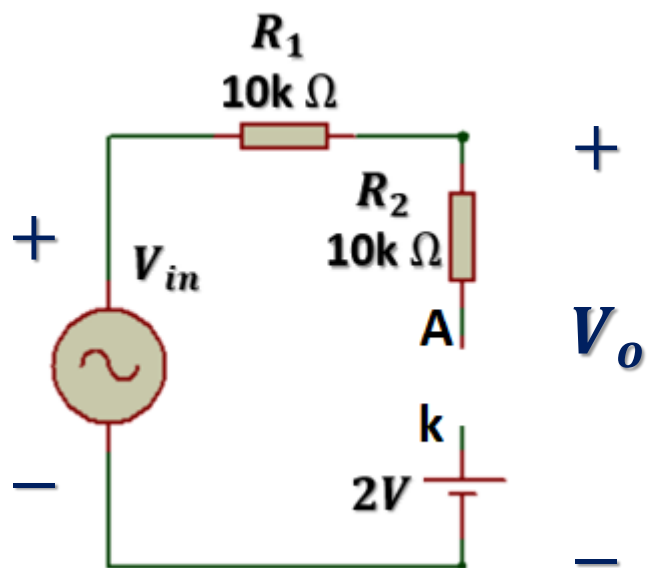


$$V_o - V_{in} = 0$$

$$V_o = V_{in}$$

$$[2] 2.6 < V_{in} \leq 5$$

D is forward

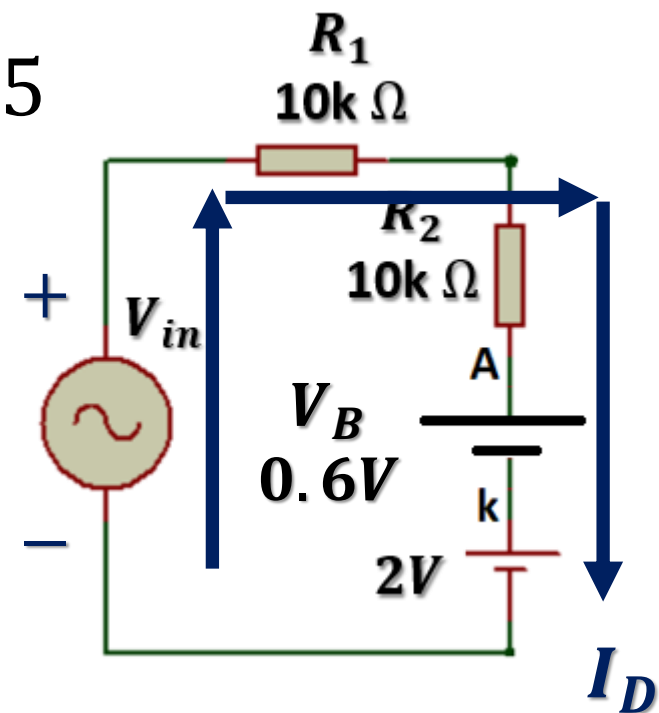

$$\sum V \text{ in closed loop} = 0$$

$$V_{in} - I_D(10k + 10k) - 0.6 - 2 = 0$$

$$\frac{V_{in} - 2.6}{20k} = I_D$$

To find V_o , write KVL between V_o and **the branch** (that you calculate on it the voltage drop):


$$V_o - I_D(10k) - 0.6 - 2 = 0$$


$$V_o = I_D(10k) + 2.6$$

$$\therefore I_D = \frac{V_{in} - 2.6}{20k}$$


$$V_o = \left(\frac{V_{in} - 2.6}{20k} \right) (10k) + 2.6$$

$$V_o = \frac{V_{in} - 2.6}{2} + 2.6$$

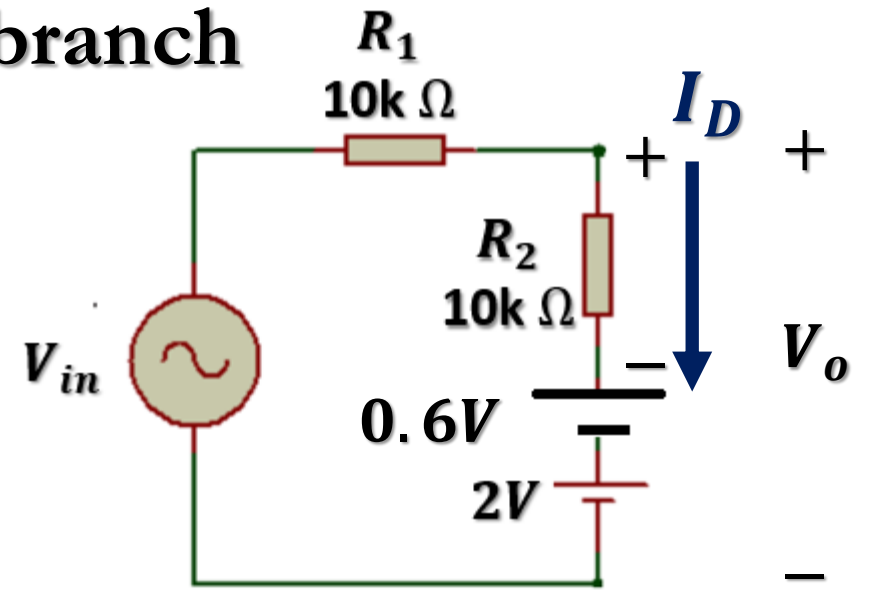

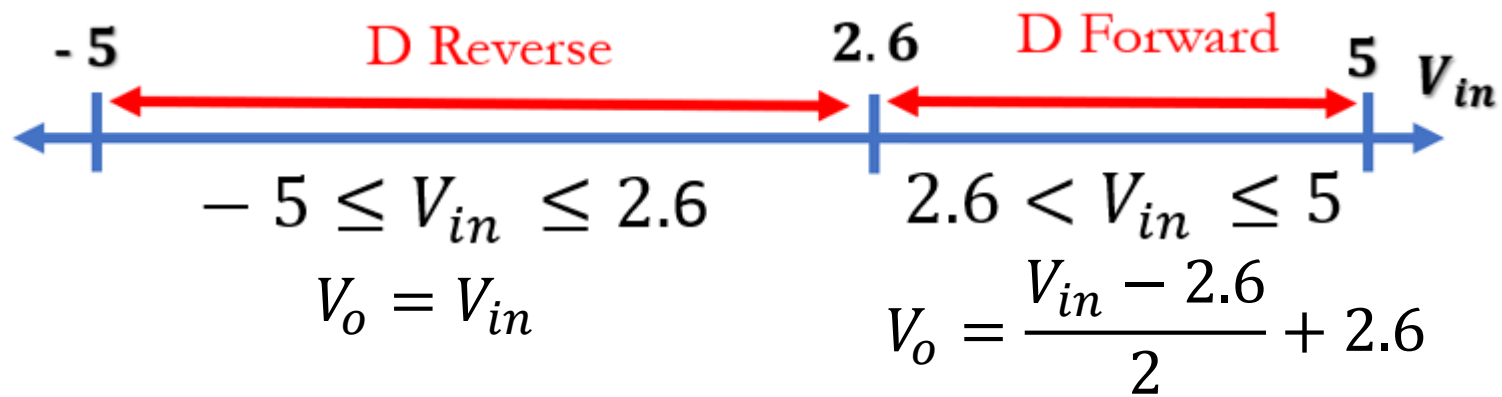


The output voltage waveform:

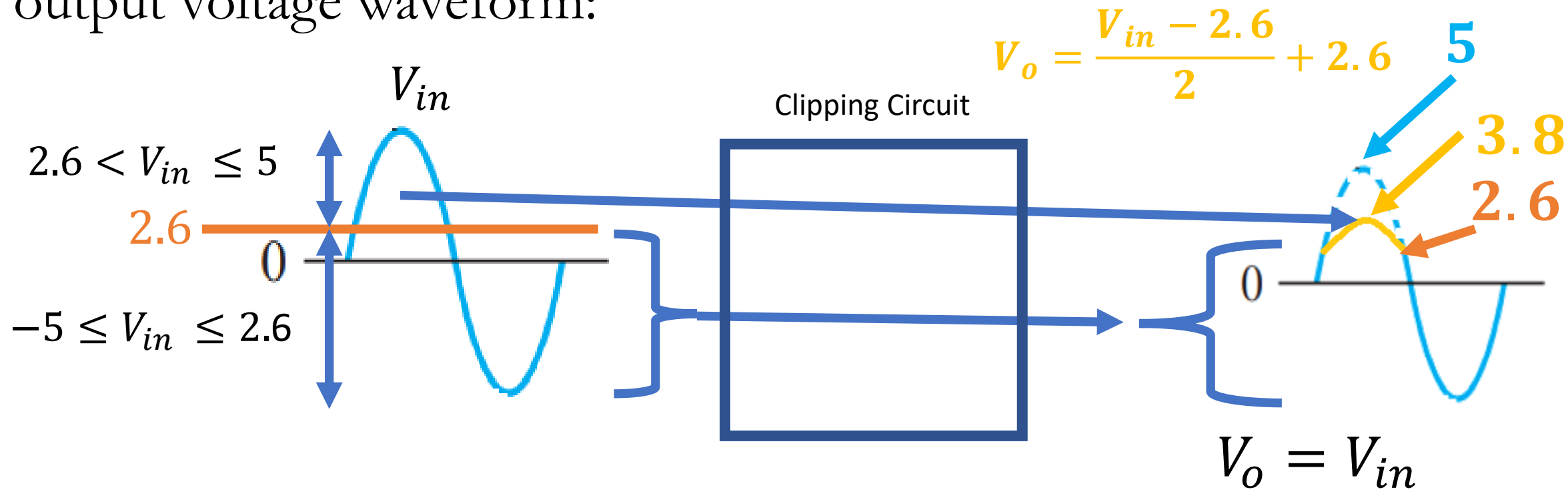

Sketch the output voltage waveform, assuming practical diode with barrier potential $V_B = 0.7V$ and $V_{in} = 5 \sin \omega t$

Diode is reverse and appears as open switch ($R_r = \infty$) when:


$$V_A \leq V_K + V_B$$

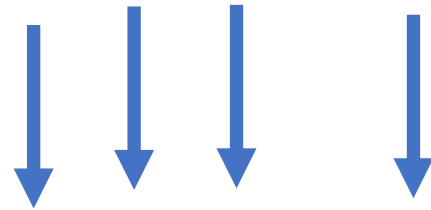


$$2 \leq V_{in} + 0.7$$

$$2 - 0.7 \leq V_{in}$$


$$1.3 \leq V_{in}$$

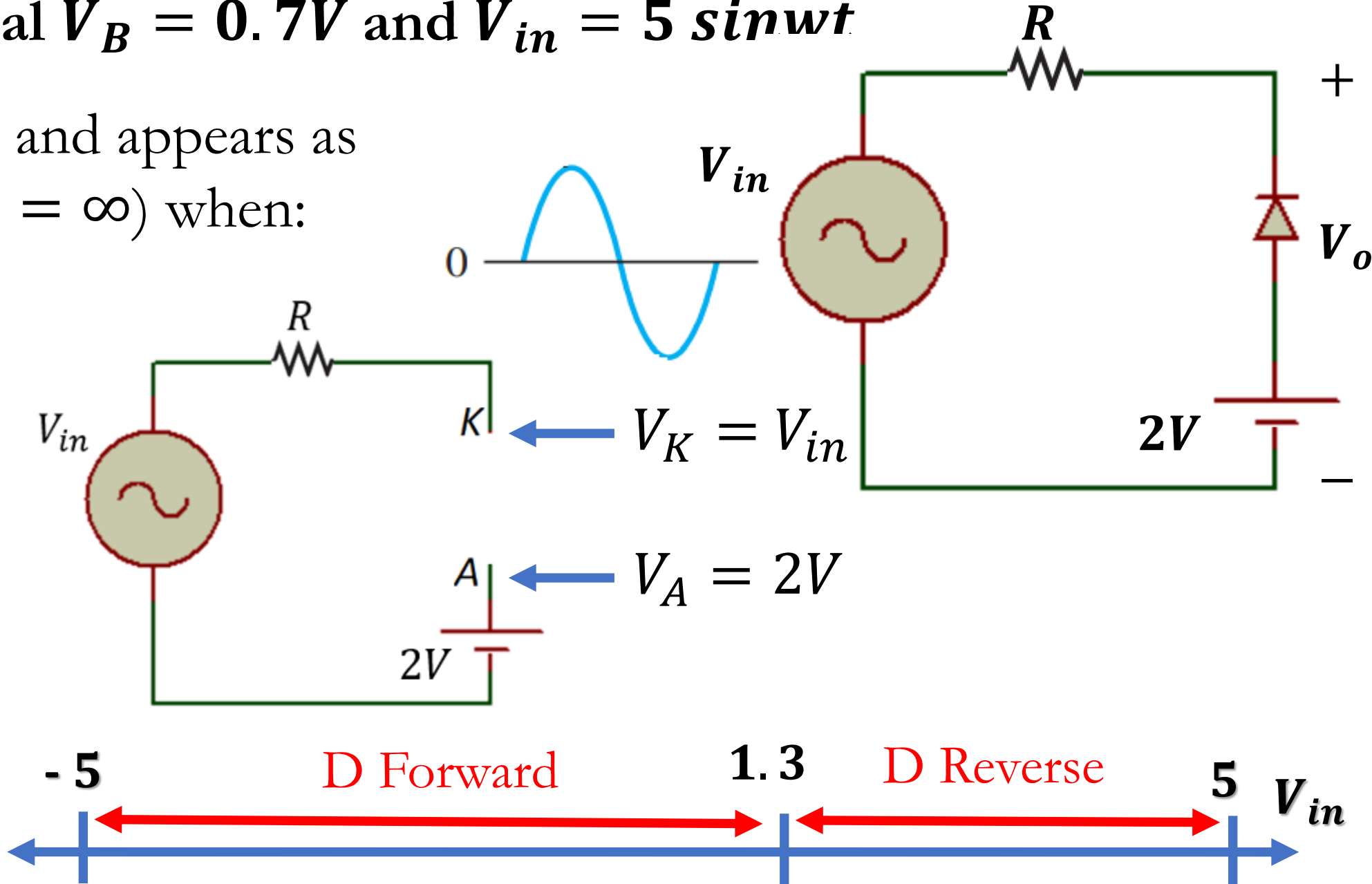

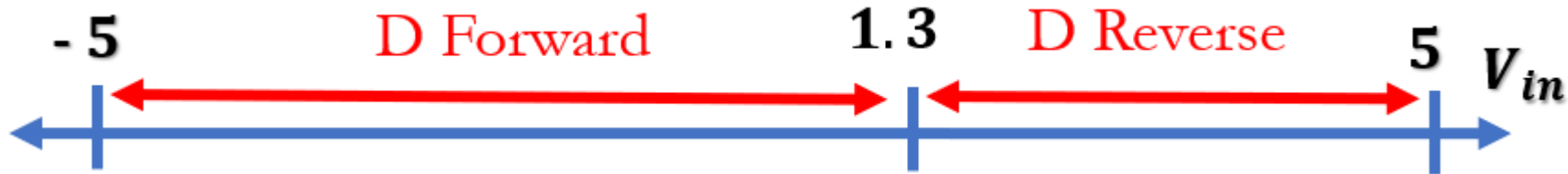

[1] $-5 \leq V_{in} \leq 1.3$

D is forward

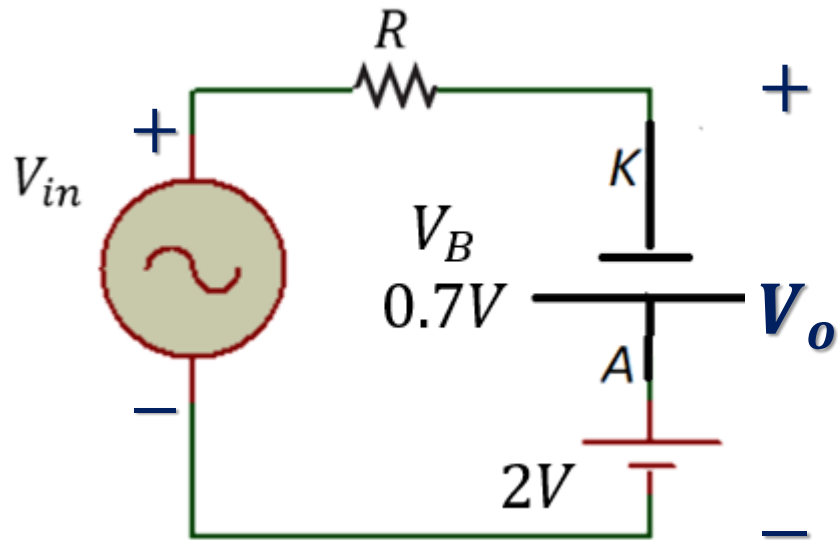


$$V_o + 0.7 - 2 = 0$$

$$V_o = 2 - 0.7 = 1.3V$$


[2] $1.3 < V_{in} \leq 5$

D is reverse

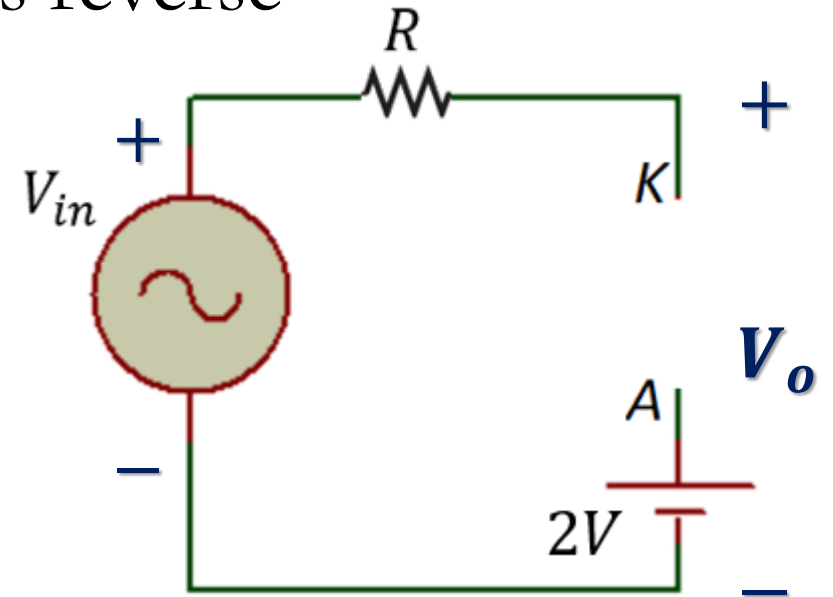


$$V_o - V_{in} = 0$$

$$V_o = V_{in}$$

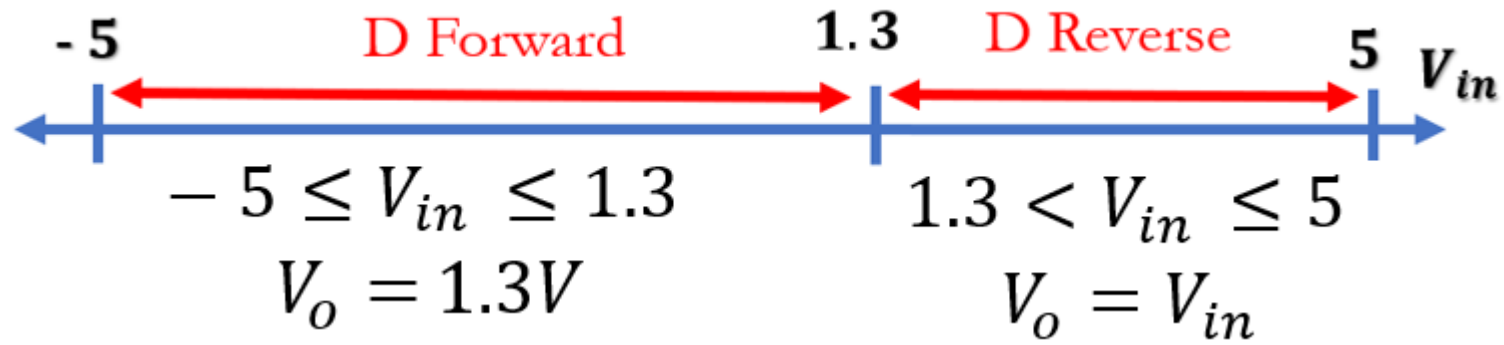


The output voltage waveform:

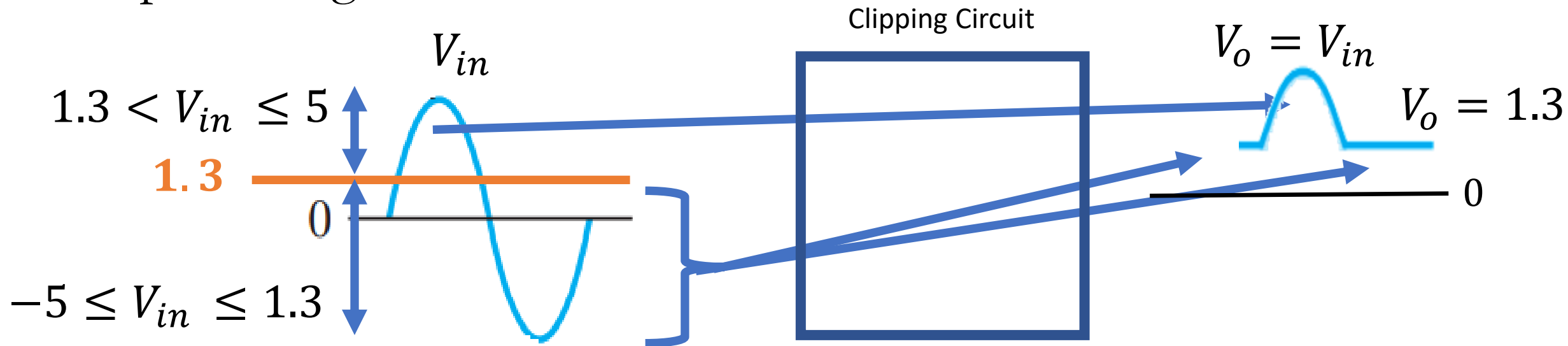

Assume practical diodes with barrier potential $V_B = 0.7V$.
 Sketch the output voltage waveform when $V_{in} = 10\sin\omega t$.


D1 is reverse and appears
 as open switch ($R_r = \infty$)
 when:

$$V_{A1} \leq V_{K1} + V_B$$

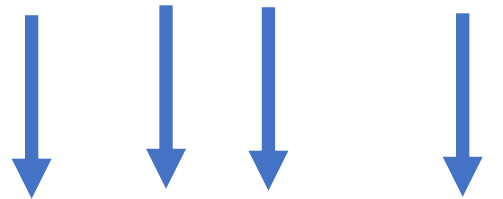

$$V_{in} \leq 5 + 0.7$$

$$V_{in} \leq 5.7$$

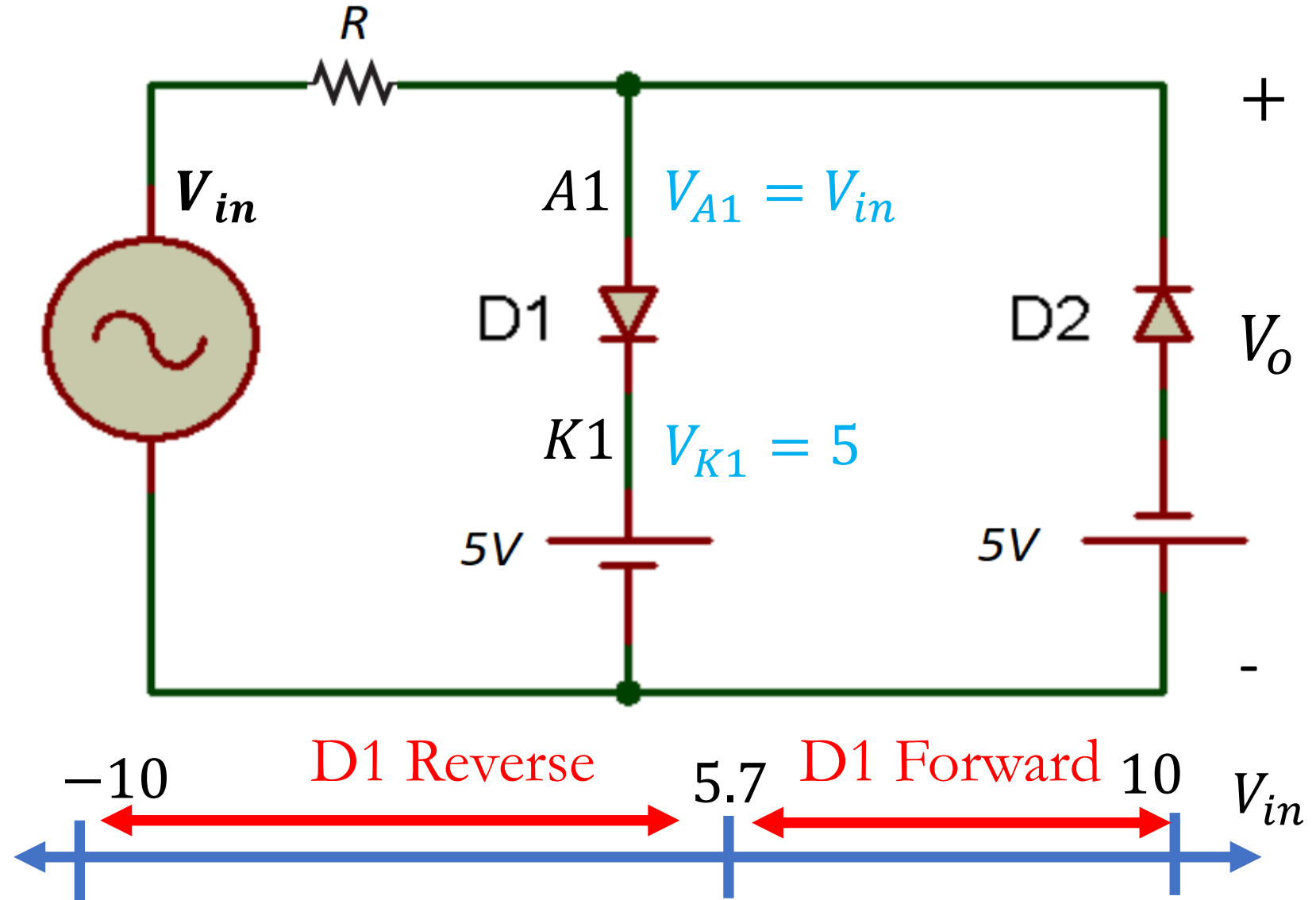

D2 is reverse and appears as open switch ($R_r = \infty$) when:



$$V_{A2} \leq V_{K2} + V_B$$


↓ ↓ ↓ ↓

$$-5 \leq V_{in} + 0.7$$

$$-5 - 0.7 \leq V_{in}$$

$$-5.7 \leq V_{in}$$

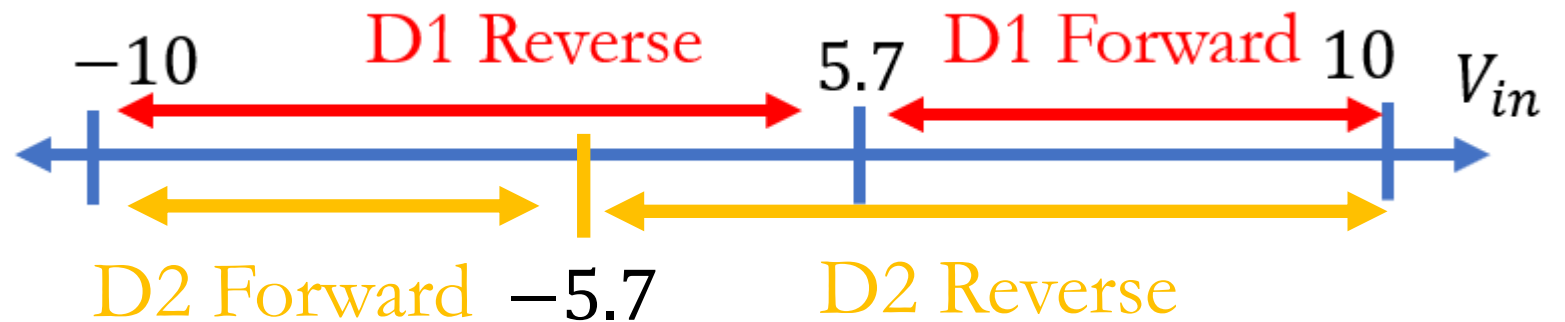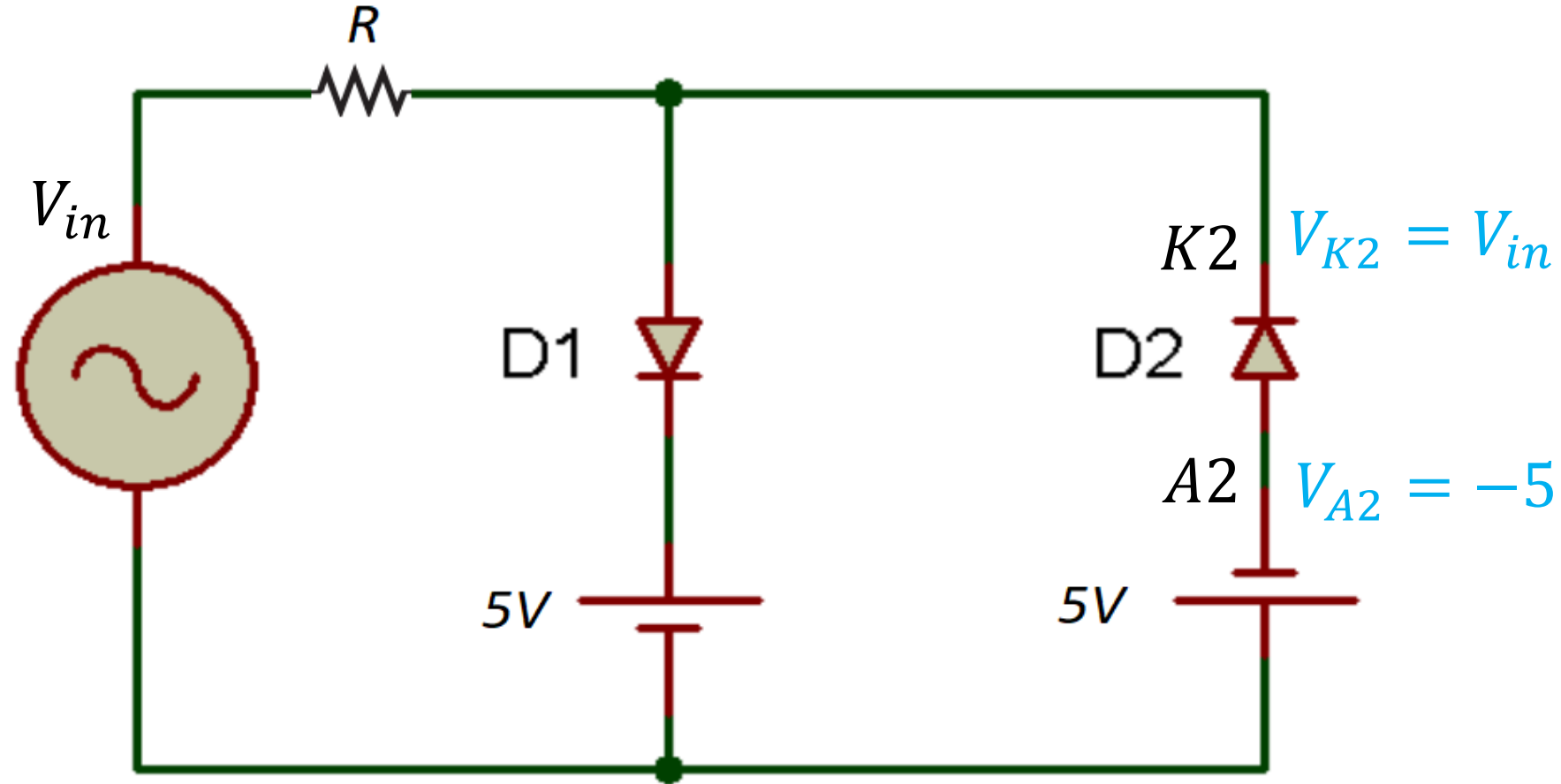

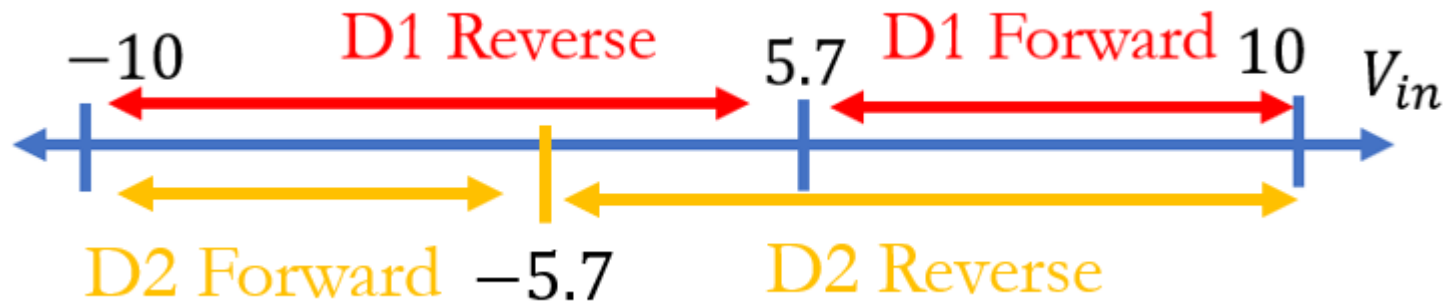


[1] $-10 \leq V_{in} < -5.7$


D1 is reverse

D2 is forward

$$V_o + 0.7 + 5 = 0$$

$$V_o = -5.7V$$

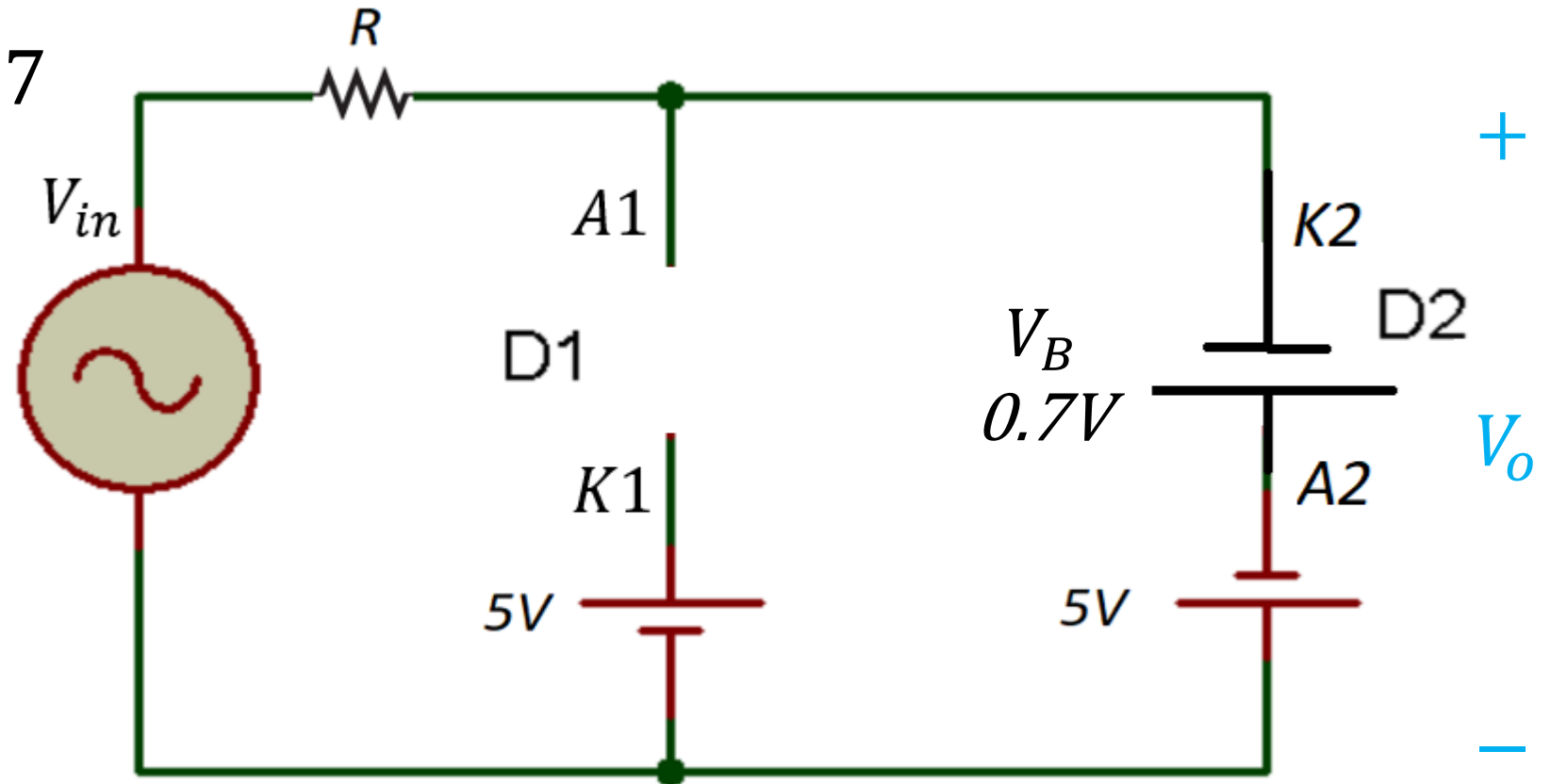

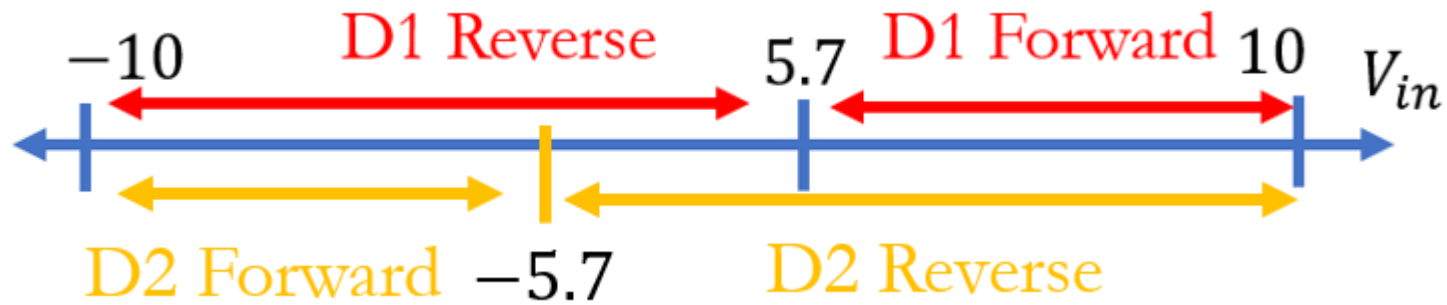


[2] $-5.7 \leq V_{in} \leq 5.7$


D1 is reverse

D2 is reverse

$$V_o - V_{in} = 0$$

$$V_o = V_{in}$$

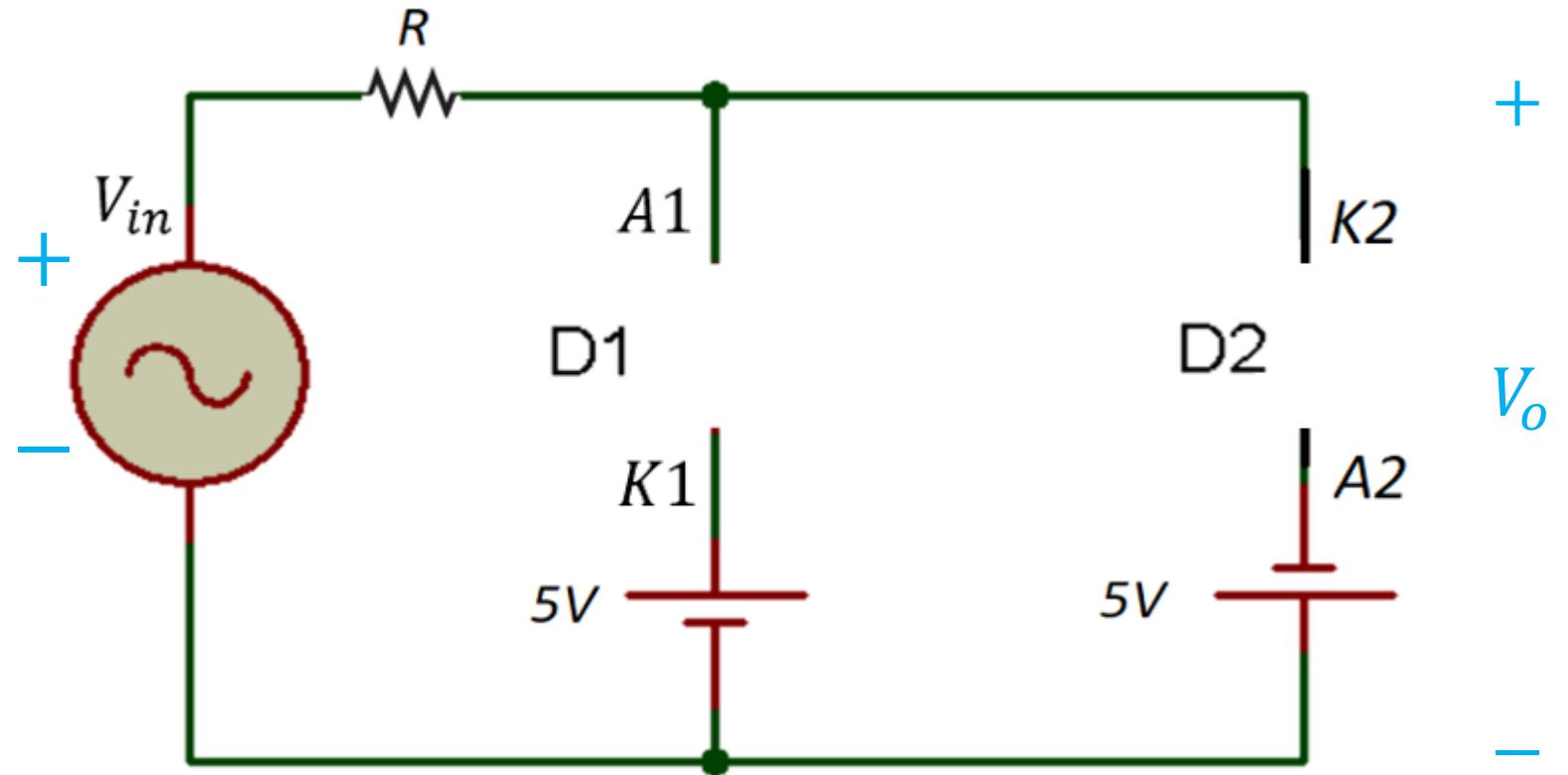

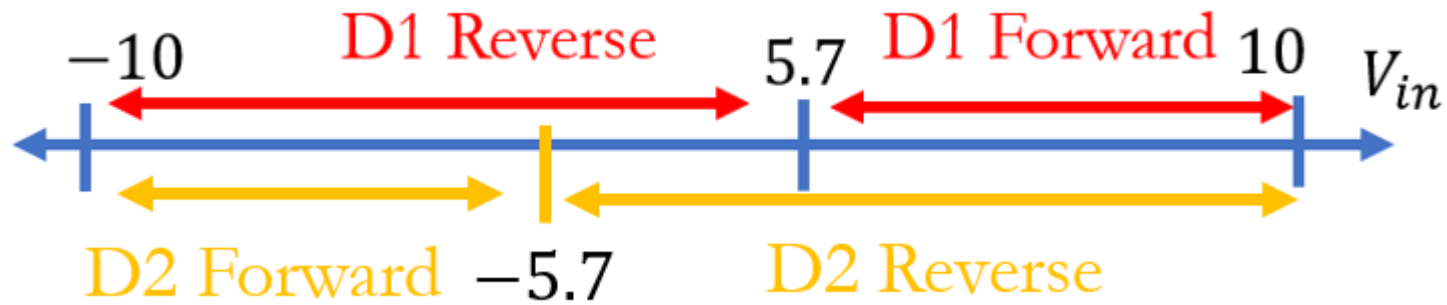


[3] $5.7 < V_{in} \leq 10$

D1 is forward


D2 is reverse

$$V_o - 0.7 - 5 = 0$$

$$V_o = 5.7V$$

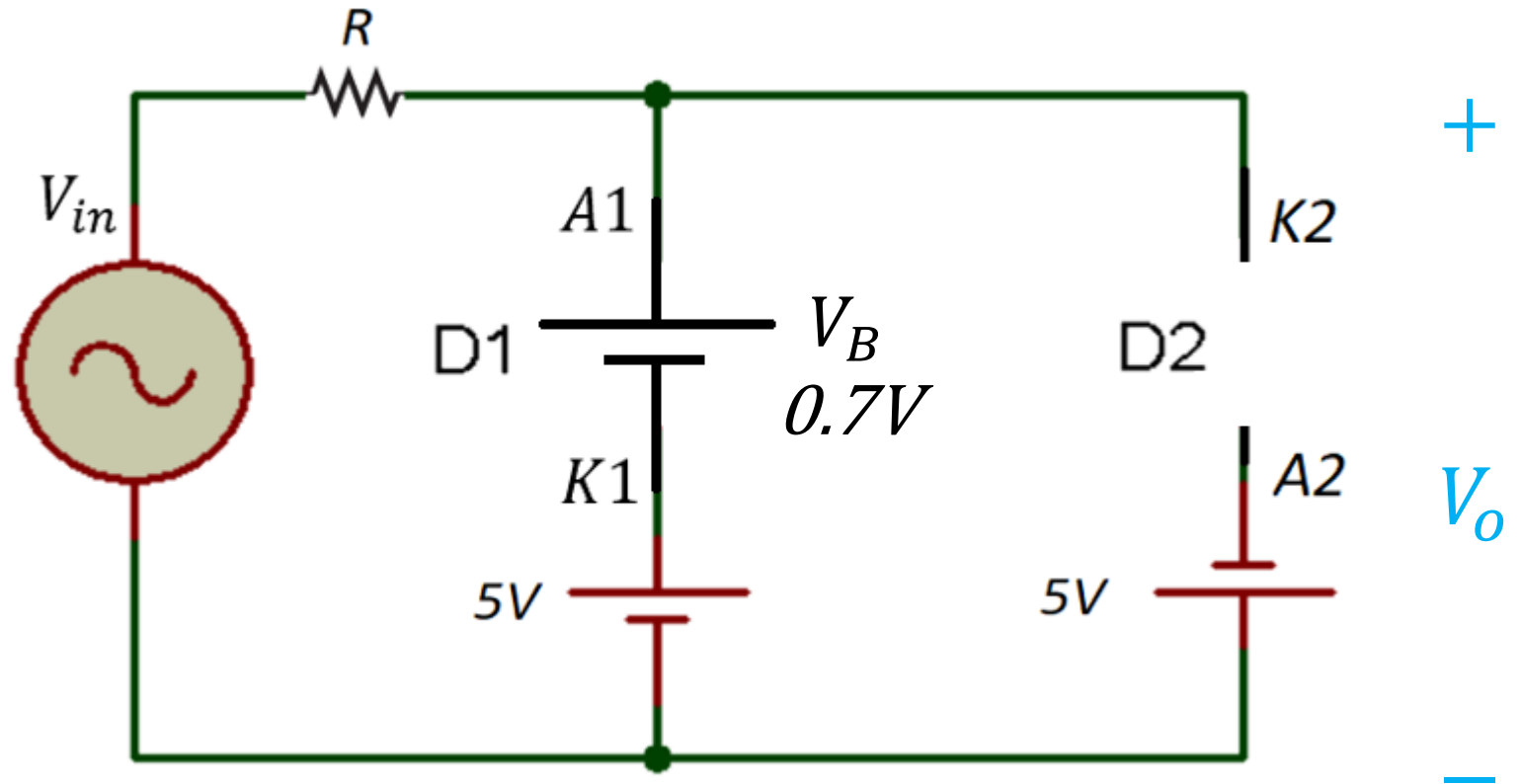

The output voltage waveform:

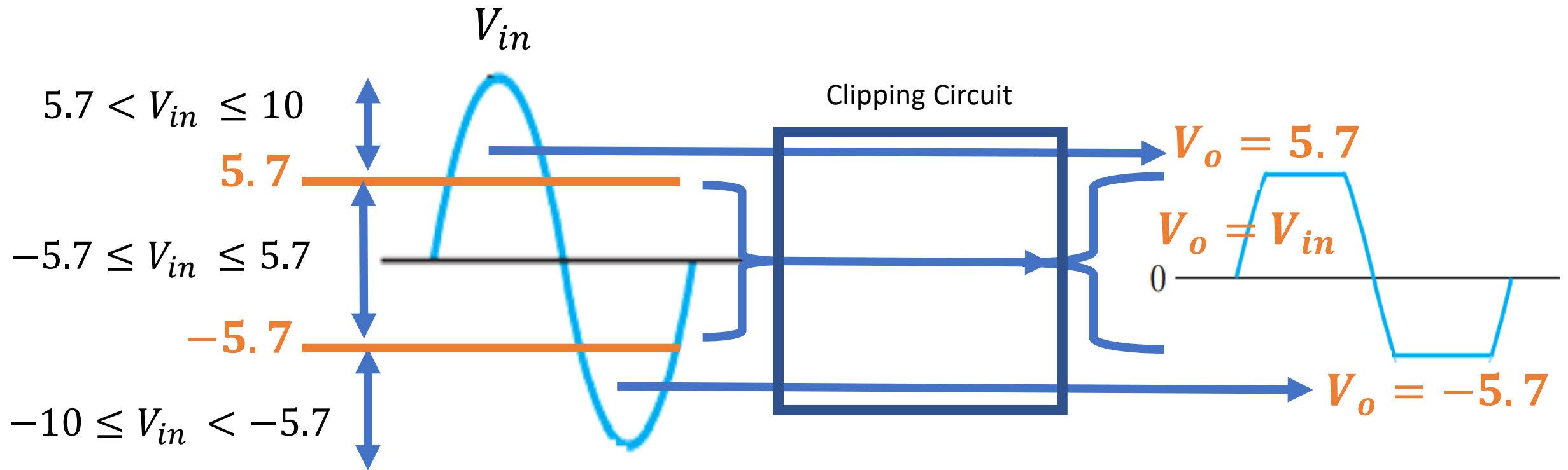


Sketch the output waveform (V_o versus time) of the circuit shown, assuming practical diode with barrier potential $V_B = 0.6V$ and $V_{in} = 10 \sin \omega t$.

D1 is reverse ($R_r = \infty$) when:

$$V_{A1} \leq V_{K1} + V_B$$


$$V_{in} \leq 2 + 0.6$$

$$V_{in} \leq 2.6$$

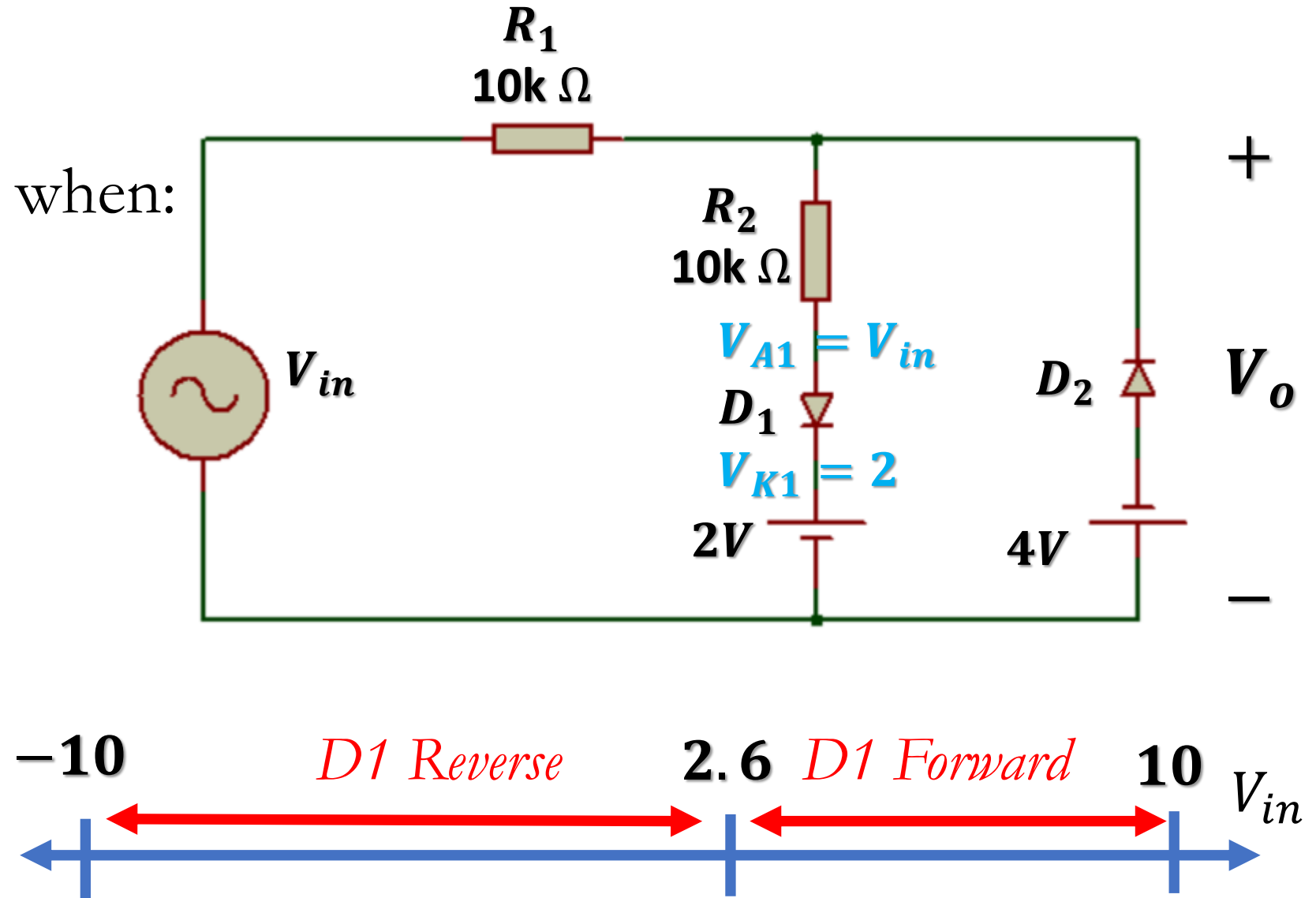

D2 is reverse ($R_r = \infty$) when:



$$V_{A2} \leq V_{K2} + V_B$$

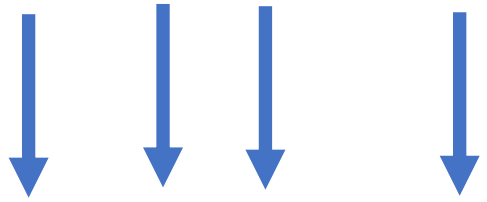

$$-4 \leq V_{in} + 0.6$$

$$-4 - 0.6 \leq V_{in}$$


$$-4.6 \leq V_{in}$$

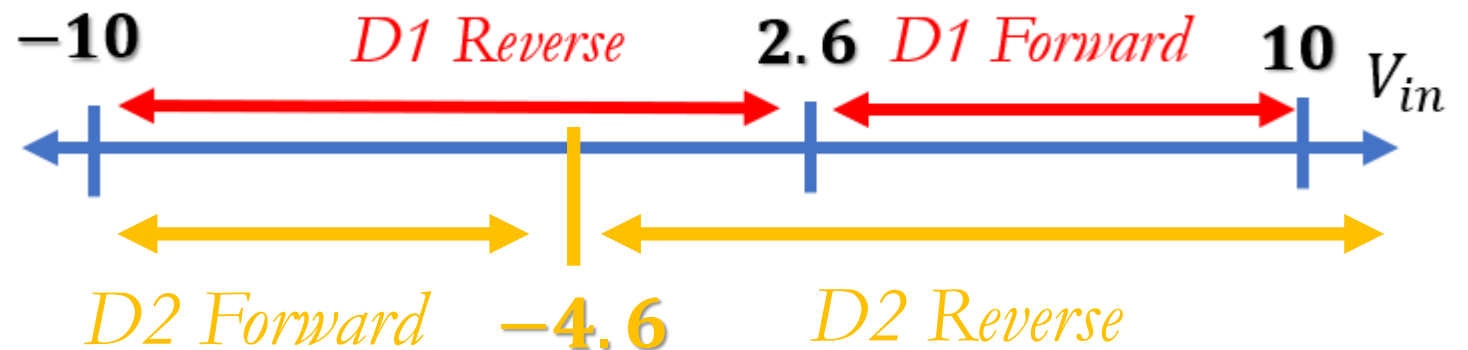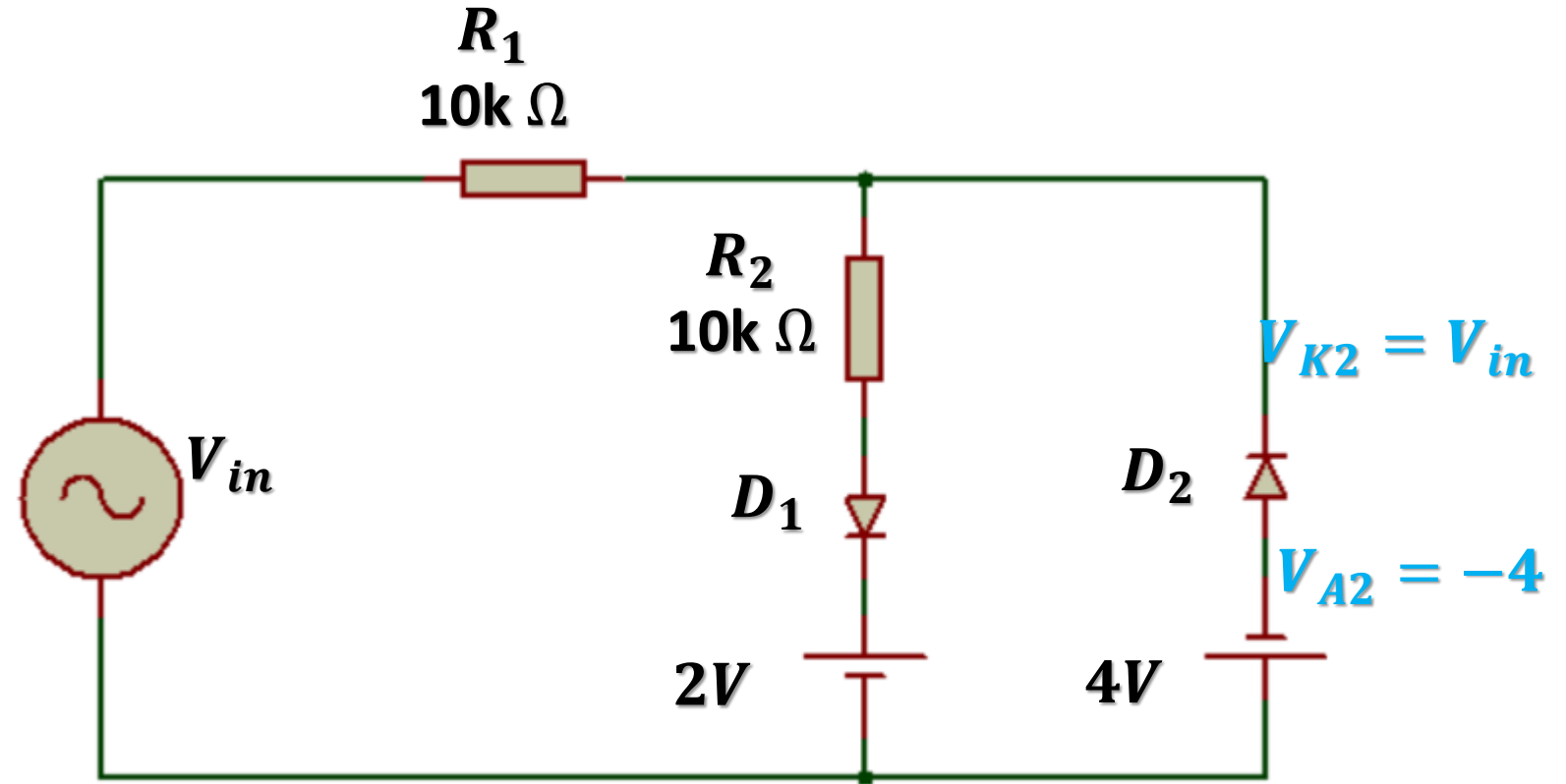

$$[1] -10 \leq V_{in} < -4.6$$


D1 is reverse

D2 is forward

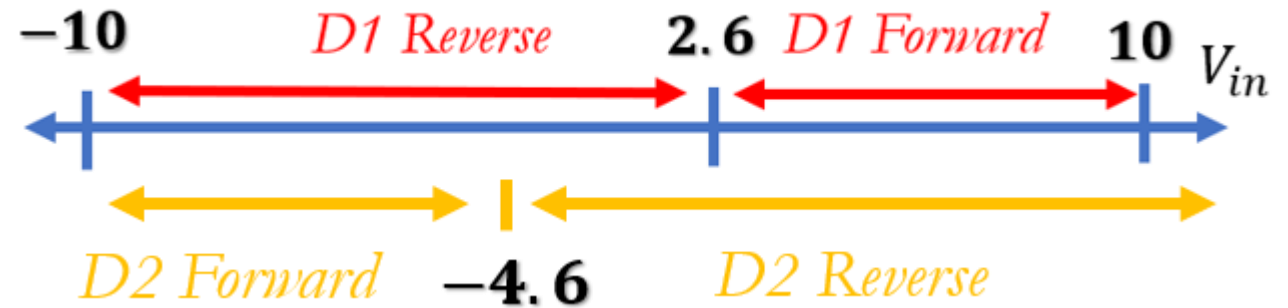

$$V_o + 0.6 + 4 = 0$$

$$V_o = -4.6$$

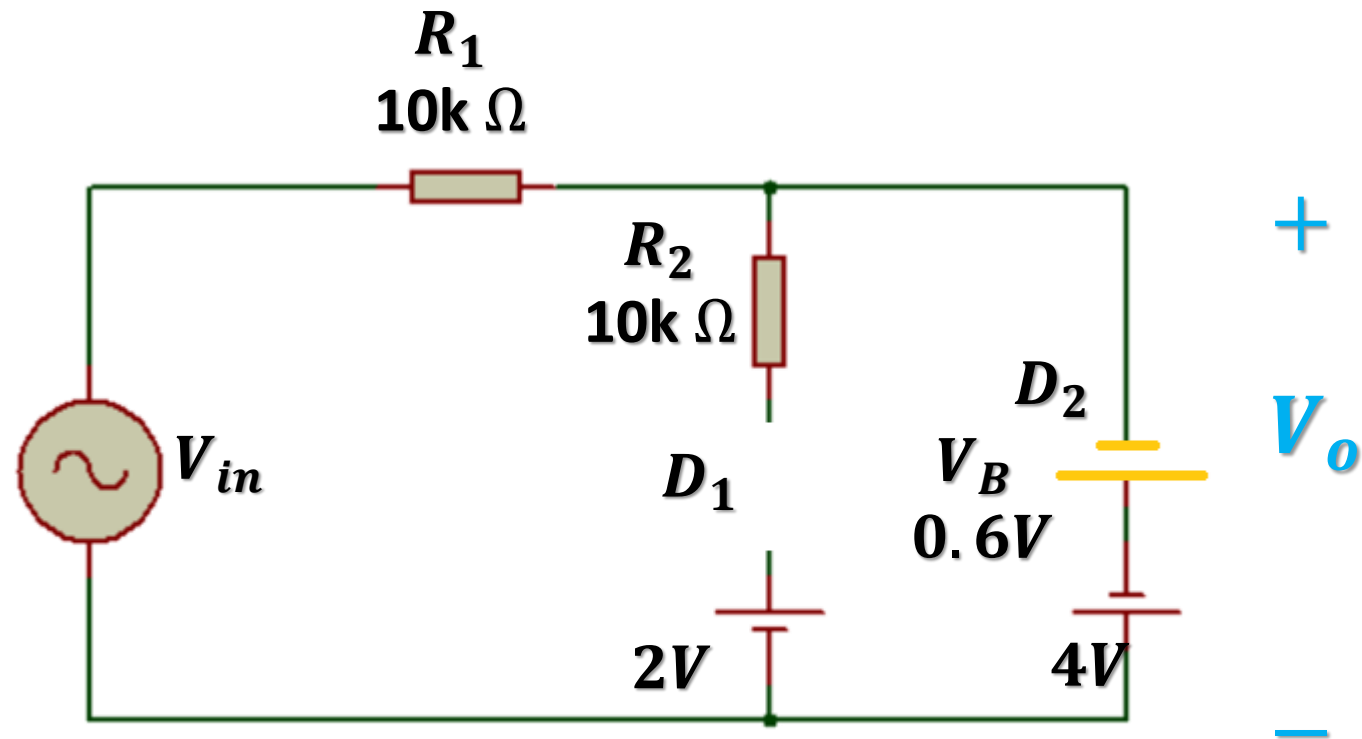



$$[2] -4.6 \leq V_{in} \leq 2.6$$

D1 is reverse

D2 is reverse

$$V_o - V_{in} = 0$$

$$V_o = V_{in}$$

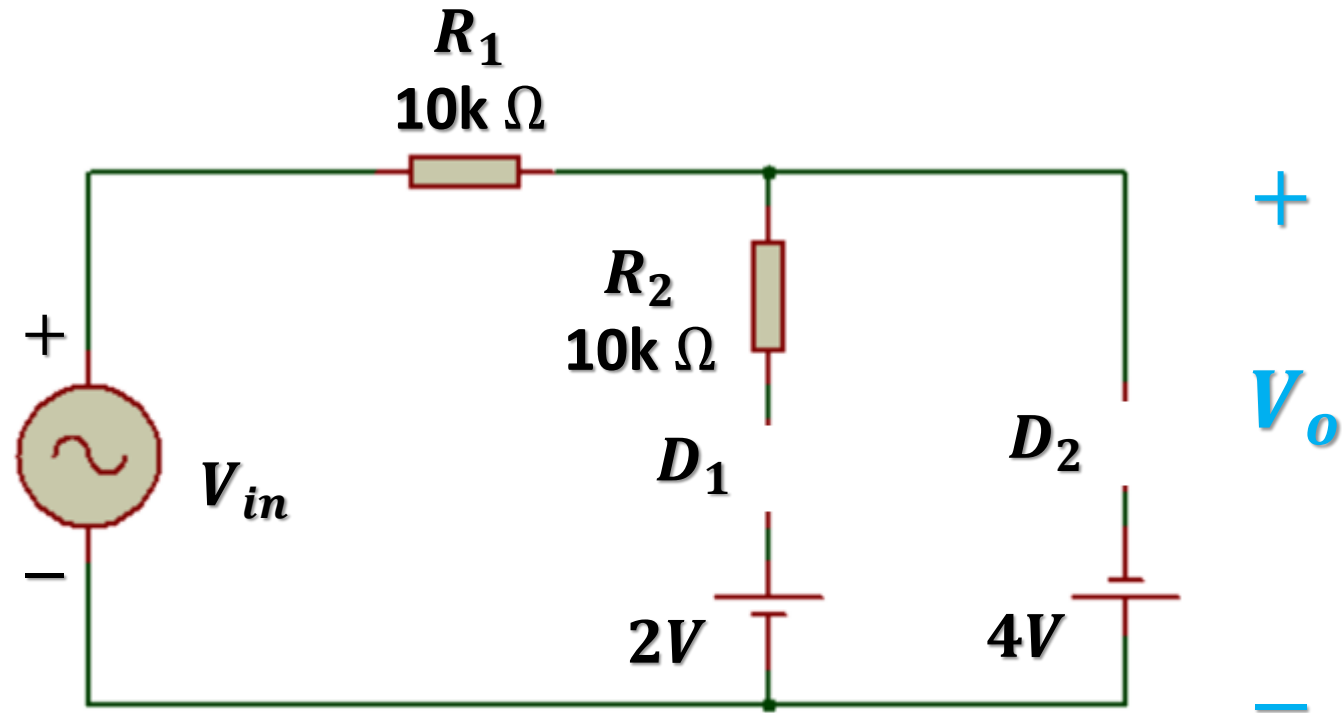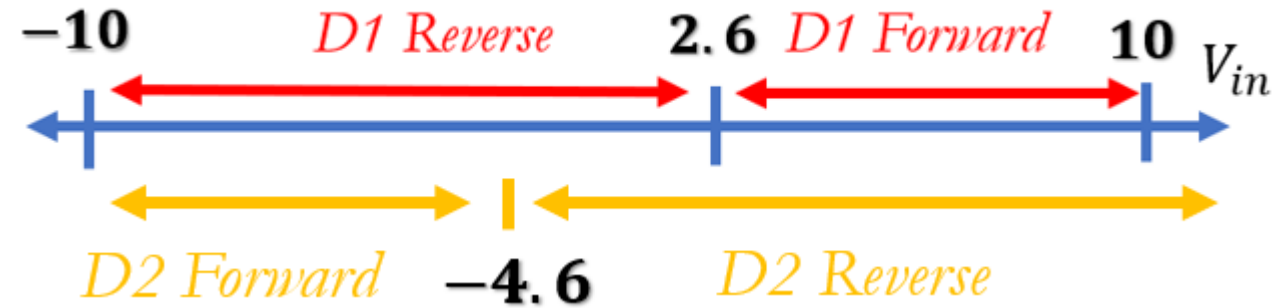

[3] $2.6 < V_{in} \leq 10$



D1 is forward

D2 is reverse

$$\sum V \text{ in closed loop} = 0$$

$$V_{in} - I_D(10k + 10k) - 0.6 - 2 = 0$$

$$\frac{V_{in} - 2.6}{20k} = I_D$$

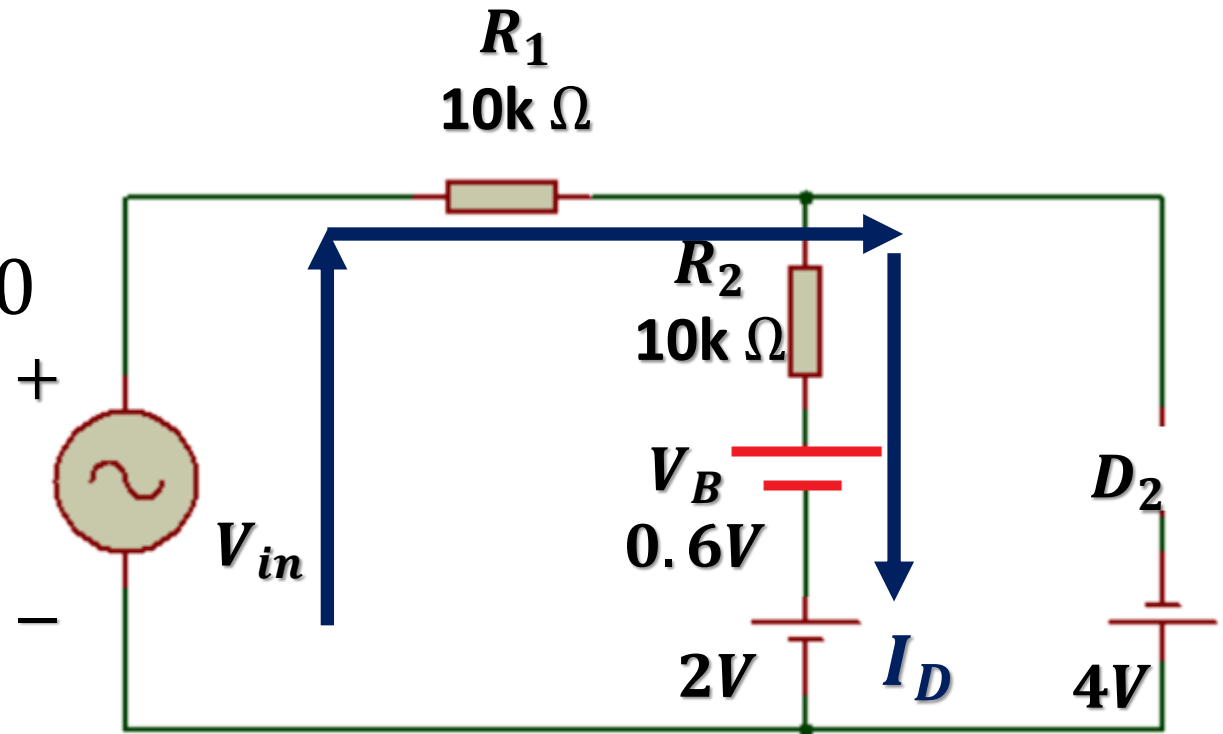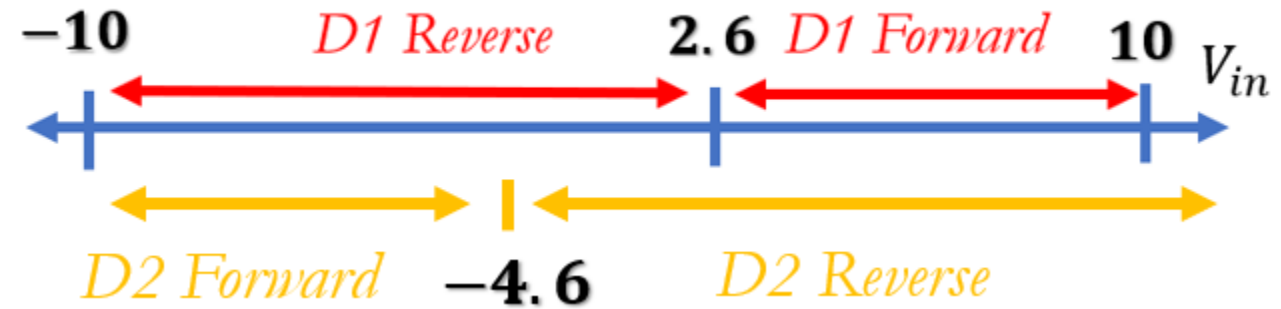

To find V_o , write KVL between V_o and **the branch** :


$$V_o - I_D(10k) - 0.6 - 2 = 0$$

$$V_o = I_D(10k) + 2.6$$

$$\therefore I_D = \frac{V_{in} - 2.6}{20k}$$

$$V_o = \left(\frac{V_{in} - 2.6}{20k} \right) (10k) + 2.6$$

$$V_o = \frac{V_{in} - 2.6}{2} + 2.6$$

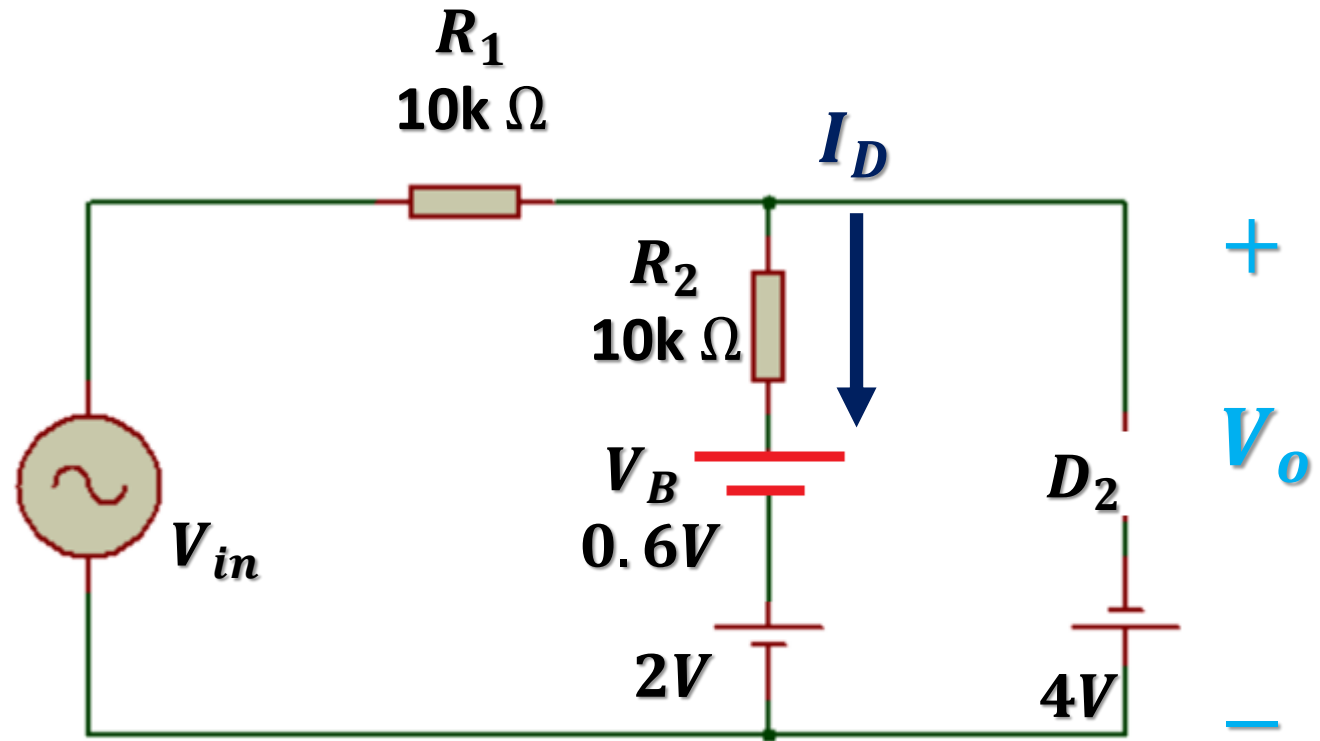

The output voltage waveform:

$$V_o = \frac{V_{in} - 2.6}{2} + 2.6$$

