

## Sheet 2: Diodes - Operation & Applications

1- Calculate the barrier potential ( $V_B$ ) at room temperature, when the resistivity of the two sides of a germanium (Ge) diode is  $2.2 \Omega\cdot\text{cm}$  (p side) and  $1.1 \Omega\cdot\text{cm}$  (n side). Repeat for a silicon (Si) diode.

$$n_i(\text{Si}) = 1.5 \times 10^{10} \text{ atoms/cm}^3$$

$$n_i(\text{Ge}) = 2.5 \times 10^{13} \text{ atoms/cm}^3$$

2- If the reverse saturation current in a silicon diode is  $1\text{nA}$ , what is the current passing through a diode when the voltage across the diode is  $0.8\text{V}$  at room temperature.

3- In the circuit shown in Figure 1, the diode D1 is germanium with a potential barrier ( $V_{B1}$ )  $0.3\text{V}$  and an incremental resistance ( $R_{f1}$ )  $25\Omega$  whereas the diode D2 is silicon with a potential barrier ( $V_{B2}$ )  $0.7\text{V}$  and an incremental resistance ( $R_{f2}$ )  $15\Omega$ . Calculate the diodes currents.

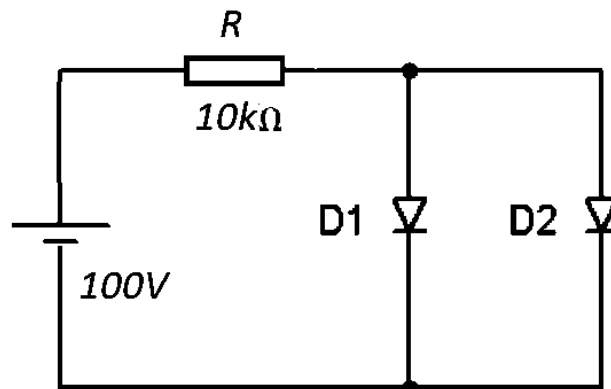


Figure 1

4- For the circuit shown in Figure 2, assume identical diodes with a barrier potential ( $V_B$ ) of  $0.6\text{V}$ . Calculate output voltage ( $V_o$ ) for the following input voltages:

(a)  $V_1 = 0\text{V}$  and  $V_2 = 0\text{V}$ .

(b)  $V_1 = 10\text{V}$  and  $V_2 = 0\text{V}$ .

(c)  $V_1 = 0\text{V}$  and  $V_2 = 10\text{V}$ .

(d)  $V_1 = 10\text{V}$  and  $V_2 = 10\text{V}$ .

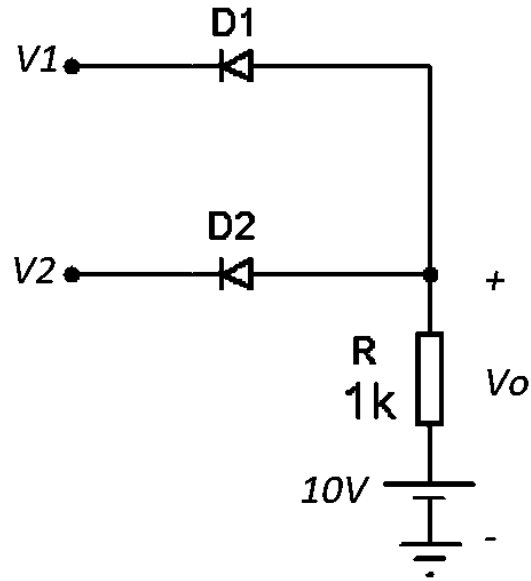


Figure 2

5- Sketch the output waveform ( $V_o$  versus time) of the circuit shown in Figure 3, assuming the diode with a barrier potential ( $V_B$ ) of 0.6V and  $V_{in} = 5 \sin \omega t$ .

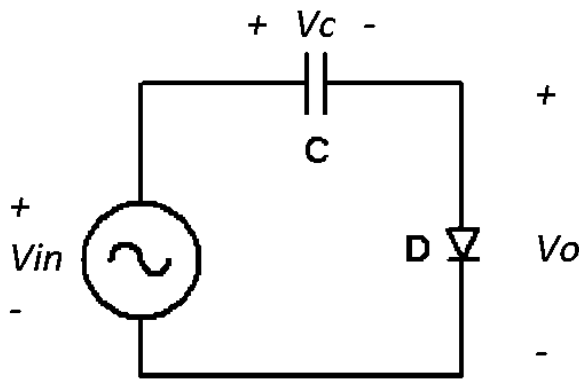


Figure 3(a)

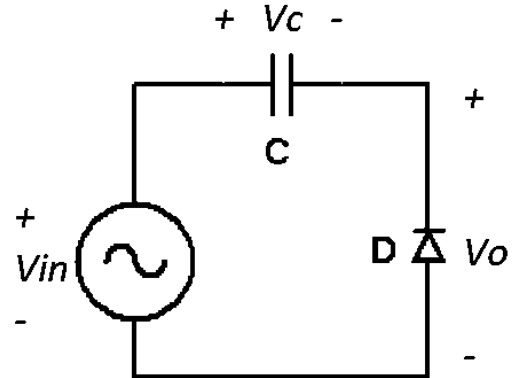


Figure 3(b)

6- Sketch the output waveform ( $V_o$  versus time) of the circuit shown in Figure 4, assuming ideal diodes and  $V_{in} = 20 \sin \omega t$ .

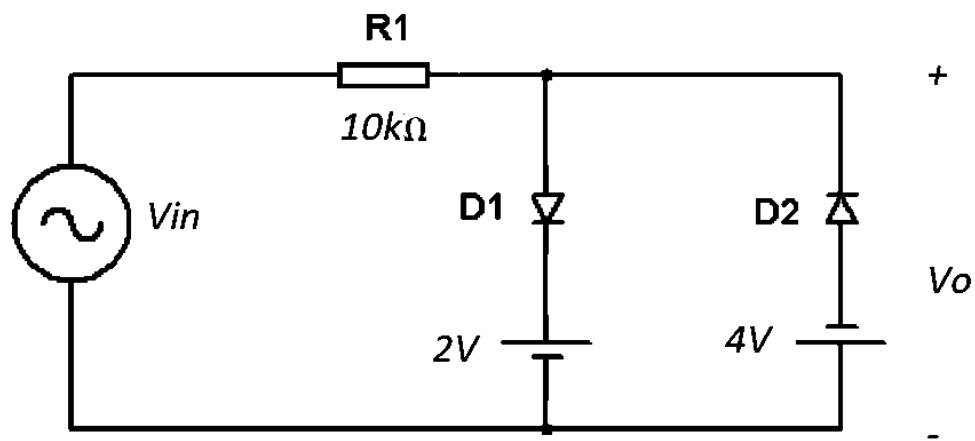


Figure 4(a)

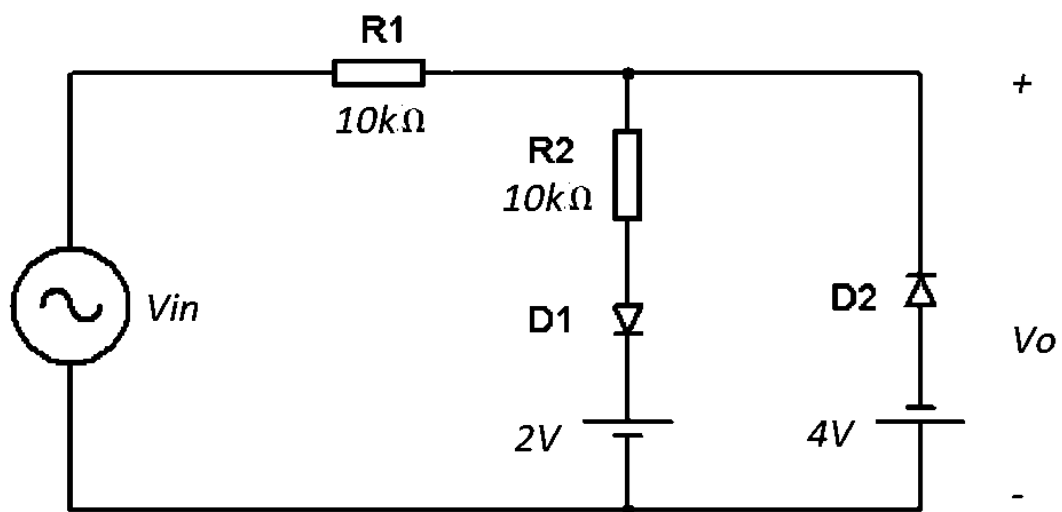


Figure 4(b)

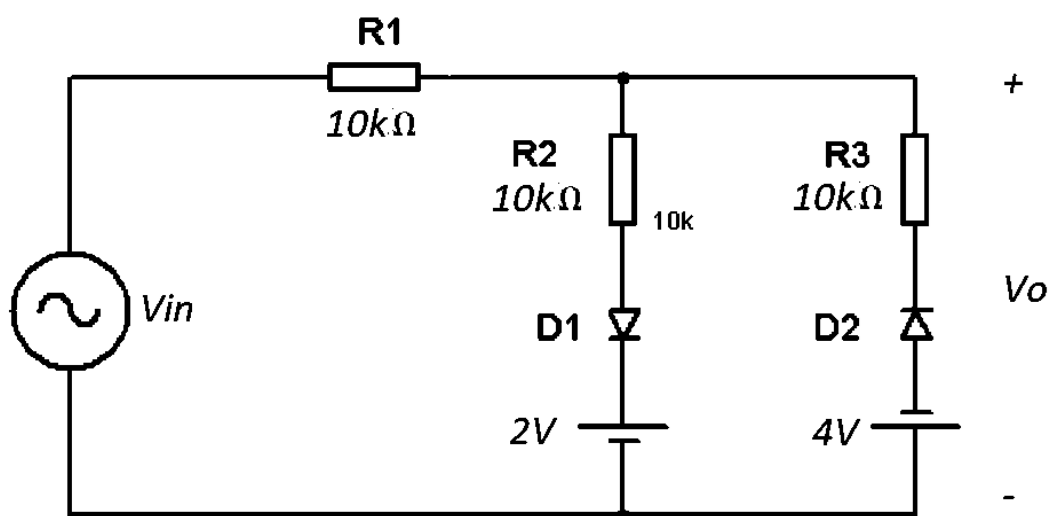


Figure 4(c)

7- (I) For the zener diode network of Figure 5, determine:

- (a) The output voltage ( $V_o$ ) across  $R_L$ .
  - (b) The voltage ( $V_R$ ) across  $R$ .
  - (c) The current through the zener diode ( $I_Z$ ).
  - (d) The zener power ( $P_Z$ ).
- (II) Repeat part (I) with  $R_L = 4k\Omega$ .

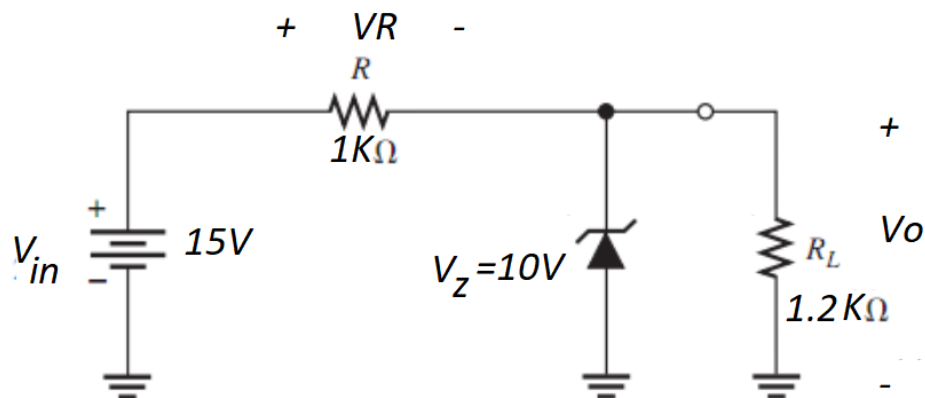


Figure 5

8- Determine the range of values of the input voltage ( $V_{in}$ ) that will maintain zener diode in Figure 6 in the regulation state.

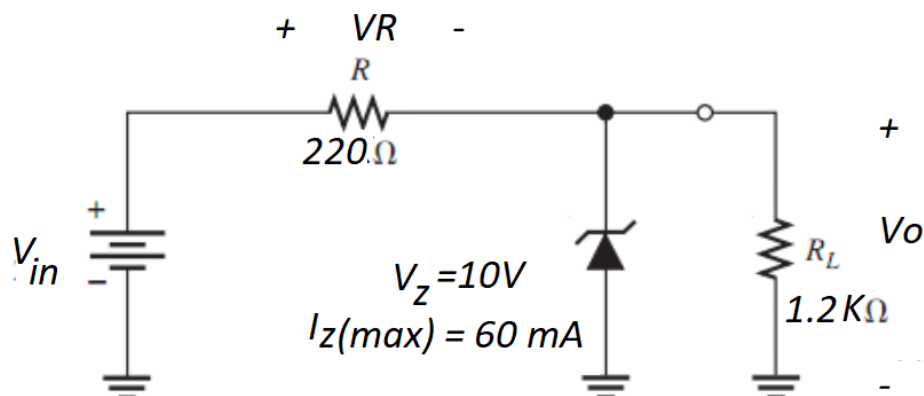


Figure 6