

CHAPTER 1: SEMICONDUCTOR BASICS.

## \* Materials:-

→ Conductors :- Copper, Aluminum, Gold, Silver, --

→ Semiconductors :- Silicon, Germanium, Gallium Arsenide, <sup>Indium-Gallium-Arsenide</sup>, --

→ Non-conductors - Insulators :- Paper, rubber, wood, plastic, Glass, --

## \* Notes:-

\* Gallium-Arsenide :-  $Gal + As$  "جالیم + آرسنید"\* Indium-Gallium-Arsenide :-  $Ind + Gal + As$  "اندیم + غالیم + آرسنید"

→ Semiconductors :- materials whose electrical properties between insulators &amp; conductors.

→ Conductivity :- "Siemen per meter" :- a physical property of materials that represents the ability of a material to conduct electricity through it.

$$\bullet \text{Siemen} = \frac{1}{\text{Ohm} \cdot \text{SL}}$$

\* Semiconductors are in the form of devices or Integrated Circuits "ICs".


\* Semiconductors are important because the most used semiconductor "Silicon" is extracted from desert sand "SiO<sub>2</sub>" "Cheaper".

- \* Semiconductors are insulators at low temperatures and conductors at high temperatures.
  - \* Electrical properties of semiconductors can be changed by introducing external atoms, "impurities" شوائب.
  - \* Silicon, Germanium are common semiconductors in the fourth group of the Periodic table.  $Si_{14}$  -  $Ge_{32}$
  - \* Four valence "four كي" electrons in the outer "valence" shell "four كي" in the Silicon, Germanium.
  - \* The farther you get from the nucleus the higher energy ~~level~~ you get.
  - \* You must remember:-
    - Number of Si atoms per  $cm^3$  equals  $5 \times 10^{22}$  atoms.
    - Number of Ge atoms per  $cm^3$  equals  $4.4 \times 10^{22}$  atoms.

\* Semiconductor crystal:- made up of atoms bonded together in a regular structure.

\* semiconductor atom has 4 valence electrons which are shared, forming covalent bonds with four atoms. "روابط سلسلية"

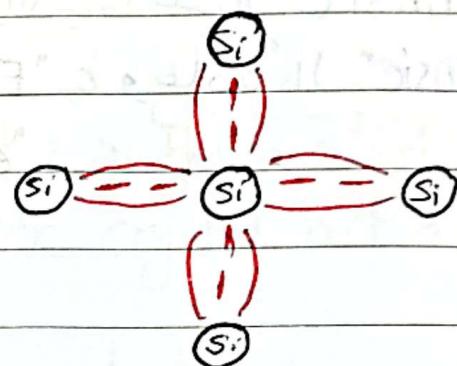\* This creates eight shared valence electrons for each atom and produces a state of chemical stability.



يتكون بلورات أشباه الموصلات من ذرات هيكلة سلسلية  
البعض من ضمنها ذرات أشباه الموصلات  
على كل ذرات تكاملية، فتقوم روابط سلسلية هو كل ذرعة  
ذرات مما يكون لها روابط سلسلية بذرات التكاملية  
ويستبع حالة عدم الاستقرار (الميئي) لأن المستوى الآخر  
ستقع بوجود ذرات التكاملية.

- \* Intrinsic Semiconductors crystals contains only Si or Ge atoms only.
- \* Extrinsic semiconductors crystals contains Si or Ge atoms plus impurities.

\*  
اللي فيه ذرات منه نفس النوع بدون شوائب هي الـ "Intrinsic"  
\*  
اللي فيها شوائب هي الـ "Extrinsic" أو عادةً ما  
يبيت فيها "extra electron" أو "hole".

- \*  
Intrinsic semiconductors crystals contains only Si or Ge atoms only.
- \*  
Extrinsic semiconductors crystals contains Si or Ge atoms plus impurities.

## Intrinsic Semiconductors :- "Pure"

- \* contains only Si or Ge atoms only "No impurities".
- \* at temperature OK, the Valence band "نطاق الكثافة" is fully occupied by the valence electrons, and the conduction band is completely empty of electrons.   
 "نطاق كثافة電子 بلا نكثة بكترونات الكثافة"   
 "نطاق كثافة كهربائية بلا نكثة بكترونات الكثافة"
- \* Because of no electrons are available in the conduction band the Intrinsic semiconductor crystal act as a insulator at OK.

\* Conductivity of Intrinsic semiconductor = zero at OK.

$$\sigma = 0 \text{ at } 0K \text{ or } -273C$$

\* as temperature increase above OK, a few valence electrons gain enough thermal energy  $\text{أو الحرارة}$  to break the bond and jump into the conduction band, leaving a hole behind them.

\* as temperature increases further more bonds break, and more electrons jump to the conduction band, and more holes "empty states" are created in the valence band.

\* number of free electrons in the conduction band equals the number of holes left in the valence band.

•  $n$   $\rightarrow$  free electrons concentration

•  $p$   $\rightarrow$  hole concentration

•  $n_i$   $\rightarrow$  intrinsic concentration, semiconductor atoms affected by temperature.

\* in room temperature  $300K = 27C$  :-

$$\bullet n_i(\text{Si}) = 1.5 \times 10^{10} = n = P \quad * n_i = \sqrt{NP}$$

$$\bullet n_i(\text{Ge}) = 9.5 \times 10^{13} = n = P$$

\* Conductivity of intrinsic semiconductor at  $300K = 27C$  :-

$$\bullet \sigma = q(nM_n + P\mu_p)$$

$$\bullet \sigma = qn_i(M_n + \mu_p)$$

\* where :-

\*  $q \Rightarrow$  electron charge  $= 1.6 \times 10^{-19}$

\*  $n \Rightarrow$  Free electron concentration.

\*  $P \Rightarrow$  Hole concentration

\*  $\sigma \Rightarrow$  Electrical conductivity.

\*  $n_i \Rightarrow$  Intrinsic concentration.

\*  $M_n \Rightarrow$  Electron mobility.

\*  $\mu_p \Rightarrow$  Hole mobility.

\* Current density ( $J$ ) = Conductivity ( $\sigma$ )  $\times$  Electric field ( $E$ )

\*  $E = \frac{V}{L}$   $V \Rightarrow$  voltage.  $L \Rightarrow$  distance between two points.

$$\bullet J = \sigma \cdot E = \sigma \cdot \frac{V}{L} = \frac{q n_i (M_n + \mu_p) \cdot V}{L}$$

at  $300K$

\* at  $0K$  :-  $J = 0, \sigma = 0$

## ★ Extrinsic Semiconductors :-

⇒ Crystals contain Si or Ge plus impurities.

## Impurities

Pentavalent atoms ("N<sub>D</sub>")

"نحاس پانچ" "D"

"atoms with 5 valence electrons like:-"

arsenic (As), 33

phosphorus (P), 15

antimony (Sb) 51

Trivalent atoms ("N<sub>A</sub>)

"نحاس تریا" "A"

"atoms with 3 valence electrons like:-"


boron (B), 5

indium (In), 49

Gallium (Ga) 31
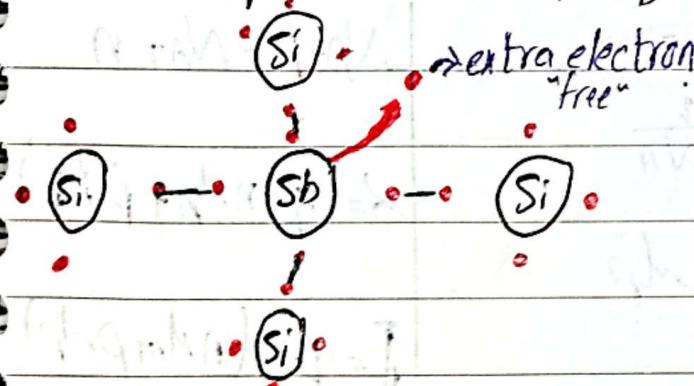
## Extrinsic Semiconductors

Si or Ge + Pentavalent atoms "N<sub>D</sub>"




\* electrons are majority carriers.

\* holes are minority carriers.

n-type Semiconductor

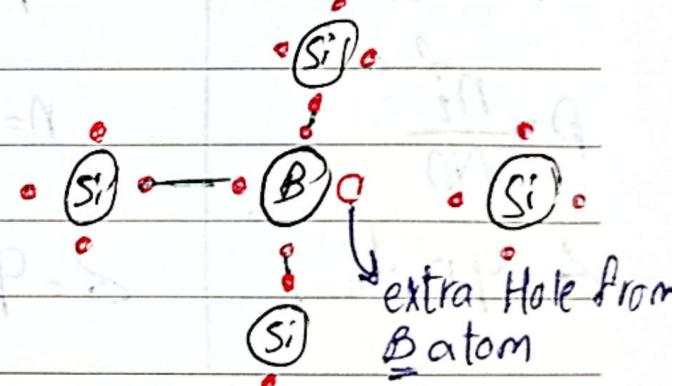Si or Ge + Trivalent atoms "N<sub>A</sub>"



\* holes are majority carriers.

\* electrons are minority carriers.

p-type Semiconductor

$$n_i^2 = N \times P$$

## Extrinsic semiconductors

N-type Semiconductors

$$n = N_D, P = \frac{N_D}{N_D + N_A}$$

$$\delta = q n \mu_n = q N_D \mu_n$$

$$J = q n \mu_n E = q N_D \mu_n E$$

$N_D \rightarrow$  Donors (Almond)

$$n_i^2 = n P$$

$$\delta = q n_i (N_D + N_A)$$

P-type Semiconductors

$$P = N_A, n = \frac{N_A}{N_D + N_A}$$

$$\delta = q P \mu_p = q N_A \mu_p$$

$$J = q P \mu_p E = q N_A \mu_p E$$

## Extrinsic semiconductors

N-type Si or Ge  
+  $N_D$

$$n = N_D$$

$$P = \frac{n_i^2}{N_D}$$

$$\delta = q n \mu_n$$

$$J = q n \mu_n E$$

P-type Si or Ge  
+  $N_A$

$$P = N_A$$

$$n = \frac{n_i^2}{N_A}$$

$$\delta = q P \mu_p$$

$$J = q P \mu_p E$$

Si or Ge +  $N_A + N_D$

$$n \cdot P = n_i^2$$

$$N_D + P = N_A + n$$

$$\delta = q (n \mu_n + P \mu_p)$$

$$J = q \cdot E (n \mu_n + P \mu_p)$$

$$\sigma = q(n\mu_n + p\mu_p)$$

- $\sigma \Rightarrow$  Conductivity
- $q \Rightarrow$  electron charge  $= 1.6 \times 10^{-19}$
- $n \Rightarrow$  free electrons concentration
- $\mu \Rightarrow$  Holes concentration
- $\mu_n \Rightarrow$  Electron mobility
- $\mu_p \Rightarrow$  Hole mobility

$$J = \sigma \cdot E = q(n\mu_n + p\mu_p) \cdot E \quad \begin{matrix} \rightarrow \text{Voltage} \\ \rightarrow E \end{matrix}$$

- $J \Rightarrow$  Current density
- $E \Rightarrow$  Electric field  $= \frac{V}{L}$
- $\rightarrow$  distance

$$n_i^2 = n \cdot p$$

- $n_i \Rightarrow$  free electrons concentration

\* Carrier concentration in doped semiconductors :-

\* for N-type :-

$$n = N_D \quad , \quad p = \frac{n_i^2}{N_D} \quad \begin{matrix} \bullet N_D \Rightarrow \text{Donor atom} \\ \text{concentration.} \end{matrix}$$

\* for P-type :-

$$p = N_A \quad , \quad n = \frac{n_i^2}{N_A} \quad \begin{matrix} \bullet N_A \Rightarrow \text{Acceptor atom} \\ \text{concentration.} \end{matrix}$$

$$\rho = \frac{1}{\sigma} = \frac{1}{q(n\mu_n + p\mu_p)}$$

$$V_d = \mu_n \cdot E$$

\*  $\rho \Rightarrow$  resistivity

•  $V_d \Rightarrow$  drift velocity

$$\rho + N_D = n + N_A$$

Remember the quadratic formula:-

If  $ax^2 + bx + c = 0$  then :-

$$x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

\*Important Note:-

\* لو العزم ضروري الأنس يتم ذلك مع  $N_D, N_A$  حيث معهم يستخدم الصنفون دهون

$$P + N_D = N + N_A$$

ولو أكير مس أو يسوي الـ 2 نتقايرم الـ  $N_D, N_A$  حيث  
يفرق المدى أكير ونغيرت هي  $P$ -type و  $n$ -type و بعده  
ستتم العناية المذايب سواء الـ  $N_D$  أو الـ  $N_A$


\* الـ  $N_D$  يعتمد على  $resistivity$  فله  $resistivity$  على  $resistivity$   $\rightarrow$  الـ  $N_D$  من أول وجديد

$$N_D = \frac{1}{q \cdot f (N_n + N_p)}$$

$$J = \frac{I}{A} = \sigma \cdot E = q_n \mu_n E = q_n v_d = q_n \mu_n \frac{V}{L} = q_n \mu_n \frac{I}{L} + R$$

If a piece of intrinsic semiconductor is doped with acceptors on one side and with donors on the other side, a boundary called pn junction is formed between the resulting p region and n region and a diode is created.

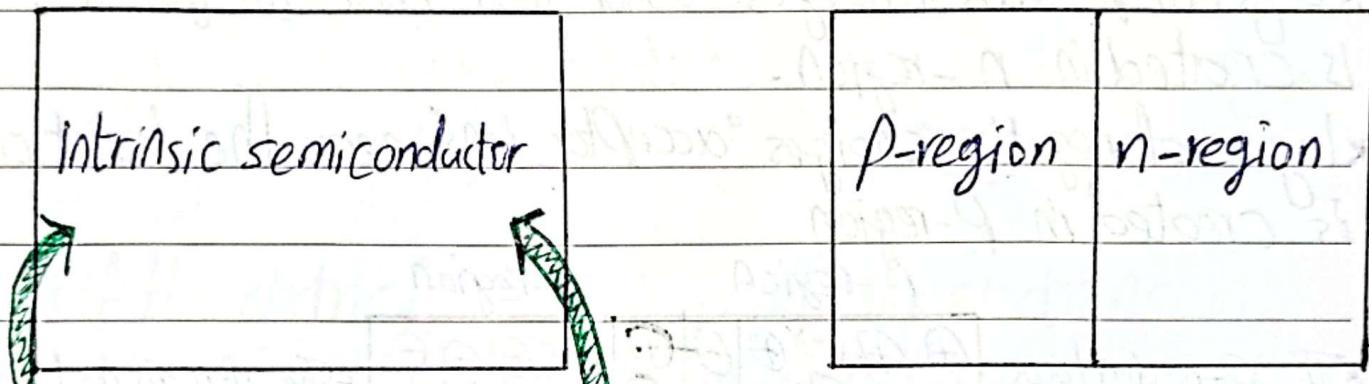Diode: a piece of an intrinsic semiconductor doped from one side with acceptors "p-type" and donors from the other side "n-type".



\* the p-region has many holes "majority carriers" from acceptor atoms and only a few thermally generated electrons "minority carriers".


\* the n-region has many electrons "majority carriers" from donor atoms and only a few thermally generated holes "minority carriers".

p-region n-region


• electrons  
• holes

pn junction

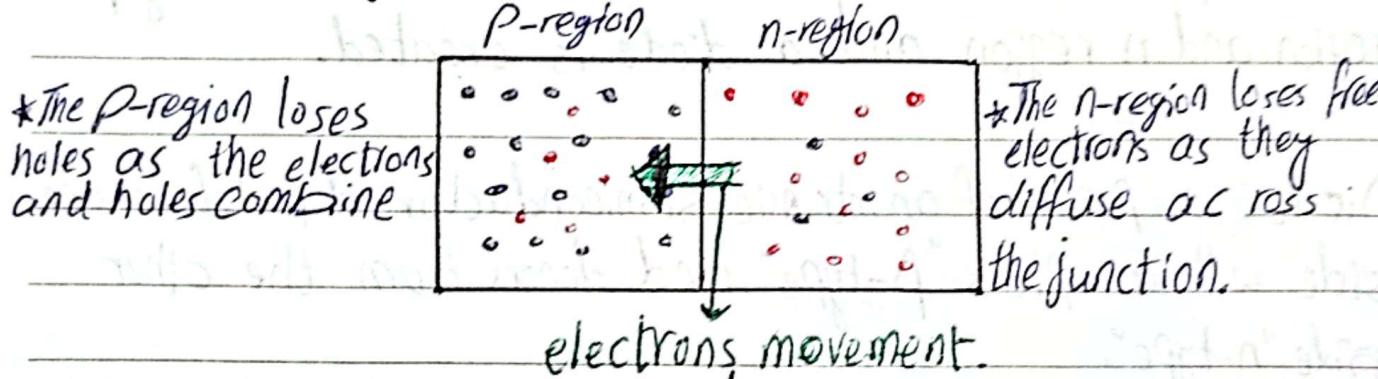- \* free electrons near the junction in n region diffuse "يسعى" into the p-region where they combine with holes near the junction.



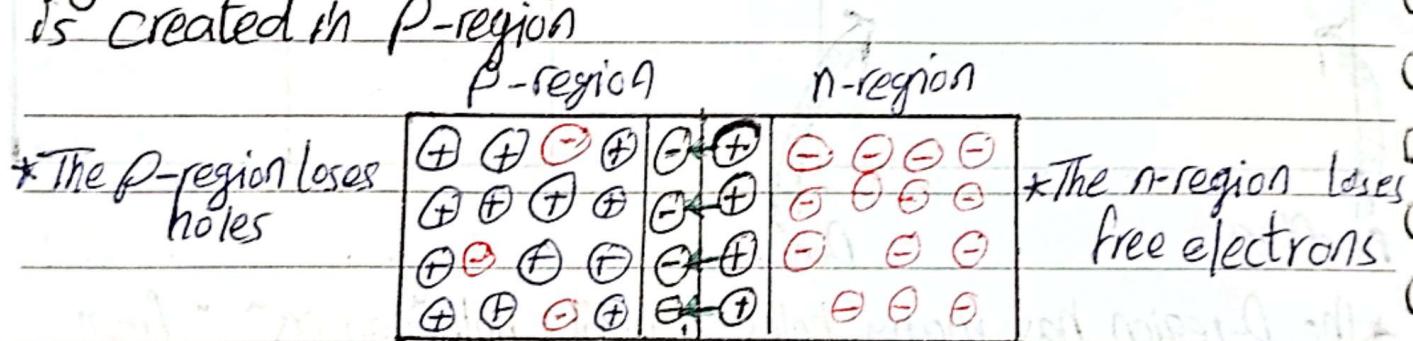- \* layer of positive charges "donor ions" near the junction is created in n-region.
- \* layer of negative charges "acceptor ions" near the junction is created in p-region



- \* The region near the junction is called a depletion region "نقطة انعدام".

- \* The term depletion region refers to the fact that the region near the junction is depleted "empty" of mobile charges "free electrons & holes".

- \* the positive & negative charges in the depletion region creates an electric field.
- \* remember:- the electric field direction is always from positive to negative.
- \* This electric field represents a barrier or a wall that prevent the flow of the carriers across the junction.

\* يُسْمِى هَذِهِ الْمَيَاهُاتِ وَالْإِلَكْتْرُوْنَاتِ الْمُرْكَبَةِ بِمَيَاهَةِ الْمُنْخُوبِ وَهِيَ الْمَيَاهَةُ الَّتِي يَسْعَى لَهَا مُجَاهِلُ كَهْرِبَاءٍ يَعْلَمُ بِمَعْنَى حَرْكَةِ الْمَيَاهَاتِ "الْإِلَكْتْرُوْنَاتِ وَفُلَقَاتِ" مِنْ حَلَالٍ مُّنْخُوبٍ.

\* if the electric field  $E$  is small, the electrons in region  $n$  continue to diffuse across the junction, then more and more positive and negative charges are created near the junction.

\* when the electric field  $E$  is large enough the diffusion process stops.

\* إِنَّ الْإِلَكْتْرُوْنَاتِ بِمَيَاهَةِ الْمُنْخُوبِ  $E$  يَعْلَمُ كَثِيرٌ بِعِنْدِهِ الْمَيَاهَةِ إِنَّهُ يَعْلَمُ مَوْرِدَهُ.


\* diffusion process stops when the layer of negative charges is strong enough to repel any further diffusion of electrons from  $n$ -region into  $p$ -region.

\* This electric field represents a barrier or a wall that prevent the flow of the carriers across the junction.

Depletion region

P-type region

n-type region

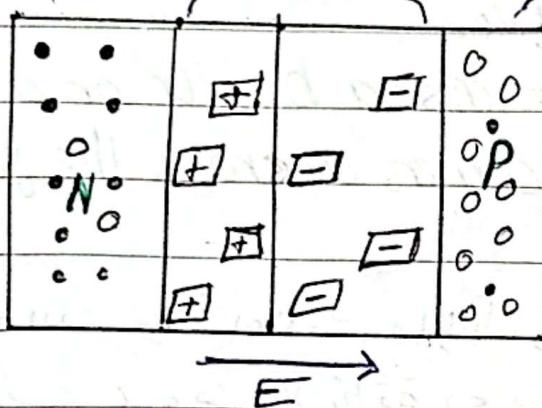


\* this electric field results in a difference of potential "V<sub>B</sub>" called **Barrier Potential** across the depletion region.

\* Barrier Potential "difference of potential" is expressed in volts and given by:-

$$V_B = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right)$$

- $V_T \rightarrow$  Thermal voltage,  $= \frac{KT}{q}$ , at  $300K = 0.025V$
- $N_D \rightarrow$  Donor doping concentration n-side
- $N_A \rightarrow$  Acceptor doping concentration p-side
- $n_i \rightarrow$  Intrinsic carrier concentration  $Si = 1.5 \times 10^{10}$   
 $Ge = 2.5 \times 10^{13}$
- $V_B \rightarrow$  Barrier Potential.

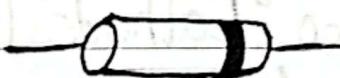\* the P-region of diode is called the anode (A) "القطب 积极" and is connected to a conductive "metal" terminal, the n-region is called the cathode (K) "القطب 负极" and is connected to a second conductive terminal.




"Anode" "cathode"

\* the anode is represented by a triangle, or an arrow and the cathode is represented by a vertical line.


\* Diode Biasing - refers to "applying an external voltage source across the diode to establish certain operating conditions".

\* There are two biasing conditions -

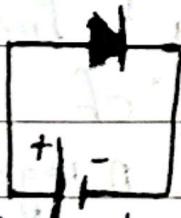

"Forward biasing" "مُحْبِّب مُعَدّل"

مُحْبِّب مُعَدّل  
الب مع مالي

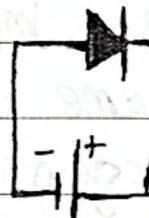

"Reverse biasing" "مُحْبِّب خَافِي"

مُحْبِّب خَافِي  
الب مع مُحْبِّب

- \* Is a condition in which the Positive side of a voltage source is connected to the P-region "anode" (the positive side of the diode) of the diode and the negative side of the voltage source is connected to the n-region "Cathode" (the negative side of the diode) of the diode.

٤- بالتحمّل: خرى التّقسيم للأهميّـ دـ بنو هـلـ المـوجـبـ بالـمـوجـبـ  
"الأثـورـ" وـالـسـالـبـ بالـسـالـبـ "الـكـافـورـ"

## Continue :- Forward biasing

21.2.2025


Electronics : Engineering

- \* Similarly, the holes in the P-region moves toward the junction.
- \* As holes in P-region flow into the depletion region, number of negative ions is reduced, and the width of the depletion region is reduced.
- \* The flow of the holes results in the hole current.

\* Forward Current - "I<sub>f</sub>"

\*  $I_f = \text{Electron current} + \text{Hole current}$
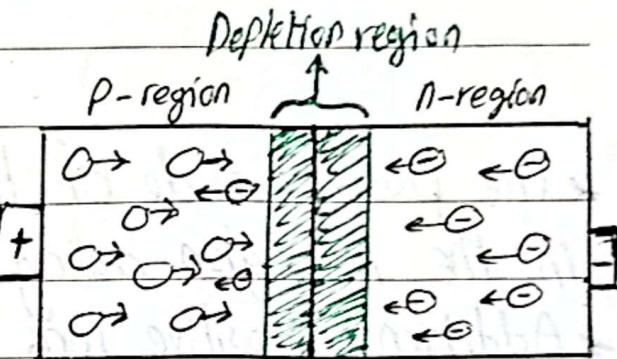
$$* I_f = I_s \cdot e^{\left(\frac{V_D}{n V_T}\right)}$$



Hole current  
Electron current

\* Where:-

\*  $V_D$  :- Voltage across the diode.

\*  $n$  :- constant = 1 for Ge and 2 for Si

\*  $V_T$  :- 0.025 V at 300 K


\*  $I_s$  :- saturation current

# Reverse Biasing

27/12/2025 التاریخ

Electronics المحتوى

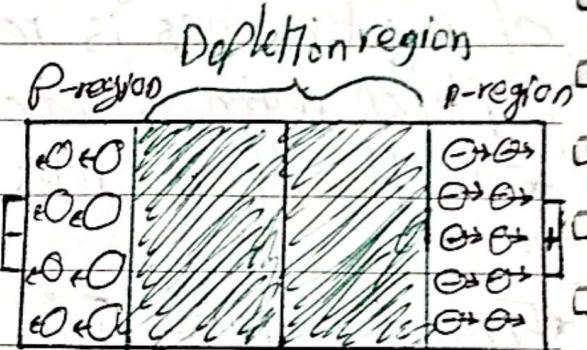- \* is a condition in which the negative side of a voltage source is connected to the P-region "anode" of the diode and the positive side is connected to the n-region "cathode" of the diode.



- \* the positive side of the voltage source attracts electrons in the n-region away from the junction.
- \* Additional positive ions are created that results in a widening of the depletion region.
- \* Similarly, holes in the p-region are pulled toward the negative side of the voltage source.
- \* additional negative ions are created that results in a widening of the depletion region.

# Reverse Current $I_r$


21/2/2023

Electronics: Engineering

- Minority electrons in the p-region are pushed toward the junction by the negative side of the voltage source and pass through the depletion region.
- Similarly, minority holes in the n-region move away from the positive side of the voltage source.
- This flow of the minority carriers results in an extremely small current.

$$\bullet I_r = \text{Electron current} + \text{Hole current}$$



$$\bullet I_r = I_s$$

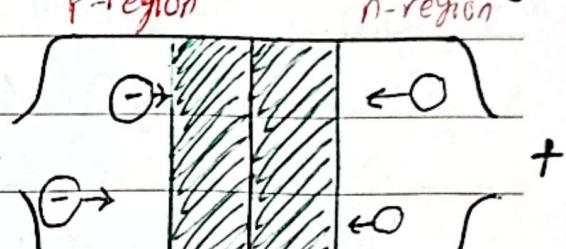

Electron Current

Hole Current

Voltage Source Current

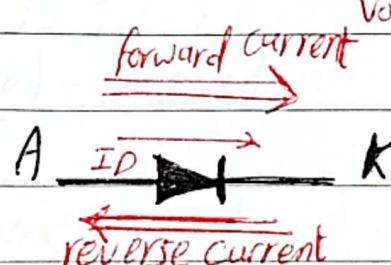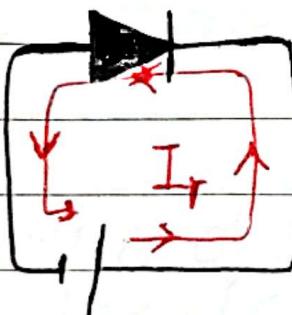

- Diode current "I<sub>D</sub>": The arrow direction in the diode symbol indicates the direction of the current through the diode.

$$\bullet I_D = I_f - I_r$$

$$\bullet I_f = I_s \exp\left(\frac{V_D}{\eta V_T}\right)$$

$$\bullet I_D = I_s \left[ e^{\left(\frac{V_D}{\eta V_T}\right)} - 1 \right]$$

# ch2 Part-1 Laws Summary

24.12.2025 التاریخ

Electronics المحتوى

$$V_B = V_T \ln \left( \frac{N_A N_D}{n_i^2} \right)$$

$$I_f = I_s e^{\left( \frac{V_D}{n_i V_T} \right)}$$

$I_r$  = Electron current + Holes current

$$I_r = I_s$$

$$I_D = I_f - I_r = I_s \exp\left(\frac{V_D}{n_i V_T}\right) - I_s = I_s \left[ \exp\left(\frac{V_D}{n_i V_T}\right) - 1 \right]$$

\*  $V_B$   $\Rightarrow$  Barrier Potential

\*  $V_T$   $\Rightarrow$  thermal voltage = 0.025V at 300K

\*  $N_A$   $\Rightarrow$  Acceptor doping concentration

\*  $N_D$   $\Rightarrow$  Doping donor concentration

\*  $n_i$   $\Rightarrow$  Intrinsic carrier concentration

\*  $I_f$   $\Rightarrow$  forward current

\*  $I_s$   $\Rightarrow$  saturation "leakage" current.

\*  $I_r$   $\Rightarrow$  reverse current.

\*  $V_D$   $\Rightarrow$  Voltage across diode.

\*  $\eta$   $\Rightarrow$  constant = 1 for Ge, 2 for Si

\*  $I_D$   $\Rightarrow$  Diode current.

$$\text{remember:- } n_i(\text{Si}) = 1.5 \times 10^{10} \text{ atoms/cm}^3$$

$$n_i(\text{Ge}) = 2.5 \times 10^{13} \text{ atoms/cm}^3$$

\* number of Si atoms per  $1\text{cm}^3$  :-  $5 \times 10^{22}$

\* number of Ge atoms per  $1\text{cm}^3$  :-  $4.4 \times 10^{22}$

$$\sigma = q(nM_n + pM_p) \quad \left. \begin{array}{l} \text{for Si} \\ M_n = 1300 \\ M_p = 500 \end{array} \right\}$$

$$\text{for Ge} \quad \left. \begin{array}{l} M_n = 3800 \\ M_p = 1800 \end{array} \right\}$$

# fast revision on chapter 1

18/13/2025 التاریخ

Electronics المحتوى

- \*intrinsic:- "جزئات شائعة بروز متساویات" بروز متساویات
- \*Extrinsic:- "جزئات شائعة مع الملوثات"
- \*Conductivity "σ" of intrinsic Semiconductors at 0K = zero.

→ the number of free electrons in the conduction band is equal to the number of holes in the valence band. علاوه على ذلك

\*The conductivity of an intrinsic semiconductor "σ" at 300K:-

$$\sigma = q(n_{ih} + p_{ip}) = q n_i (m_h + m_p)$$

\*where:-

- $q$  → electron charge =  $1.6 \times 10^{-19}$
- $n_i$  → intrinsic carrier concentration
- $n$  → free electrons concentration
- $m_h$  → Electron mobility
- $p$  → holes concentration
- $m_p$  → Hole mobility

\*when no doping is done "Intrinsic Semiconductors":-

$$n_i = n = p$$

\*Current density "J":-

$$J = \sigma \cdot E = \sigma \cdot \frac{V}{L} = q(n_{ih} + p_{ip}) \cdot \frac{V}{L} = q n_i (m_h + m_p) \cdot \frac{V}{L}$$

•  $V$  → Voltage

$L$  → distance between two points

- \*  $N_D$  "تقاضی خاس" pentavalent: - As, P, Sb more electrons
- \*  $N_A$  "تقاضی لاذق" Trivalent: - B, In, Ga more holes

in n-type "N<sub>D</sub>"

$$n = N_D \quad p = \frac{n_i^2}{N_D}$$

$$J = q n v_h = q N_D v_h$$

$$J = q n v_h E = q N_D v_h E$$

in p-type "N<sub>A</sub>"

$$p = N_A \quad n = \frac{n_i^2}{N_A}$$

$$J = q p v_h p = q N_A v_h p$$

$$J = q p v_h p E = q N_A v_h p E$$

→ في الموقت  $\tau$  نعیی  $N_A$  - Acceptors و  $N_D$  - Donors

$$n \cdot p = n_i^2$$

$$n + N_A = p + N_D$$

$$J = q(n v_h + p v_h p)$$

$$J = q(n v_h + p v_h p) \cdot E$$

$$Remember: - \quad \rho = \frac{1}{J}$$

$$V_d = M_h \cdot E$$

Where:-

•  $N_D$  : - Donor atoms concentration

•  $N_A$  : - Acceptors Atoms concentration

•  $\rho$  : - resistivity

•  $V_d$  : - drift velocity

n-type  $\rightarrow$  the current is due electrons

resulted positive & out

p-type  $\rightarrow$  holes

# Continue Ch 1

التاريخ: 19/3/2025

الموضوع: Electronics

\* Remember:-

\* if  $ax^2 + bx + c = 0$  then:  $x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$

\* الضرعه في اللاس بين  $N_D$  و  $N_A$  هي  $N_D - N_A$   $\rightarrow$   $N_D + N_A = N_i$

\* ولو العرق  $N_i$  يكون  $\geq$  بقداره وشوقه في يكون عشاريعرفه  $\rightarrow$  P-type و N-type

\*  $N_i$  depends on  $\phi$  :-

\* فـ  $N_i$  حـ  $\phi$   $\rightarrow$   $N_i = \frac{1}{qP(M_h + M_p)}$  يـ  $\phi$   $\rightarrow$   $N_i = \frac{1}{qP(M_h + M_p)}$

$$\cdot J = \frac{I}{A} = \phi \cdot E = q(N_h M_h + N_p M_p) \cdot \frac{IR}{L}$$

\* Constants:-

for Si:-

$$N_i = 1.5 \times 10^{10} \text{ atoms/cm}^3$$

$$M_h = 1300 \text{ cm}^2/\text{Vs}$$

$$M_p = 500 \text{ cm}^2/\text{Vs}$$

$$\text{number of atoms per cm}^3 = 5 \times 10^{22}$$

for Ge:-

$$N_i = 2.5 \times 10^{13} \text{ atoms/cm}^3$$

$$M_h = 3800 \text{ cm}^2/\text{Vs}$$

$$M_p = 1800 \text{ cm}^2/\text{Vs}$$

$$\text{no. atoms per cm}^3 = 4.4 \times 10^{22}$$

## Chapter 2 - Diodes: Structure & Operation & Applications

20/3/2023 التاريخ

Electronics


الموضوع:

موجة تطبيقيّة "intrinsic semiconductor"

جهاز دوّار diode

هيكله يتألّف من P قليل النتروجين و N كثيف النتروجين.

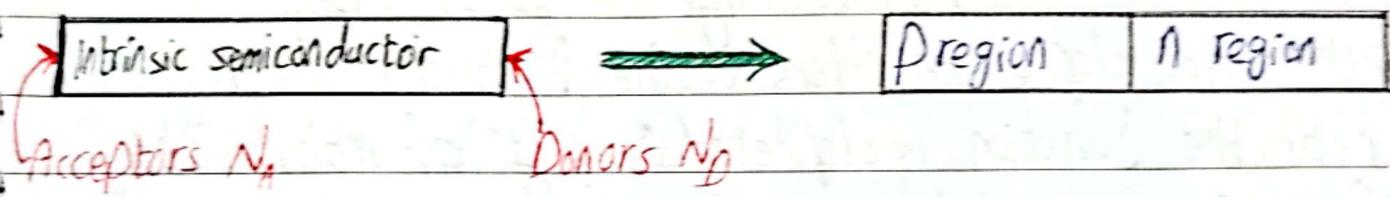
\* Diode: - a piece of intrinsic semiconductor doped with acceptors from one side and with donors from the other side, a boundary called "Pn" junction is formed between the resulting P region and N region.



\* The P-region has many holes "majority carriers" from acceptors atoms and only a few thermally generated electrons "minority carriers!"

\* The N-region has many electrons "majority carriers" from Donors atoms, and only a few thermally generated holes "minority carriers".

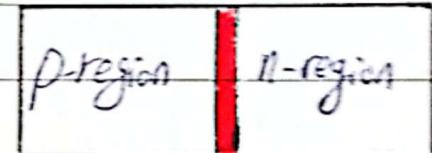\* free electrons near the junction in N region diffuse into P region where they combine with holes near the junction.



\* the N-region loses electrons as they dissolve.

Pn junction

\* the P-region loses holes as they combine with electrons. electrons movement

- \* layer of positive charges "donor ions" near the junction is created in "n" region.
- \* layer of negative charges "acceptor ions" near the junction is created in the "p" - region.

\* the p-region loses holes

P-region	n-region
0 0 0 0	0 0 0 0
0 0 0 0	0 0 0 0
0 0 0 0	0 0 0 0

\* the n-region loses electrons

Depletion range المقطوب

- \* the term depletion refers to the fact that the region near the junction is depleted "empty" of mobile charges "free electrons & holes"

المايوه هو عبارة عن الماء الذي يجب شربه عوضاً عن ماء الاترورات  
هي ناجية و خاسياً هي ناجية و قوية الاترورات  
في الماء "P" يتزوج ناجية الفتحات في الماء "P" و يتزوج  
هذا الماء وبعد كده ستصدر فيه طبقة من الشحنة الموجبة  
والسلبية ناجية مقطبة الناجي "مكانه مفيهوش" ولا الاترورات  
ولا فتحات".

\* The Positive & negative charges in the depletion region create an electric field.

\* This electric field represents a barrier or a wall that prevent the flow of the carriers across the junction.

→ Remember:- the electric field direction is from the Positive to negative. ("n" to "p").

\* If the electric field "E" is weak, electrons in the n region will continue to diffuse across the junction, then more & more positive & negative charges are created near the junction.

\* When the electric field is large enough the diffusion process stops.

\* Diffusion process stops when the layer of negative charges is strong enough to repel any further diffusion of electrons from "n" region into "p" region.

\* This electric field results in a difference of potential "V<sub>B</sub>" called barrier potential across the depletion region.



\* Barrier potential "difference of potential" is expressed in volts and given by :-

$$V_B = V_T \cdot \ln \left( \frac{N_A N_D}{n_i^2} \right)$$

•  $V_T \rightarrow$  thermal voltage, at room temperature "300 K" :-

$$V_T = 0.025 \text{ V}$$

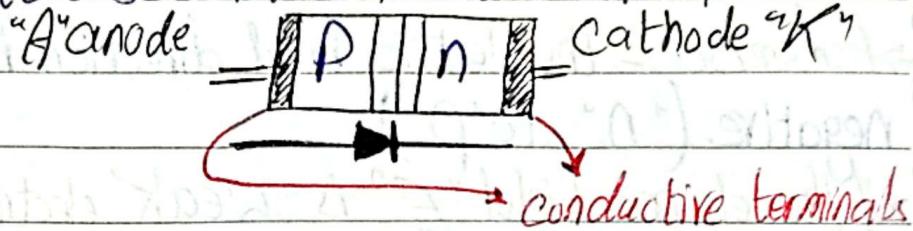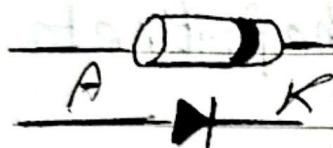- \* Diode Symbol: - the P-region is called the "anode" "Positive side" and its connected to a conductive "metal" terminal, the n-region is called a cathode "negative side" and its connected to a second conductive terminal



- \* The anode is represented by a triangle, the cathode is represented by a vertical line


الأشحنات الموجبة والسلبية في شبكة النضوب تغير مجال كهربائي أقوى مما يمكّن المقاومات والثوابت. عبارة "ذرويات موجبة"  $P$  عن ذرويات سالبة  $N$  بالشكل الذي يعيّن كل ما من شأنه أن ينبع تأثيره في مانعية النضوب لقوى لدرجه أنها تقل مجال كهربائي يوقف حركة الإلكترونات. الحركة التي يتوقف لها طبقة الذرويات السالبة في شبكة النضوب تنتهي كسرى مانعه لأنها تمنع الإلكترونات من الحركة. تصف الإلكترونات "ضرر الجهد الذي يستلزم" لعدم تمرر ذرث الجذر  $P$  صوالذ فوزان. صوالذ تغير  $V$  الأندود موجبيه والثانود سالبيه ويتم توصيله بـ "طرف معيني موصلي للأجهزة".

24/13/2025

\* Diode biasing :- applying an external voltage source across it to establish certain operating conditions.



+ Forward Biasing

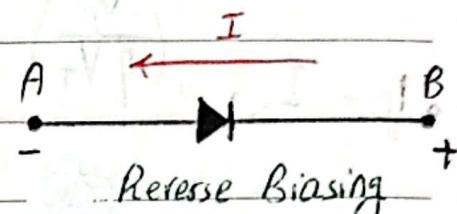

- Reverse Biasing

### Forward operation

- \* the positive side of a voltage source is connected to the P-region & the negative side of a voltage source is connected to the N-region.
- \* the anode "+" is the P-region & the cathode "-" is the N-region.
- \* the negative side of a voltage source pushes the electrons in the N-region towards the PN junction, and as they flow in the depletion region, the number of positive ions is reduced, resulting in the depletion region to narrow.
- \* the voltage source imparts sufficient energy to free electrons to overcome the barrier potential of the depletion region & move into the P-region, this flow of free electrons results in electron current.
- \* Similarly the holes in the P-region move toward the junction, and as they flow into the depletion region, number of negative ions is reduced, and by that the width of the depletion region is reduced.
- \* the flow of holes results in the hole current.

21/5/2025

Forward current  $I_f = I_s + I_e$  = Hole current + electron Current.

$$I_f = I_s + I_e = I_s e^{(V_D / V_T)}$$

$I_s \Rightarrow$  saturation current.

$V_D \Rightarrow$  Voltage across diode.

$\eta \Rightarrow$  constant = 1 for Ge, 2 for Si.

$V_T \Rightarrow 0.025$  at 300K.

معنى التوصيل الأذهاني :-

يعد حل الطري الموجب بالـ "P" واللطف

السلب بالـ "N"  $\Rightarrow$  الجهد المعاكس له

التيار ينبع  $\Rightarrow$  الـ "N" ينبع

في الـ "N" تترك ناحية الـ "P" وعده

يتدفق  $\Rightarrow$  لذا ينبع مع الصوّفات


وبعد ذلك يصفر العزلقة بقائه المضبوط

حركة الـ "electrons" في الـ "N" يتدفق

بتيار الـ "electrons"  $\Rightarrow$  الجهد منه  $\Rightarrow$  لذا  $\Rightarrow$  حرارة

يتدفق لـ "current" يتدفق بتيار الصوّفات الجهد منه  $\Rightarrow$  لذا

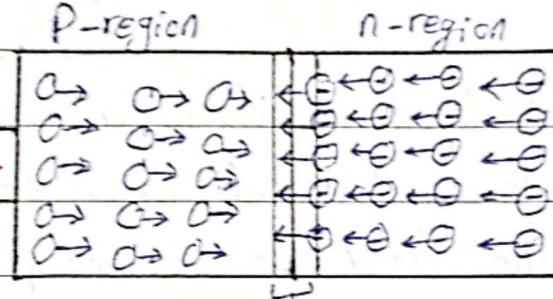لـ "current" يتدفق بتيار الـ "electrons" وتيار العوّضات ينبع  $\Rightarrow$  الـ "N"  $\Rightarrow$  تيار الأذهاني



depletion region

electron current  
Hole current

$I_f$

Reverse Operation

- \* the negative side of a voltage source is connected to the "P-region," and the positive side is connected to the "N-region".
- \* the positive side of voltage source attracts the electrons in the "N-region", resulting in creating additional positive ions that results in widening of the depletion region.
- \* Similarly the holes in P-region are pulled towards the negative side of the voltage source, resulting in creating additional negative ions, resulting in widening of the depletion region.

Reverse Current:-

- \* minority electrons in the P-region are pushed toward the junction by the negative side of voltage source and pass through depletion region, Similarly minority holes in the N-region are pushed toward the junction, moving away from the positive side of voltage source.



\* This flow of carriers results in an extremely small current.

$$\bullet I_r = \text{Electron current} + \text{Hole current}$$

$$\bullet I_r = I_s$$

$\Rightarrow I_s \Rightarrow$  saturation current.

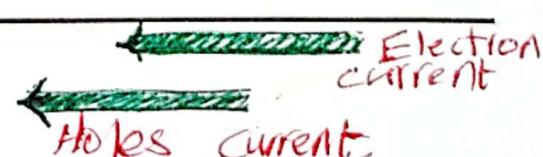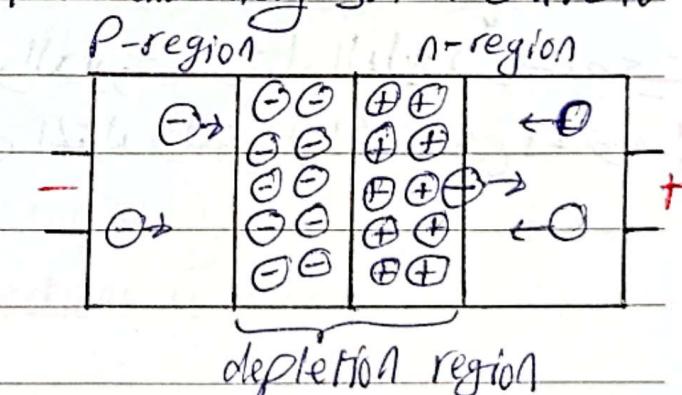$\Rightarrow I_r \Rightarrow$  reverse current.



\* Diode current,  $I_D$ : - the arrow direction in the diode symbol indicates the direction of current through the diode.

$$I_D = I_f - I_r = I_f - I_s$$

$$I_D = I_s \cdot e^{\left(\frac{V_D}{\eta V_T}\right)} - I_s = I_s \left[ e^{\left(\frac{V_D}{\eta V_T}\right)} - 1 \right]$$

\* في حالة التوصيل الخلفي "العكس للتيار" يتم توصيل الطرف الموحي له وللجهة بار "+" والطرف السالب بار "-" مما يؤدي إلى تناوب بين الكترونات الـ "e" والطرف الموحي للجهة وبيسم "موجات الـ "e" والطرف السالب للجهة، فتسوء منطقه التصوب وتنصرف في موجات الـ "e" في بعض الكترونات الـ "e" و موجات الـ "e" تكون منطقه التصوب مما يؤدي إلى تولد تيار صغير جداً يسمى بالتيار العكسي.

### \* تيار الداير:

\* السهم يشير إلى إتجاه تيار الداير، و تيار الداير يسمى بـ "التيار المعاكس" لأنها تعيق التولد والتيار المعاكس المولد.

\* Voltage-Current Characteristic of Diode:-

→ The Graphical relationship between the voltage and the current in a diode.

\* with 0 volt across the diode, there is zero current.

\* if a voltage across a diode is increased above zero volt and below the barrier Volt "Potential", the current increases very little.

\* when a voltage across a diode reaches the barrier potential, the current increases rapidly.

\* when a reverse voltage is applied across a diode there is an extremely little small reverse current through a diode.

$$I_D = I_f - I_s \Rightarrow I_D = -I_s$$


\* if the reverse current increased to a value called the breakdown voltage "V<sub>BD</sub>", The high reverse voltage "V<sub>BD</sub>" imparts energy to the minority electrons so that they speed through the p-region, they collide with atoms and knock valence electrons out of orbit and into the conduction band.

$$V_d = v_n \cdot E = v_n \cdot \frac{V}{L} \Rightarrow \text{Drift velocity}$$

\* the newly created conduction electrons repeat the process.

\* as a result the number of electrons quickly multiply, and the multiplication of conduction electrons is known as the "avalanche effect".

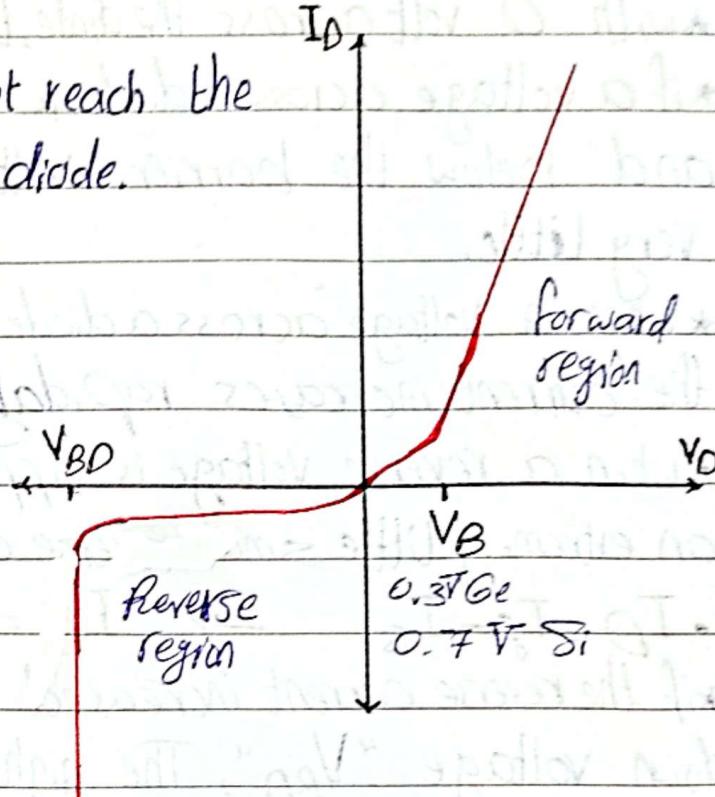- \* the resulting conduction electrons go through the n-region and result in a very high reverse current.
- \* The resulting heating from the increased reverse current will damage the diode.
- \* the reverse voltage does not reach the breakdown voltage of the diode.




\* الدايوود ليس كوه الفولت رقيقة، يكونه استار (الى ماشى فيه ده مصر) لو فحنتها نفسي الفولت (هذا ظر يادة خصيصة عى التيار) لعد ما الكهرو يوصل للجهة الموجة (وتفتح التيار بعده جاحد) وده من حالة التوصيل الأهمى.

\* ده من حالة التوصيل العكسي لما يتصور جهود على الدايوود يفتأمل يطلع ويقيم خصيصة لدها يوصل لفقيهة جهه الانفيار  $V_{BD}$  وعنهما استار يعدي عادي بعد ما الكهرو يوصل لجهود إلى نسار، الانفيار وينحرج تأثير اقلانشى على أنه التخانعه بتاع الالكترونيات

الموصولة "الى كانت الكترونات رابطة التلاميذ قبلها نهر التيار"


التاريخ 21/3/2025
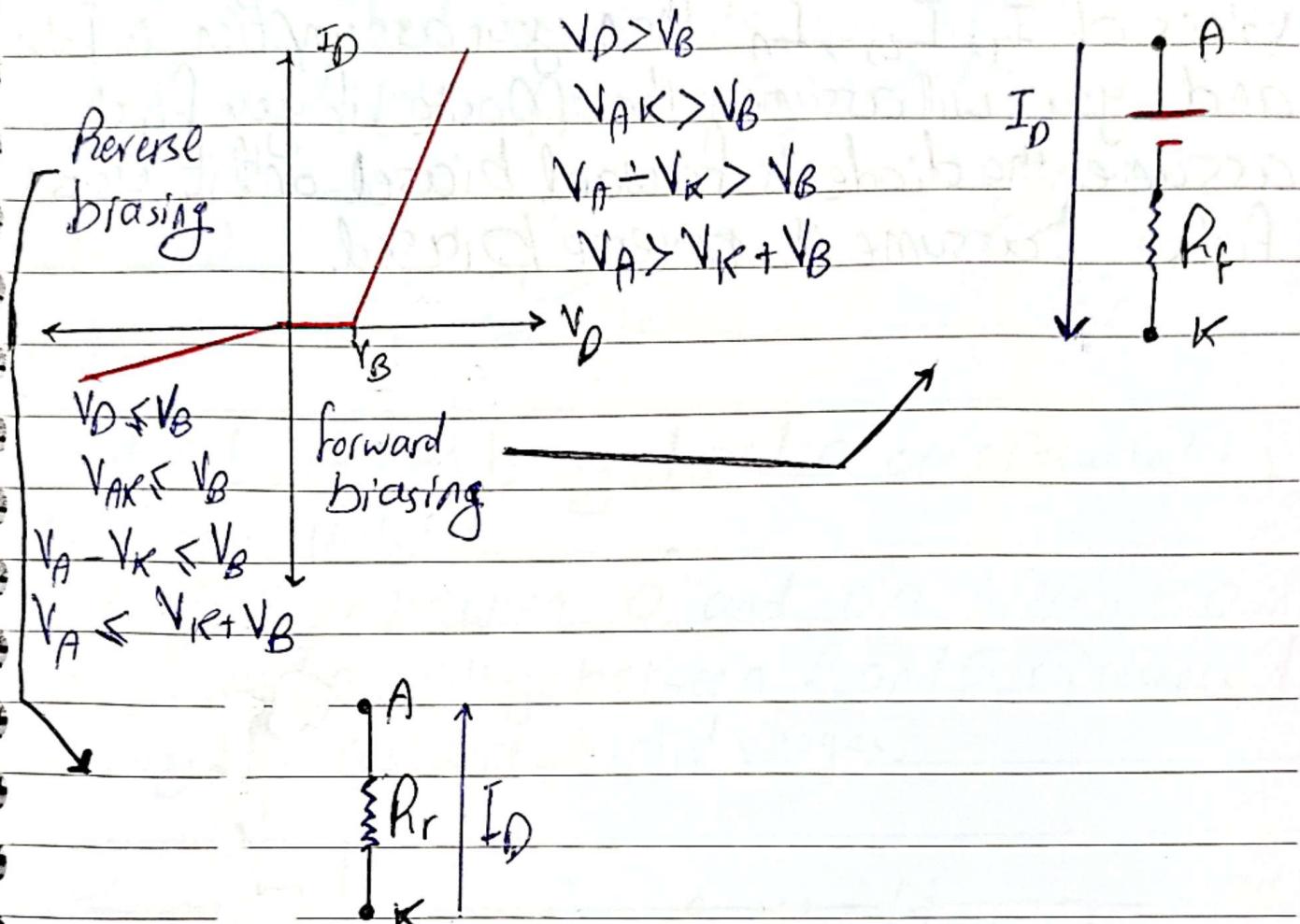
## \* Piecewise linear characteristics of Practical Diode -



## \* Piecewise linear characteristics of Ideal Diode:-

Reverse biasing      forward biasing

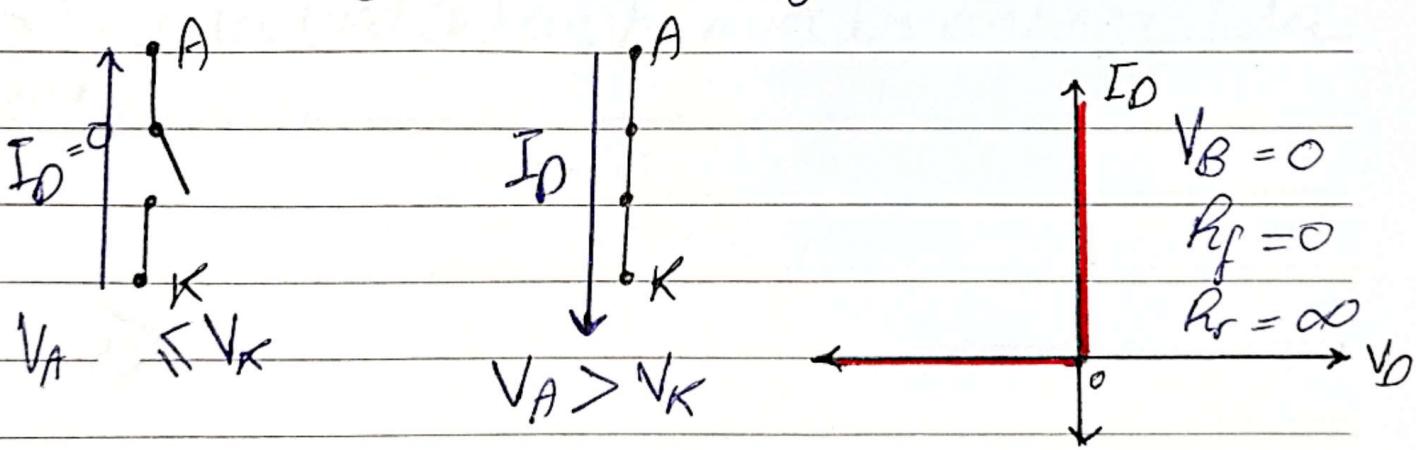

Ideal diode neglects the effects of barrier potential, forward resistance & reverse current, working like a switch.

# Continue Chapter 2

21/8/2025 التاریخ:

Electronics الموضع:

\* while solving with Kershoff's law if you get negative values of  $I_1, I_2, I_3$  then your assumption is false and you will assume the opposite, if you first assume the diode is forward biased and it was false, assume it reverse biased


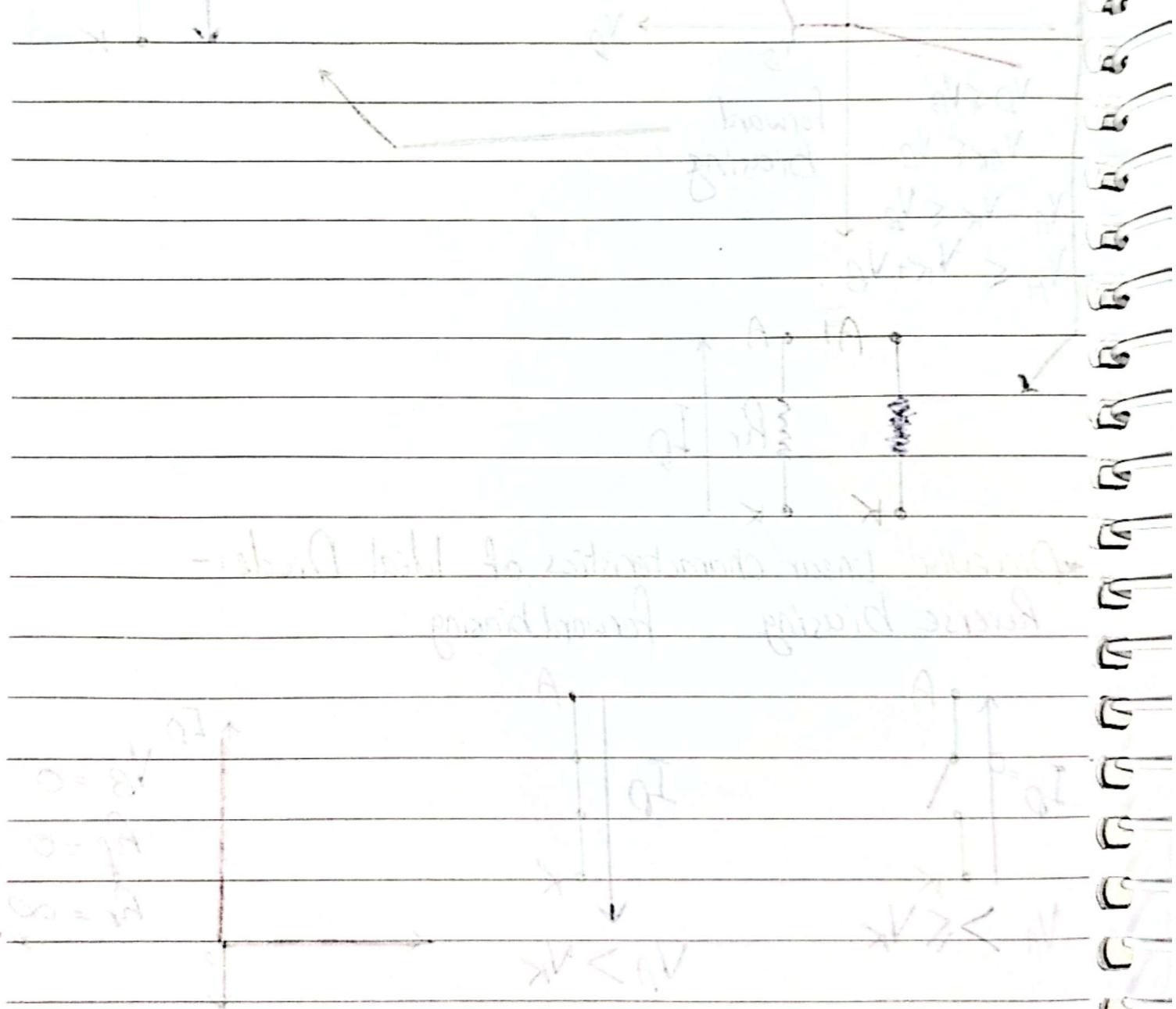




Diagram indicates need to do it with simple steps, will do it with parallel circuit now.

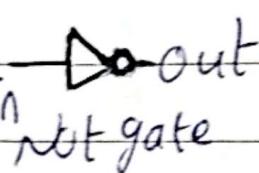- \* Digital Circuits: - like microprocessors, memory, ...
- \* logic gates, - hardware elements that perform the logical operations on binary numbers "0" and "1".



- \* in digital circuits, binary 1 and 0 are represented by two voltage levels.

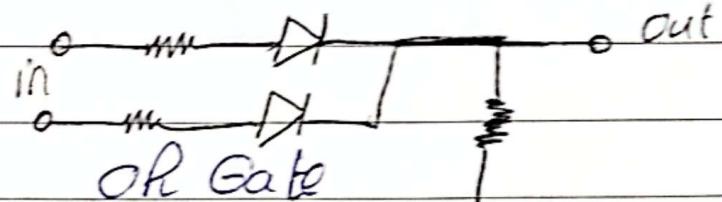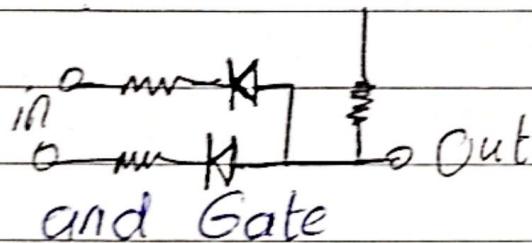→ any voltage between 0 and 0.9 represent 0 in binary, and any voltage between 2 and 5 represents 1 in binary, the rest are invalid voltages.



- \* logic gates (and, OR) can be made by combining diodes and resistors.

## Chapter 3: Bipolar Junction Transistors "BJT's"

21/3/2025 تاریخ


Electronics المحتوى

\* Bipolar Junction transistor:-

\* the term bipolar refers to the use of both holes and free electrons as current carriers.


\* BJT consists of three doped semiconductors regions

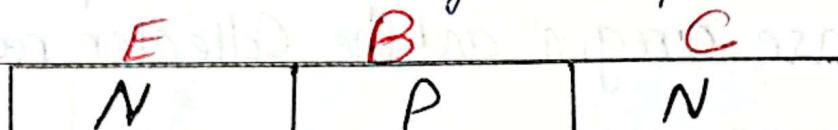\* NPN BJT:- has two "n" regions separated by "P" region.



\* PNP

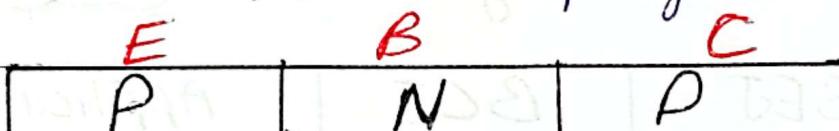BJT:- has two "P" regions separated by "n" region



\* the three regions are called:-

• E  $\Rightarrow$  emitter

• B  $\Rightarrow$  base

• C  $\Rightarrow$  collector

\* the emitter region is heavily doped.

\* the collector region is moderately doped.

\* the base region is lightly doped and very thin

\* each region is connected to a conductive terminal "Metallic lead" These are labeled E, B, C for emitter, base, collector.

\* Junctions of NPN BJT, - it has 2 junctions.

→ the base-emitter junction "BEJ" - the pn junction joining the base region and the emitter region.



→ The base-collector junction "BCJ" - the pn junction joining the base region and the collector region.

\* Modes "operation regions" of NPN BJT -

Mode	BEJ	BCJ	Applications
Active	forward	reverse	Amplifier
Saturation	forward	forward	Closed switch
Cutoff	reverse	reverse	Open switch

→ Digital circuits

\* Symbol of NPN BJT:-

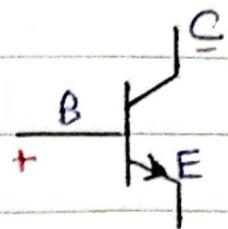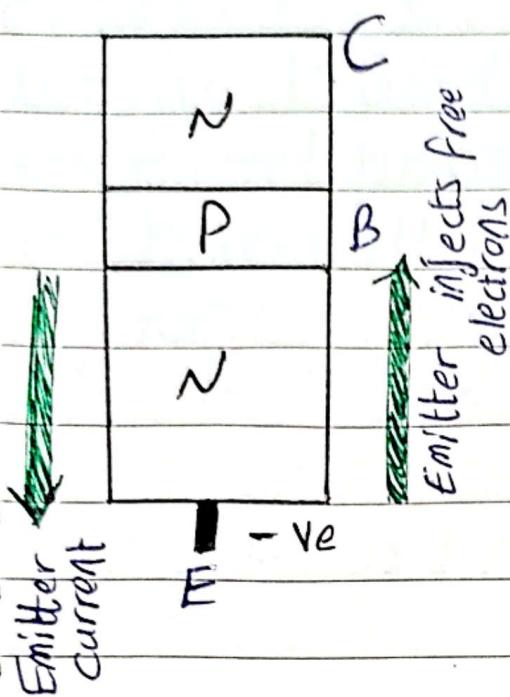

\* the arrow on the emitter terminal refers to the flow direction of emitter current when the emitter-base junction is forward biased.

- \* Active mode of  $NPN$  "Amplifier" - external dc voltages are applied to set  $BEJ$  is forward biased &  $BCJ$  is reverse biased
- \* the forward biasing between base and emitter narrows the base-emitter depletion region.
- \* the reverse biasing between base and collector regions widens the base-collector depletion region.
- \* Operation of Active mode of  $NPN$  BJT :- in  $nPN$  BJT, the heavily doped  $N$ -type emitter region has a very high free electrons density.
- \* these free electrons easily diffuse "move" into the "P" type base region, most of the emitter electrons diffuse into the collector region by the attraction of the positive collector voltage source.
- \* Small percentage of the emitter electrons recombine with holes at the base region.


\* الباونت تقييم وابا مع مخطط والقاعد  
 \* لـ  $BEJ$  توصيل الترانزستور الاولي  $\rightarrow$  يدخل من  $BEJ$  ويزداد عرض مساحة جذب  $\rightarrow$  ولو  $\rightarrow$   $BCJ$  يدخل  $\rightarrow$  ينبع من  $BCJ$  بحجم اكبر للتيار  
 \* السعى الذي عا باعث يحد ايجي متياره  $\rightarrow$  لا يتوصل ايجي

- \* Just as in a forward biased diode, -
  - \* the flow of electrons from emitter into base results in electron current  $I_{nE}$ .
  - \* the flow of holes from base into emitter results in hole current  $I_{pE}$ .
  - \* the total emitter current is the sum of these two currents.
- $I_E = I_{nE} + I_{pE}$
- \* the flow of the emitted electrons from emitter into collector results in electron current  $I_{nC}$ .
  - \* The flow of minority holes from collector into base results in hole current  $I_{pC}$ .
  - \* the other part of the collector current  $I_{CB}$  is due to the flow of the minority electrons from base into collector.
  - \* The total collector current is the sum of these currents.

•  $I_C = I_{CB} + I_{nC} + I_{pC}$

التاريخ: 21/3/2025

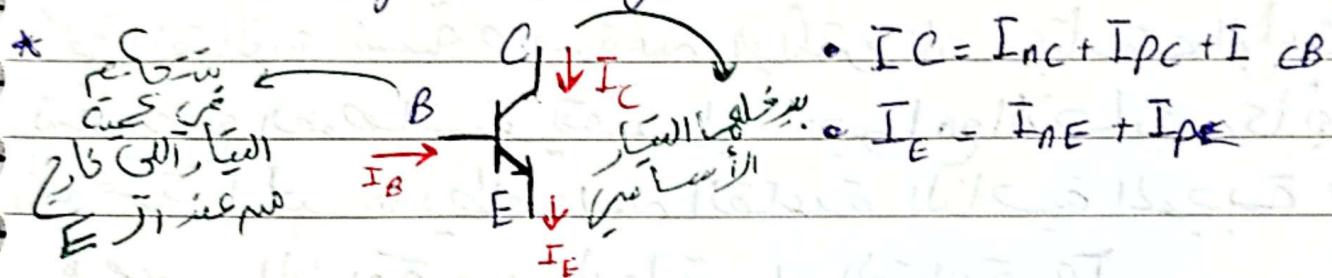- \* In base region, a small percentage of emitter electrons recombine with holes.
- \* These recombined electrons move from one hole to the next and finally flow out of the base lead towards the positive side of external source forming the base electron current "I<sub>B</sub>".
- \* This recombination are less in number because of smaller area and light doping of base.



ستتحكم في حركة الالكترونات

PNP  $\Rightarrow$  ستتحكم في حركة الفوهةات

كل ما في التوزيع  $I_B$  كل ما في  $I_C$  كل ما في  $I_B$

لأن جهد موجب بالـ  $E$

لأن جهد سلبي بالـ  $B$

وحيثما ينبع كثرة نسبية emitter من  $E$  فيه جزء ينبع

جاءه الالكترونات الأخرى التي فيه ينبع  $I_C$  فيه جزء ينبع

وهو جزء ينبع  $I_C$  فيه جزء ينبع  $I_E$  فيه جزء ينبع  $I_B$

الـ "base" حركة الالكترونات ينبع  $I_B$ :-

وهي حركة  $I_{NE}$  ينبع  $B$  و  $E$  و  $I_{PE}$  ينبع  $E$  و  $I_{NE}$  ينبع  $B$

الـ "E" ينبع  $I_E$  و  $I_E$  ينبع  $I_B$  و  $I_E$  ينبع  $I_C$  و  $I_E$  ينبع  $I_E$  ينبع  $I_E$

$$I_E = I_{PE} + I_{NE}$$

مجموع

\* بال بالنسبة للجهاز "Collector"  $I_C = I_{NC} + I_{PC} + I_{CB}$

\* حركة الإلكترونات من المCollector للجهاز يسمى  $I_{PC}$

\* حركة الفوتونات من الجهاز للCollector يسمى  $I_{CB}$

\* حركة الإلكترونات من المCollector للجهاز يسمى  $I_{NC}$

\* تيار الجهاز الكلي  $I_C$  يسمى مجموعهم

$$I_C = I_{NC} + I_{PC} + I_{CB}$$

\* في المقادير نسبة كبيرة من الإلكترونات يتبع المCollector  
يتردج مع الفوتونات. و يقدروا بين 50% و 70% من التحالب بينهم  
ينتظر كلوا لـ  $\beta$  ما يطلقوا عليه المقادير المائية الموجبة من  
نوع المطردة و يولدوا تيار الماء  $I_B$ .

\* كل تيار يولد منه إيجاد

- تيار الماء  $I_B$  من المتردجات المCollector

- تيار المCollector  $I_E$  هو مجموع المطردة و مصدر المتردجات المCollector

- تيار الجهاز  $I_C$  هو المتردجات المCollector و مجموع المطردة المCollector

$$\beta = \frac{I_C}{I_B} \quad \alpha = \frac{I_C}{I_E}$$

\* مجموع المطردة  $I_E = I_C + I_B$

\* نسبة المطردة  $\alpha = \frac{I_C}{I_E}$

$$\bullet I_E = I_C + I_B = \beta I_B + I_B = (\beta + 1) \cdot I_B$$

$$\bullet I_C = \alpha I_E = \alpha I_C + \alpha I_B$$

$$\bullet \alpha I_B = I_C - \alpha I_C = I_C (1 - \alpha)$$

$$\bullet I_C = \frac{\alpha I_B}{1 - \alpha}$$

Continue

التاريخ: 21/3/2025

Chapter 3

الموضوع: Electronics

## Summary of laws

$$\bullet I_C = I_{nC} + I_{pC} + I_{CB} \quad \bullet I_E = I_{nE} + I_{pE}$$

$$\bullet I_E = I_C + I_B \quad \bullet \beta = \frac{I_C}{I_B} \quad \bullet \alpha = \frac{I_C}{I_E}$$

$$\bullet I_E = I_C + I_B = \beta I_B + I_B = (\beta + 1) I_B$$

$$\Rightarrow I_E = I_C + I_B = \alpha I_E + I_B = \alpha(I_C + I_B) + I_B$$

$$\Rightarrow I_C = \alpha I_E = \alpha(I_C + I_B) = \alpha I_C + \alpha I_B$$

$$\Rightarrow I_C - \alpha I_C = \alpha I_B \Rightarrow I_C(1 - \alpha) = \alpha I_B$$


$$\bullet I_C = \frac{\alpha I_B}{1 - \alpha} \Rightarrow \bullet \beta = \frac{\alpha}{1 - \alpha}, \text{ since } I_C = \beta I_B$$

$$\bullet \frac{\beta}{1 + \beta} = \alpha$$

\* the Application of Active mode BJT is Amplifiers-

\* Amplifier is a device which used to increase the amplitude of the signal applied to its input.

• أكبر موجة جهاز التكبير في دائرة الموجة

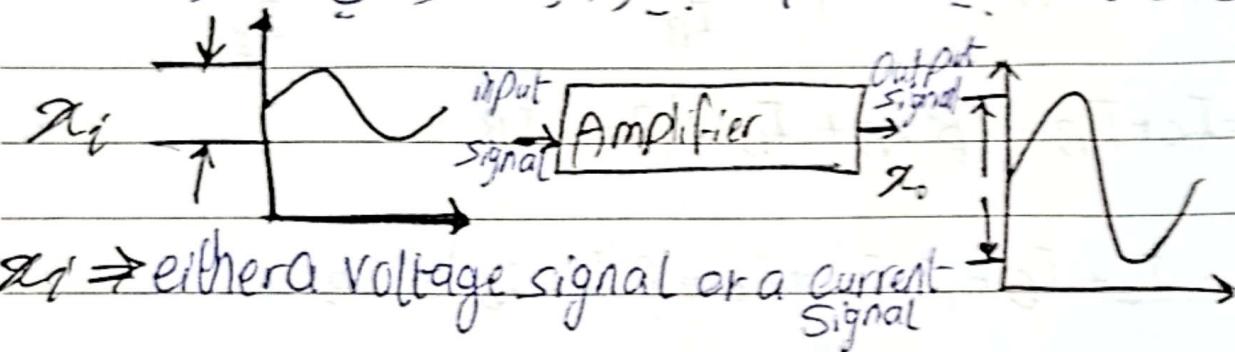


•  $x_i \Rightarrow$  either a voltage signal or a current signal

\* Amplifier Gain "A":- the ratio of output signal to the input signal

$$A = \frac{x_o}{x_i}$$

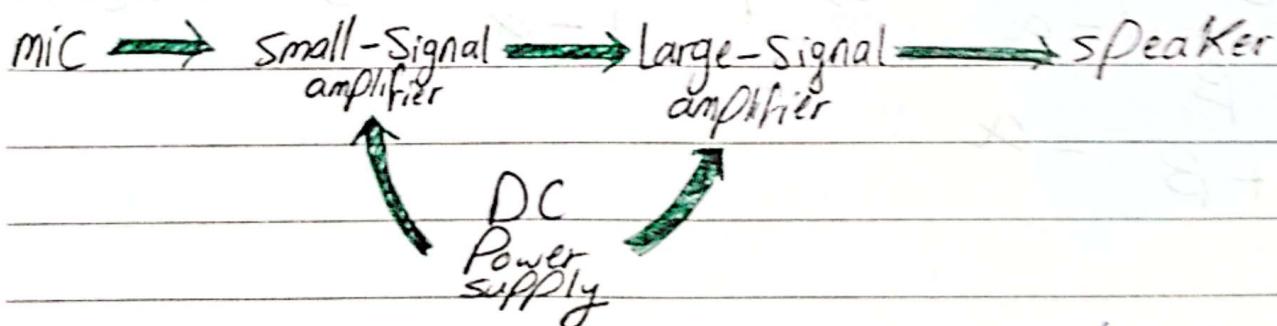\* Small Signal Amplifier vs. Large Signal Amplifier:-



\* Mic:- Converts sound to electrical signal in microvolts/millivolts range.

\* Small Signal Amplifier:- converts the millivolts signal to large output signal in the volt range and output power less than 1 watt.


\* Large Signal Amplifier:- produces power greater than 1 watt to the load 'Speaker'.

\* Speaker:- converts electrical signal to sound.

\* in general, an amplifier has triangle symbol indicates the direction of signal flow from the input side to the output side.





\*  $R_{in}$  - input resistance of the amplifier, is seen at the input terminal by the signal source "V<sub>s</sub>". It is a ratio of the input voltage to the input current.

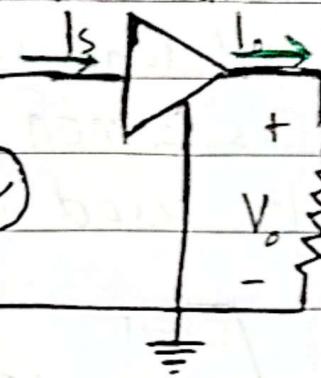\*  $R_{out}$  - output resistance of the amplifier, is seen at the output terminal by the load "R<sub>L</sub>".



\* Non-Inverting amplifier - amplifies the signal with 0° phase shift between input & output signals.

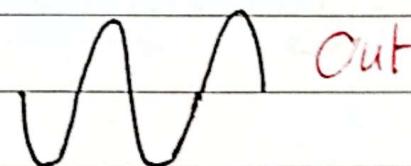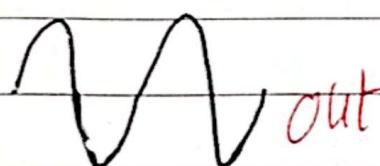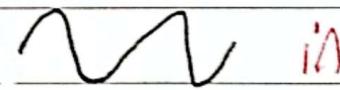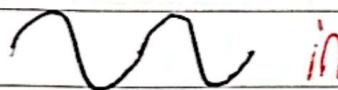\* Inverting amplifier - amplifies the signal with 180° phase shift between input and out signal.




Non inverting amplifier.

Inverting amplifier.

\* Bipolar transistors can be connected in 3 different ways.

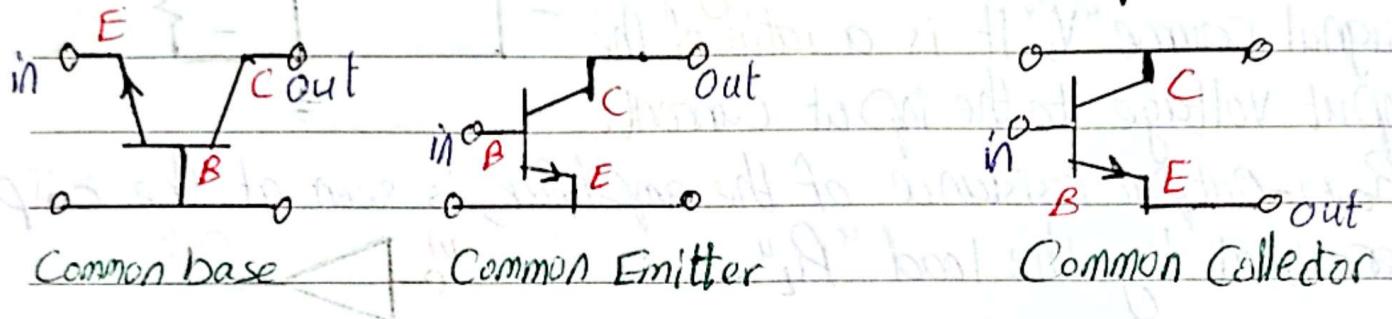\* in each one of the, one lead is connected to the input, a second lead is connected to the output and a third lead is common, connected to both input and output, and it's used as a circuit reference point.



\* Characteristics of Common-Emitter Amplifiers "CE":-

1. Current gain " $A_I$ " is high.

2. Voltage gain is high.

3. Input resistance is medium.

4. Output resistance is medium.

\* Applications:- of the three Configurations the CE amplifier alone is capable to provide both voltage gain and current gain, Hence the CE amplifier is widely used for amplification purpose.

\* Characteristics of common-base amplifiers:-

1. Current gain is less than unity

2. Voltage gain " $A_v$ " is high.

3. The input resistance is the lowest of all 3 configurations.

4. The output resistance  $R_o$  is the highest of all 3 configurations.



\* Applications:- the CB amplifier is not commonly used for amplification purpose, It is used for:-

1. matching low impedance source

2. as an amplifier with a voltage gain exceeds unity.

3. for driving a high impedance load.

4. as a constant current source.

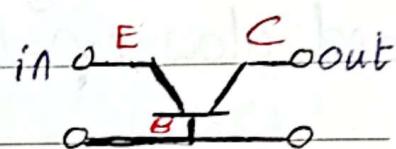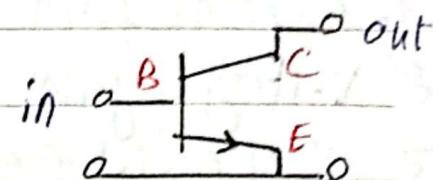


الفكرة هي أن  $A_v$  يزيد مع  $R_o$  وهذا ينافي المفهوم المتعارف عليه

Part II

## \* Characteristics of Common collector Amplifiers

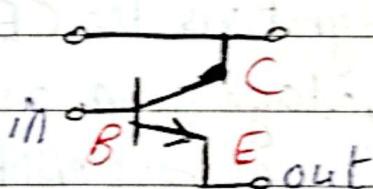1. Current gain is high and almost equal to CE Gain
2. Voltage gain is less than unity.
3. Input resistance is the highest of all 3 of them
4. Output resistance is the lowest of all 3 of them



\* Applications:- The CC amplifier is commonly used as a buffer stage between a high impedance source and a low impedance source.

\* Cutoff mode of NPN BJT: - external dc voltages are applied to set  $BE_J$  and  $BC_J$  to reverse biasing.

\* all the terminal currents are zero and the BJT acts like an open switch.  $I_F = I_C = I_B = \text{zero}$

\* Saturation mode of NPN BJTs: - In saturation mode, external DC voltages are applied to set  $BE_J$  and  $BC_J$  to forward biasing, and the BJT acts like a closed switch.

\* when the base-emitter junction becomes forward biased, the base current is increased " $I_B$ " the collector current is also increased ( $I_C = \beta I_B$ ) and " $V_{CE}$ " decreases as a result of more voltage drop across the collector resistor ( $V_{CE} = V_{CC} - I_C R_C$ )

$$\bullet V_{CE} = V_{CC} - I_C R_C$$

→  $V_{CE}$  → the voltage between the collector and emitter.

→  $V_{CC}$  → the supply voltage.

→  $I_C$  → the collector current.

→  $R_C$  → the collector resistance.

$$V_{CE} \text{ in saturation mode} = 0.2 \text{ V}$$

$$\text{and } V_{BE} = 0.7 \text{ V}$$

## Chapter 1 Laws Summary

التاريخ: 23/3/2025

## Electronics : الالكترونيات

$$\star \text{Siemen} = \frac{1}{\text{Ohm}} = \frac{1}{\text{S}}$$

\*Conductivity of intrinsic semiconductor "σ" = zero at  $0\text{K} = \frac{273}{\text{C}}$

$$N_i^2 = N_0 P$$

$$\bullet \delta = q(nM_n + Pnlp)$$

$$\bullet \delta = q n_i (\mu_n + \mu_p) \text{ for intrinsic semiconductors only.}$$

•  $n_i = n = P$  •  $n_i^2 = n^2 = P^2$  for intrinsic semiconductors only.

$$J = \mathcal{Q} \cdot E = \mathcal{Q} \cdot \frac{V}{L} = \mathcal{Q} \cdot (N_{Mn} + P_{Mn}) \cdot \frac{V}{L} = \mathcal{Q} (N_{Mn} + P_{Mn}) \cdot \frac{A \cdot I}{L} = \frac{I}{A}$$

## $N$ -type Semiconductors:-

$$n = n_0, \rho = \frac{n^2}{n_0}$$

$$\cdot 6 = 9 \pi M_n = 9 \pi_0 M_n$$

## \*P-type Semiconductors:-

$$P = N_A \rightarrow n = \frac{N_A}{N_A}$$

$$\bullet \delta = q D \delta p = q N_p \delta p$$

\* in case of Si or Ge +  $N_A + N_D$  -

$$N_D + P = n + N_A$$

$$\nabla d = \mu_n \cdot E$$

$$\bullet f = \frac{1}{6}$$

الفرق بين  $N_p$  و  $N_n$  أقل من 2، يستخدم المقاومات -  
العنصر من الأسيين  $N_p$  و  $N_n$  أكبر من 2، تحقق أنهما أكبر  
عندما تحقق هذان  $P$ -type و  $N$ -type

\* Symbols meaning:-

- $n \rightarrow$  Free electrons concentration
- $p \rightarrow$  Holes concentration.
- $N_A \rightarrow$  Basic carrier Concentration.
- $n_d \rightarrow$  Free electrons mobility
- $\mu_p \rightarrow$  Holes mobility.
- $q \rightarrow$  electron charge =  $1.6 \times 10^{-19}$
- $E \rightarrow$  Electric Field
- $\sigma \rightarrow$  Conductivity.
- $\rho \rightarrow$  resistivity
- $V \rightarrow$  Voltage
- $L \rightarrow$  distance between two points
- $R \rightarrow$  resistance
- $I \rightarrow$  current
- $A \rightarrow$  Cross sectional area of the conductor.
- $N_A \rightarrow$  Acceptor Atoms concentration.
- $N_D \rightarrow$  Donor Atoms concentration.
- $V_d \rightarrow$  drift velocity.

\* remember:-

\* if  $ax^2 + bx + c = 0$  then -

$$x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

## \* Constants :-

→ for Si :-

- $N_i = 1.5 \times 10^{10}$  atoms/cm<sup>3</sup>
- $\mu_n = 1300$  cm<sup>2</sup>/V.s
- $\mu_p = 500$  cm<sup>2</sup>/V.s
- number of atoms per cm<sup>3</sup> =  $5 \times 10^{22}$

→ for Ge :-

- $N_i = 2.5 \times 10^{13}$  atoms/cm<sup>3</sup>
- $\mu_n = 3800$  cm<sup>2</sup>/V.s
- $\mu_p = 1800$  cm<sup>2</sup>/V.s
- number of atoms per cm<sup>3</sup> =  $4.4 \times 10^{22}$

# Chapter 4: Digital Circuits

13/4/2025 التاریخ


ELECTRONICS : الالكترونيات

\*Types of logic gates:-

\*AND Gate ( $A \cdot B$ ):- Outputs 1 only if all inputs are 1.



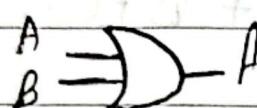\*OR Gate ( $A + B$ ):- Outputs 1 if at least one input is 1.



\*NOT Gate ( $\bar{A}$ ):- Inverts the input (if it's 1 it gives 0, and if it's 0 it gives 1).



«Truth table»

C	B	A	$F(\text{AND})$	$F(\text{OR})$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

\* Boolean Algebra rules:-

$$* A + 0 = A \quad * A \cdot 1 = A \quad * A + 1 = 1 \quad * A \cdot 0 = 0$$

$$* A + A = A \quad * A \cdot A = A \quad * A + \bar{A} = 1 \quad * A \cdot \bar{A} = 0$$

$$* A + B = B + A \quad * A \cdot B = B \cdot A \quad * (A + B) + C = A + (B + C)$$

$$* (A \cdot B) \cdot C = A \cdot (B \cdot C) \quad * A \cdot (B + C) = A \cdot B + A \cdot C$$

$$* A + (B \cdot C) = (A + B) \cdot (A + C) \quad * A + A \cdot B = A$$

$$* A \cdot (A + B) = A \quad * A \cdot B + A + \bar{B} = A = A \cdot (B + \bar{B})$$

$$* (A + B) \cdot (A + \bar{B}) = A(A + B) + \bar{B}(A + B) = A \cdot A + A \cdot B + A \cdot \bar{B} + \bar{B} \cdot B \\ = A + A + 0 = A$$

$$* \overline{(A + B)} = \bar{A} \cdot \bar{B} \quad * \overline{(A \cdot B)} = \bar{A} + \bar{B}$$

## 1.2 Introduction to number Systems

9/15/2025

ELECTRONICS: Engineering

\* characteristics to define a number system:-

1. the number of independent digits used in the number system.
2. the place values of the different digits constituting the number.
3. the maximum numbers that can be written with the given number of digits.

\* the radix "Base" of the number system:- the number of independent digits used in the number System, like:-

⇒ the decimal number System radix = 10, so it has 10 digits:-

0 1 2 3 4 5 6 7 8 9 0

⇒ the binary number System radix = 2, So it has 2 digits:-

0 1

⇒ the octal number System radix = 8, so it has 8 digits:-

0 1 2 3 4 5 6 7

⇒ the hexadecimal number system radix = 16, so it has 16 digits:-

0 1 2 3 4 5 6 7 8 9 A B C D E F

\* the place values of different digits in the integer Part of a number are given by " $r^0, r^1, r^2, r^3, \dots$ ", for the Fractional Part these are " $r^{-1}, r^{-2}, r^{-3}, r^{-4}, \dots$ ".

\* the maximum numbers that can be written with "n" digits in a given number System are equal to " $r^n$ ".

# 1.3 Decimal Number System

9 ١٥٢٠٢٥ التاریخ

Electronics المفهوم

\* it has a radix of 10, therefore it has 10 different digits:-

0, 1, 2, 3, 4, 5, 6, 7, 8, 9

\* the place values in a decimal number System:-



$10^5$   $10^4$   $10^3$   $10^2$   $10^1$   $10^0$  .  $10^{-1}$   $10^{-2}$   $10^{-3}$   $10^{-4}$   $10^{-5}$   $10^{-6}$

\* the value "magnitude" of a given decimal number can be given as the sum of various digits multiplied by their place values like this:-

Ex 3586.265 is:-

$$3586 = 6 \times 10^0 + 8 \times 10^1 + 5 \times 10^2 + 3 \times 10^3$$

$$0.265 = 2 \times 10^{-1} + 6 \times 10^{-2} + 5 \times 10^{-3}$$

## 1.4 Binary Number System

9/15/2025

Electronics : Engineering

\* is a radix-2 number System with "0", "1" as the two independent digits.

\* the Place values in a binary number System:-

$2^5$   $2^4$   $2^3$   $2^2$   $2^1$   $2^0$  .  $2^{-1}$   $2^{-2}$   $2^{-3}$   $2^{-4}$   $2^{-5}$   $2^{-6}$

\* the binary numbers from 0 to 64 are represented like this:-

0	1101	11010	100111	110100
1	1110	11011	101000	110101
10	1111	11100	101001	110110
11	10000	11101	101010	110111
100	10001	11110	101011	111000
101	10010	11111	101100	111001
110	10011	100000	101101	111010
111	10100	100001	101110	111011
1000	10101	100010	101111	111100
1001	10110	100011	110000	111101
1010	10111	100100	110001	111110
1011	11000	100101	110010	111111
1100	11001	100110	110011	1000000

## 1.7.1 Binary Number System

9/15 Role: التاريخ

Electronics الموضع:

- \* **Bit** - the smallest unit of information, an abbreviation of the term "Binary digit", & it is either "0" or "1".
- \* **Byte** - a byte is a string of 8 bits, the byte is the basic unit of data operated upon a single unit in computers.
- \* the 1's complement of a binary number is obtained by complementing all its bits, ie by replacing each "0" with "1" & each "1" with "0":  
$$\Rightarrow (10010110)_2 \text{ 1's complement} = (01101001)_2$$
- \* the 2's complement of a binary number is obtained by adding 1 to its 1's complement:  
$$\Rightarrow (10010110)_2 \text{ 2's complement} = (01101010)_2$$

## 1.7.2 Decimal Number System

Electronics

95/200

\* Corresponding to the 1's & 2's complement in the binary number System, Decimals has a 9's & 10's Complements.

\* 9's Complement - Obtained by subtracting each digit from 9. For Example:-

$$(2496)_{10} \text{ 9's complement} = (7503)_{10}$$

\* 10's complement - Obtained by adding 1 to the 9's complement, like:-

$$(2496)_{10} \text{ 10's complement} = (7504)_{10}$$

## 1.8.1 Sign Bit Magnitude

9/5/2025 التاریخ:

Electronics الموضع:

\* in eight bit representation of a binary number we take the last bit to represent the sign:-

$$\text{if } (+9)_{10} = (00001001)_2$$

$$\text{then } (-9)_{10} = (10001001)_2$$

\* An n-bit binary representation can be used to represent decimal numbers in the range:-

$$-(2^{n-1}-1) \text{ to } +(2^{n-1}-1)$$

\* So 8-bits ranges from -127 to +127

## 1.8.2 1's Complement

9.5.2021

Electronics : 9.5.2021

- \* the positive numbers remains unchanged.
- \* the negative numbers are obtained by taking the 1's complement of the positive counterparts:-

$$(-9)_{10} = (10001001)_2$$

$\xrightarrow{\text{1's complement}}$

$$(11110110)_2$$

## 1.8.3 2's Complement

- \* the positive numbers only we add 1 to them to represent their 2's complement.
  - \* the negative numbers are obtained by taking the 2's complement of their counter parts.
- \* the 2's complement of the magnitude of -9 equals +9

## 1.9.1 Binary -to-decimal Conversion

9.15.2025 التاریخ

Electronics الموضوع

\* to convert a binary number to decimal multiply each number by its place values:-

$$(1001.0101)_2 =$$

$$(1001)_2 = 1 \times 2^0 + 0 \times 2^1 + 0 \times 2^2 + 1 \times 2^3 = 1 + 8 = 9$$

$$(0.0101)_2 = 0 \times 2^{-1} + 1 \times 2^{-2} + 0 \times 2^{-3} + 1 \times 2^{-4} = 0.25 + 0.0625 = 0.3125$$

$$9 + 0.3125 = 9.3125$$

$$(1001.0101)_2 = (9.3125)_{10}$$

Perhaps P- Is that you all the final year of

## 1.10 Decimal to Binary Conversion

9/15/2025

Electronics : 2025

\* for the Integer Part the binary equivalent can be found by successfully dividing the integer part of the number by 2 & recording the remainders until the quotient becomes "0", then the remainders are written in a reverse order.

\* for the fractional part its found by successfully multiplying the fractional decimal part by 2 & recording the carry until the result is "0", the carry sequence in forward order constitutes the binary equivalent of the fractional part of the decimal number.

Ex. Find the binary equivalent of  $(13.375)_{10}$  :-

\* Integer Part :-

$$\begin{array}{r} 2 \quad 13 \quad - \\ 2 \quad 6 \quad 1 \\ 2 \quad 3 \quad 0 \\ 2 \quad 1 \quad 1 \\ \hline 0 \quad 1 \end{array} \quad (13)_{10} = (1101)_2$$

\* Fractional Part :-

$$\begin{array}{l} 0.375 \times 2 = 0.75 \quad 0 \quad (0.375)_{10} = (0.011)_2 \\ 0.75 \times 2 = 0.5 \quad 1 \\ 0.5 \times 2 = 0.0 \quad 1 \end{array}$$

$$(13.375)_{10} = (1101.011)_2$$

## 2.1.1 BCD to Binary Conversion

Q 15 Date: التاریخ

Electronics الموضع

first write its decimal equivalent & then convert it to binary "bit digit by digit" like this

$(0010 \ 1001.0111 \ 0101)_{BCD}$  to binary -

0010 1001.0111 0101  
↓ ↓ ↓ ↓ ↓  
2 9.7 5

$(0010 \ 1001.0111 \ 0101)_{BCD} = (29.75)_10$

$2(29.75) -$   
2 14 1  $(29)_{10} = (11101)_2$   
2 (107) .0  
2 3 1  
2 1 1  
- 0 1

$0.75 * 2 = 0.5$  1  $(0.75)_{10} = (0.11)_2$   
 $0.5 * 2 = 0.0$  1

$(0010 \ 1001.0111 \ 0101)_{BCD} = (11101.11)_2$

$(110.1011) = (259.51)$

## L-1.2 Binary to BCD Conversion

Q 15 ل 25 التاریخ

Electronics : ۱۴۰۰۰۱۱

\* write the given Binary number in decimal form  
the BCD "by turning each digit to binary": -

Ex. 1010 1011. 101 to BCD:-

to decimal

$$(10101011.101)_2 = (1 \times 2^0 + 1 \times 2^1 + 0 \times 2^2 + 1 \times 2^3 + 0 \times 2^4 + 1 \times 2^5 + 0 \times 2^6 + 1 \times 2^7 + 1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3})_{10} = (171.625)_{10}$$

128      0.5      0.0125

to BCD:-

1	7	1	.	6	2	5
0001	0111 0001	. 0110	0010	- 0101		

$$(10101011.101)_2 = (0001 0111 0001. 0110 0010 0101)_{BCD}$$

### 3.1 Basic Rules of Binary Addition &

9/15/2025 | شارج | Subtraction

Electronics | الموضوع

\* Basic Rules of binary Addition :-

- $0+0=0$
- $0+1=1$
- $1+0=1$
- $1+1=0$  with a carry of 1
- $1+1+1=1$  with a carry of 1

\* Basic Rules of Binary Subtraction :-

- $0-0=0$
- $1-0=1$
- $0-1=1$  with a borrow of 1 from the next more significant bit
- $1-1=0$

\* 2's complement representation = Binary representation

### 3.2.1 Addition using the 2's complement Method.

9 15 مالک علی

Electronics : 910011

\* we have 4 different Cases:-

1. Both the numbers are positive.
2. Larger of two numbers is positive.
3. Larger of two numbers is negative.
4. Both the numbers are negative.

\* for positive numbers 2's complement means the binary representation.

\* Case 1:  $(37 + 18) = 00100101 + 00010010 = 00110111 = 55$

\* Case 2:  $(37 + (-18)) = 00100101 + 11101110 = 100010011$   
final carry  $\leftarrow$

we remove the final carry so  $-(00010011)_2 = (19)_{10}$

\* Case 3:  $(-37 + 18) = 11011011 + 00010010 = 11101101$   
which is in the 2's complement form is -19

$(10010011)_2 = -19$ , if the first bit is for the sign

\* Case 4:  $(-37) + (-18)$

$$\begin{array}{r} 1110 \ 1110 \\ 1101 \ 1011 \\ \hline 11100 \ 1001 \end{array} +$$

\* Since there is an overflow of 1 it's negative

$$(1100 \ 1001)_2 \Rightarrow (1011 \ 011 \ 1)_2 = (-55)_10$$

### 3.2 Addition of larger-bit Binary numbers

$$\begin{array}{r} 01010111 \\ 10101000 \\ \hline (11111111)_2 = (255)_{10} \end{array}$$

$$\begin{array}{r} 110100110 \\ 00010111 \\ \hline (11101101)_2 = (237)_{10} \end{array}$$

### 3.3 Subtraction of larger-bit binary number

9/15/2025 التاریخ

Electronics : گروہ ۱۱

\* We use the binary subtraction rules.

\* wherever the bit to be subtracted is larger than the bit we are subtracting from it we borrow from the next adjacent higher bit position a "1".

\* Ex.  $(1100)_2 - (1001)_2 =$

$$\begin{array}{r} 1 \ 0 \ 1 \\ 1 \ 0 \ 0 \ 1 \\ \hline 0 \ 0 \ 1 \ 1 \end{array}$$

#### 3.3.1 Subtraction Using 2's complement Arithmetic

\* Subtrahend: - the bit to be subtracted

\* Minuend: - the bit we are subtracting from it  
Minuend - Subtrahend = result

\* Here we have 6 Cases:-

1. minuend & Subtrahend are positive, the subtrahend is the smallest.
2. minuend is positive, so as the subtrahend, the subtrahend is the largest.
3. minuend is positive, subtrahend is negative & smaller in magnitude.
4. minuend is positive, subtrahend is negative & bigger in magnitude.
5. both are negative, the minuend is the smallest.
6. both are negative, the minuend is the largest.

\* Case 1 -  $(24 - 14) =$

$$\begin{array}{r}
 0\ 10\ 1 \\
 0\ 0\ 0\ 1\ 1\ 0\ 0\ 0 \\
 \hline
 0\ 0\ 0\ 0\ 1\ 1\ 1\ 0 \\
 \hline
 0\ 0\ 0\ 0\ 1\ 0\ 1\ 0
 \end{array}
 \Rightarrow 10$$

\* Case 2 -  $(14 - 24) =$

$$\begin{array}{r}
 0\ 0\ 0\ 1\ 1\ 1\ 0 \\
 1\ 1\ 1\ 0\ 1\ 0\ 0\ 0 \\
 \hline
 1\ 1\ 1\ 1\ 0\ 1\ 1\ 0
 \end{array}$$

we get its 2's Complement

get its 2's complement:  
 $= (10001010)_2$

\* Case 3 -  $(24 - (-14)) = (24 + 14) =$

$$\begin{array}{r}
 0\ 0\ 0\ 1\ 1\ 0\ 0\ 0 \\
 0\ 0\ 0\ 0\ 1\ 1\ 1\ 0 \\
 \hline
 0\ 0\ 1\ 0\ 0\ 1\ 1\ 0
 \end{array}
 \Rightarrow 38$$

\* Case 4 -  $(14 - (-24)) = (14 + 24) =$

$$\begin{array}{r}
 0\ 0\ 0\ 0\ 1\ 1\ 1\ 0 \\
 0\ 0\ 0\ 1\ 1\ 0\ 0\ 0 \\
 \hline
 0\ 0\ 1\ 0\ 0\ 1\ 1\ 0
 \end{array}
 \Rightarrow 38$$

التاريخ: 15/2/25

Continue

Electronics الموضع:

\* Case 5:  $-(-24 - (-14)) = (-24 + 14) = (14 - 24) =$

$$\begin{array}{r} 11101000 \\ 00001110 \\ \hline 11110110 \end{array} \Rightarrow (10001010)_2 = (10)_10$$

\* OR: -

$$\begin{array}{r} 00001110 \\ 11101000 \\ \hline 11110110 \end{array}$$

get its 2's complement  $(10001010)_2 = (-10)_10$

Case 6:  $-(-14 - (-24)) = (-14 + 24) = (24 - 14) =$

$$\begin{array}{r} 11110010 \\ 00011000 \\ \hline 11101010 \end{array} \Rightarrow \text{answer} = -14$$

# BCD Addition in Excess-3 Code

Q. 15 Let's التاريخ

Electronics الموضوع:

\* Steps :-

1. Convert the BCD to Excess-3 by adding 0011 to each group
2. Add the two codes using Binary addition Rules.

3. Correct if :-

- Sum result  $> (9)_10$   $((1001)_2$ ), subtract 0011
- the group produces a carry  $>$  add 0011

## 4.3.1 OR Gate

10 15 2015 التاریخ

Electronics: إلكترونیک

$$* A \text{ OR } B = A + B = \overline{A} \overline{B} \overline{D}$$

\* returns 1 if atleast one of the inputs is 1 & returns 0 otherwise.



A	B	y
0	0	0
0	1	1
1	0	1
1	1	1

## 4.3.2 AND Gate

$$* A \text{ AND } B = A \cdot B = \overline{A} \overline{B} \overline{D}$$

\* returns 1 only & only if all the inputs equals 1, & returns 0 otherwise.



A	B	y
0	0	0
0	1	0
1	0	0
1	1	1

### 4.3.3 NOT Gate


التاريخ: 10/15/2025

Electronics

الموضوع:

$$* \bar{x} = x' = \bar{x} \rightarrow \bar{x}$$

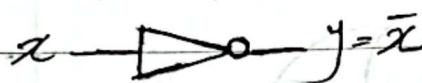\* returns the complement of the input, returns "0" if the input is "1" & return "1" if the input is "0".



x	y
0	1
1	0

### 4.3.4 Exclusive OR Gate "XOR"

$$* A \oplus B = \bar{A}B + A\bar{B} = \begin{array}{c} A \\ \oplus \\ B \end{array} \rightarrow \text{Y}$$

\* returns "1" if the inputs are different & return "0" otherwise.



A	B	y
0	0	0
0	1	1
1	0	1
1	1	0

## 4.3.5 NAND Gate


10/15/2025 التاریخ

Electronics: المفهوم

$$*(\overline{A \cdot B}) = \overline{A} \quad \overline{B} \quad \text{D}$$


\* gives 0 if  
otherwise

all inputs are 1 & returns 1

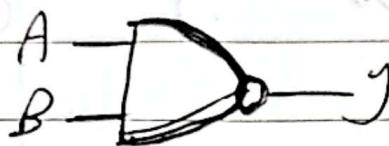


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

## 4.3.6 NOR Gate

$$*(\overline{A+B}) = \overline{A} \quad \overline{B} \quad \text{D}$$

\* gives one if all inputs = zero.

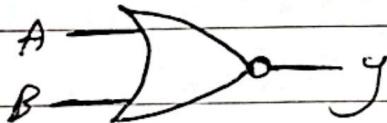

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

## 4.3.7 Exclusive NOR Gate


10 15 20 درجات

Electronics الموضع:

\* returns 1 if all inputs are same, 0 otherwise.

$$* (A \oplus B) = (A \cdot B + \bar{A} \cdot \bar{B}) \Rightarrow D$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

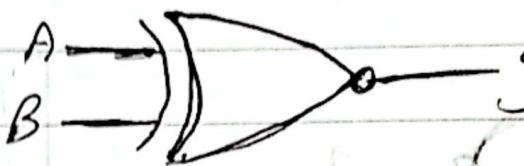

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

## 6.1.1 Variables, literals & Terms in Boolean Expressions

13/5/2025 التاريخ

Electronics : الالكترونيات

- \* Variables can take values either "0" or "1" in Boolean expressions.
- \* The complement of a variable is not considered as a separate variable

## 6.1.2 Equivalent & Complement of Boolean Expressions

- \* two given Boolean expressions are said to be equivalent if one of them equals "1" when the other equals "1" & also equals "0" only when the other equals zero.

Ex. get the complement of  $\bar{A}B + A\bar{B}$  :-

$$\begin{aligned}\bar{A}B + A\bar{B} &\Rightarrow \bar{A}B + A\bar{B} = \bar{A}B \cdot A\bar{B} \\ &= (A + \bar{B}) \cdot (\bar{A} + B)\end{aligned}$$

Ex Get the Complement of  $\bar{A}\bar{B} + A \cdot B$

$$\begin{aligned}\bar{A}\bar{B} + A \cdot B &\Rightarrow \bar{A}\bar{B} + A \cdot B = (\bar{A} \cdot \bar{B}) \cdot (\bar{A} \cdot B) \\ &= (A + B) \cdot (\bar{A} + \bar{B})\end{aligned}$$

# A Summary of Boolean Algebra rules

13/15/2020: جاري

Electronics

الموضوع

$\oplus$  → OR

$\cdot$  → AND

$\sim, \neg, \overline{\cdot}, \overline{1}$  → NOT

\* Identity Rules:-

$$* A + 0 = A \quad * A \cdot 1 = A$$

\* NULL Domination laws:-

$$* A + 1 = 1 \quad * A \cdot 0 = 0$$

\* Idempotent laws:-

$$* A + A = A \quad * A \cdot A = A$$

\* Complement laws:-

$$* A + \bar{A} = 1 \quad * A \cdot \bar{A} = 0$$

\* Double Negation law:-

$$* \overline{\overline{A}} = A = \bar{\bar{A}} = 1 | A$$

\* Commutative laws:-

$$* A + B = B + A \quad * A \cdot B = B \cdot A$$

\* Associative laws:-

$$* (A + B) + C = A + (B + C) \quad * (A \cdot B) \cdot C = A \cdot (B \cdot C)$$

\* Distributive laws:-

$$* A \cdot (B + C) = A \cdot B + A \cdot C \quad * A + (B \cdot C) = (A + B) \cdot (A + C)$$

\* DeMorgan's laws:-

$$* \overline{A + B} = \overline{A} \cdot \overline{B} \quad * \overline{A \cdot B} = \overline{A} + \overline{B}$$

\* Absorption laws:-

$$* A + (A \cdot B) = A \quad * A \cdot (A + B) = A$$

## \* Redundancy Laws:-

(أ) مبدأ "Absorption" مبدأ امتصاص

$$* A + A \cdot B = A$$

$$* A \cdot (A + B) = A$$

## \* Consensus Theorem:-

$$* A \cdot B + \bar{A} \cdot C + B \cdot \bar{C} = A \cdot B + \bar{A} \cdot C$$

\* Definition of "XOR":-  $A \oplus B = (A \cdot \bar{B}) + (\bar{A} \cdot B)$ 

$$* \text{inverse: } A \oplus 1 = \neg A$$

$$* \text{Zero-Sum "Cancellation": } A \oplus B \oplus B = A$$

$$* \text{Complement law: } A \oplus \neg B = \neg(A \oplus B)$$

### 6.6.1 Construction of a Karnaugh Map

التاريخ: 15/05/2013

## Electronics : engineer

A Karnaugh Map is a graphical representation of the logic system. It can be drawn directly from the either min-term (sum-of-products) or max term (product-of-sums) Boolean expressions.

\* An  $n$ -variable Karnaugh Map has " $2^n$ " Squares, & each possible input is allotted a square. In the case of a minterm Karnaugh Map, "1" is placed in all those squares for which the output is "1", "0" is placed in all those squares for which the output is "0", "0"s are omitted for simplicity. An "X" is placed in squares corresponding to "don't care" conditions. In the case of a maxterm Karnaugh Map, "a "1" is placed in squares for which the output is "0", and a "0" is placed for input entries corresponding to a "1" output, & also here "0"s are omitted for simplicity & an "X" is placed in squares corresponding to "don't care" conditions.

ـ "f" ـ> "output" ـ>  $\delta^o K-map$  ـ>  $f$  ـ>  $f$

ـ "o" يـ "output" اـ "K-map" مـ "o" بـ "input" اـ "o" يـ "output" اـ "K-map" مـ "o" بـ "input"

٤- يُنظر "X" في الأماكن التي تعيّنها حالة أو

# Continue

التاريخ: 13/15/2025

الموضوع: Electronics

بالنسبة لـ "master" -

1- يخرج 1 من الـ "output" لو الا "K-map" بد

2- يخرج 0 من الـ "output" لو الا "K-map" بد 1

3- ينخدع اد 0 في الرسمة للتسلسل

4- ينخدع K في الا "K-map" الى فتوح حالة الـ "don't care"

5- ينخدع K في الا "K-map" الى غلق حالة الـ "don't care"

6- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

7- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

8- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

9- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

10- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

11- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

12- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

13- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

14- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

15- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

16- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

17- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

18- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

19- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

20- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

21- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

22- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

23- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

24- ينخدع K في الا "K-map" الى غير مكتوب حالة الـ "don't care"

# K-maps

13/15/2025 التاريخ

Electronics الموضع:

\* why K-maps?

→ Better & more precise than Boolean Algebra.

\* K-maps only works for 5-variables at most.

\* K-maps is a way to simplify Boolean expressions graphically without having any doubt that it's in the simplest form.

\* K-maps "How to use":-

1. Make a table with  $2^n$  squares in it ("n" is the variables count)

2. We number the squares like this:-

for 2 variables:-

00	01	11	10
0			
1			

مخطط الحالات جميع القيم  
للمتغير

for 3 variables:-

000	010	110	100
001	011	111	101
010	011	110	100
011	001	101	100
100	101	111	011
101	100	110	010
110	111	011	001
111	101	010	000

دائم وانت يتطلب  
دوك غير عادة واحدة  
كما تذكرت خاتمة

for 4 variables:-

0000	0100	1100	1000
0001	0101	1101	1001
0010	0110	1110	1010
0011	0111	1111	1011
0100	0101	1101	1001
0101	0111	1111	1011
0110	0010	1010	0000
0111	0011	1011	0001
1000	1001	1101	0101
1001	1011	1111	0111
1010	1011	1110	0100
1011	1111	0111	0011
1100	1101	0101	0000
1101	1111	0111	0011
1110	1010	0100	0000
1111	1011	0111	0011

3. For each term, mark it with 1 on the K-map.

Ex  $xyz + \bar{x}y + \bar{x}\bar{y}z + \bar{x}$

$\bar{z}$	$\bar{x}\bar{y}$	00	01	11	10
$\bar{z}$	0	0	0	0	0
$\bar{x}$	4	5	7	6	0
$\bar{y}$	12	13	15	14	1
$y$	8	9	11	10	1

So  $xyz \rightarrow$  Marked with 1

$\bar{x}y, \bar{y}z \rightarrow$  Marked with 0

4. Group each 1's Group if they are next to each other & can be divided by 2 {8, 6, 11, 2}

From 8 to 2 Ex:-

$\bar{z}$	$\bar{x}\bar{y}$	00	01	11	10
$\bar{z}$	0	1	0	0	1
$\bar{x}$	4	5	1	7	6
$\bar{y}$	12	13	15	1	14
$y$	8	1	9	1	10

5. write their corresponding values like this:-

$$xyz + \bar{x}yz + \bar{y}z + \dots$$






١٣١٥٢٠٢٠ التاریخ

Continue

Electronics

الموضوع:

\* Shapes you can make -

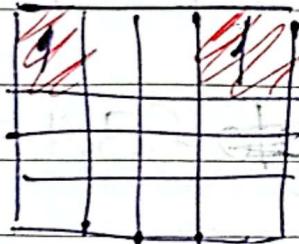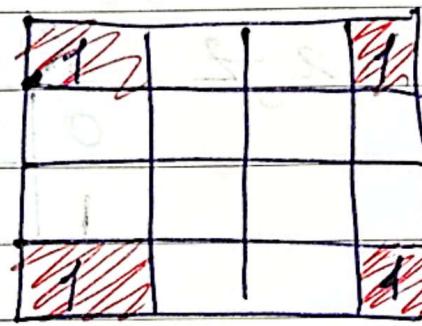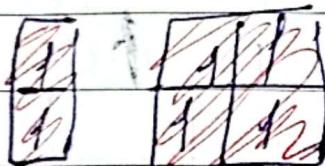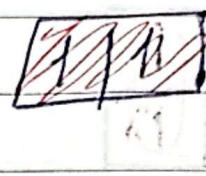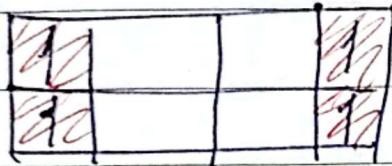

\* Interception may occur but remember to take all ones



Ex.  $F = \bar{x}y + x\bar{y} + xy \rightarrow$  Simplify Using K-map

$\bar{x}$	0	1
0	0	1
1	1	0

$$\Rightarrow y + x'$$

Ex.  $F = x\bar{y}z + x\bar{y}z' \rightarrow$

$\bar{x}$	00	01	11	10
0	0			
1		1	1	1

$$\Rightarrow xz$$

Ex. Using K-Map Simplify:  $F(x,y,z) = \sum(1,3,4,5)$

$$= F = \sum(010, 011, 100, 101)$$

$\bar{x}$	00	01	11	10
0	1	1		1
1			1	1

$$\Rightarrow x\bar{y} + \bar{x}y = xy$$

Ex.  $F(x,y,z) = \sum(3,4,5,7) \rightarrow$  Simplify using K-map.

$$= F = \sum(011, 100, 110, 111)$$

$\bar{x}$	00	01	11	10
0	1	1	1	1
1	1	1	1	1

$$\Rightarrow x\bar{z} + y\bar{z}$$

التاريخ: 13/15/2025

Continue

Electronics

الموضوع:

Ex. Simplify  $f = \bar{a}\bar{b}\bar{c} + \bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}cd + ab\bar{c}$ , using Kmap

cd	00	01	11	10
ab	1			1
cd	1			1
ab	00	01	11	10
cd	00	01	11	10

$$= \bar{b}d$$

cd	00	01	11	10
ab	1	1		1
cd	1	1		1
ab	00	01	11	10
cd	00	01	11	10

$$\Rightarrow \bar{b}\bar{c} + \bar{a}\bar{d}c + ad\bar{b}$$

Ex. Simplify  $y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D}$ , using Kmap

cd 0000 1110

cd	00	01	11	10
ab	1	1	1	1
cd	1	1	1	1
ab	00	01	11	10
cd	00	01	11	10

$$\Rightarrow AB\bar{C}\bar{D} + \bar{A}BC\bar{D} + \bar{B}\bar{C}\bar{D}$$

Thank you

# 5 Variables K-MAP

التاريخ 13/5/2025

Electronics الموضع:

$f(E, a, b, c, d)$  : 5 3d array تعتبر المدخلات

		ab	00	01	11	10
		cd	00	01	11	10
a	b	00	0	1	3	2
		01	4	5	7	6
c	d	11	12	13	15	14
		10	8	9	11	10

		ab	00	01	11	10	
		cd	00	16	17	19	18
a	b	01	20	21	23	22	
		11	28	29	31	30	
c	d	10	24	25	27	26	
		00	18	19	21	20	

$$E = 0$$

$$E = 1$$

الكتل المماثلة (الكتل المماثلة) Group 3, Group 1

$$\text{Ex. } f(a, b, c, d, e) = \bar{a} \bar{b} \bar{c} \bar{d} + \bar{b} \bar{c} + a \bar{b} \bar{c} + a \bar{b} e + a e b + \bar{a} d + a d$$

		ab	00	01	11	10
		cd	00	1	X	X
a	b	00	1	X	X	X
		01	1	1	1	1
c	d	11	1	1	1	1
		10		X	X	X

		ab	00	01	11	10
		cd	00	1	X	X
a	b	01	1	1	1	1
		11	1	1	1	1
c	d	10		X	X	X
		00	1	X	X	X

$$e = 0$$

$$e = 1$$

$$ab + \bar{b} \bar{c} + a \bar{d} + \bar{a} d$$


$$= ab + \bar{b} \bar{c} + (a \oplus d)$$

## F.I.1 Half-Adder

14/15 Dol: ١٤/١٥ دل:

Electronics : إلكترونيات

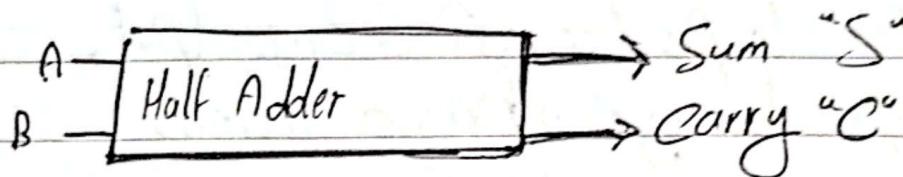
\* an arithmetic circuit block that can be used to add two bits




A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Sum } S = \bar{A}B + A\bar{B} = A \oplus B$$

$$\text{Carry} = A \cdot B$$

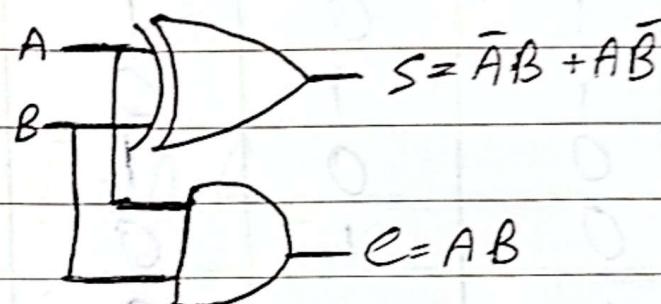

\* Half Adder using Nand Gates:-

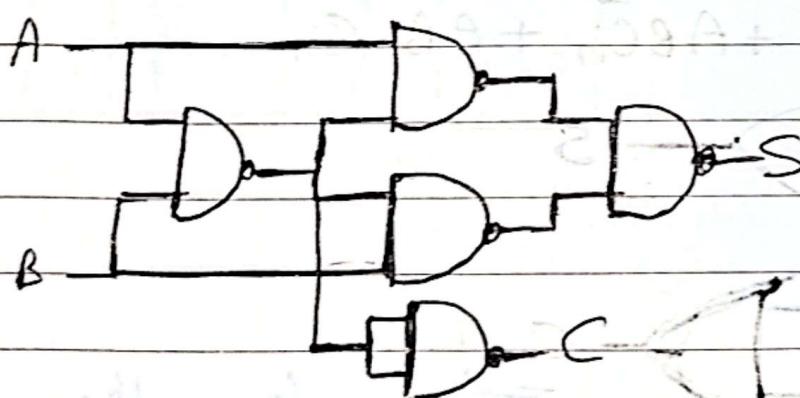

## F.3.2 Full Adder

14-15-25 التاریخ


Electronics الموضع:

- \* an arithmetic circuit block that can be used to add three bits to produce a sum or carry output.
- \* used for larger binary numbers addition.

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = \bar{A} \bar{B} C_{in} + \bar{A} B \bar{C}_{in} + A \bar{B} \bar{C}_{in} + A B C_{in}$$
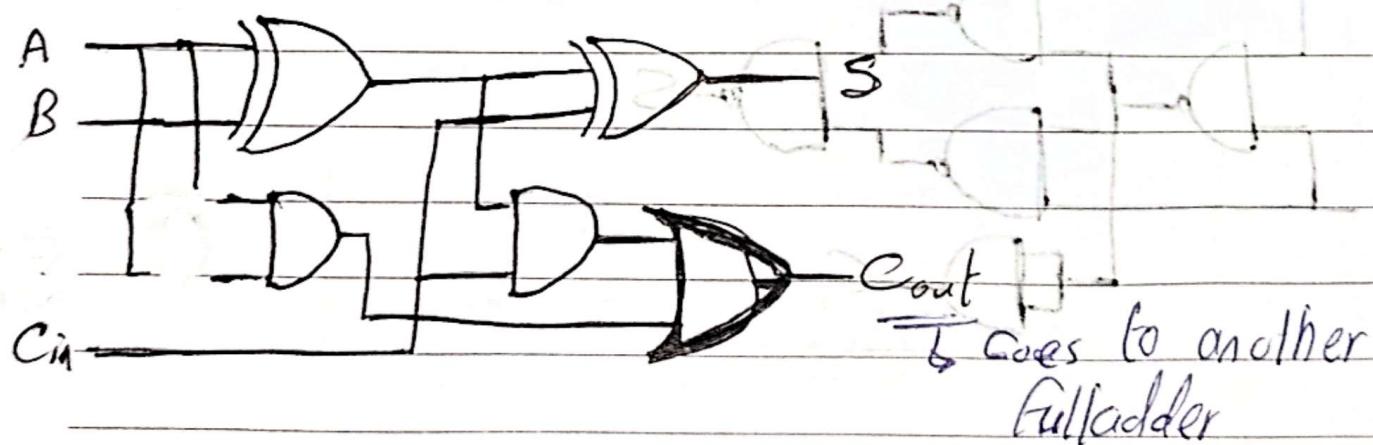
$$Cout = \bar{A} B C_{in} + A \bar{B} C_{in} + A B \bar{C}_{in} + A B C_{in}$$



### 7.3.3 Half Subtractor

Electronics

: ١٤١٥٢٠٢٥

التاريخ:

Minuend - Subtrahend = result


\* We can also add the 2's complement of the subtrahend to the minuend to get the same result.

\* half subtractor: - a combinational circuit that can be used to subtract one binary digit from another, it produce a difference output & a borrow output the borrow specifies whether a "1" was borrowed to perform the subtraction or not.

$$\text{Difference } D = \bar{A} \cdot B + A \cdot \bar{B}$$

$$\text{Borrow } B_o = \bar{A} \cdot B$$

A	B	D	$B_o$	A	B	Half Subtractor	$D = A - B$	$B_o$
0	0	0	0					
0	1	1	1					
1	0	1	0					
1	1	0	0					

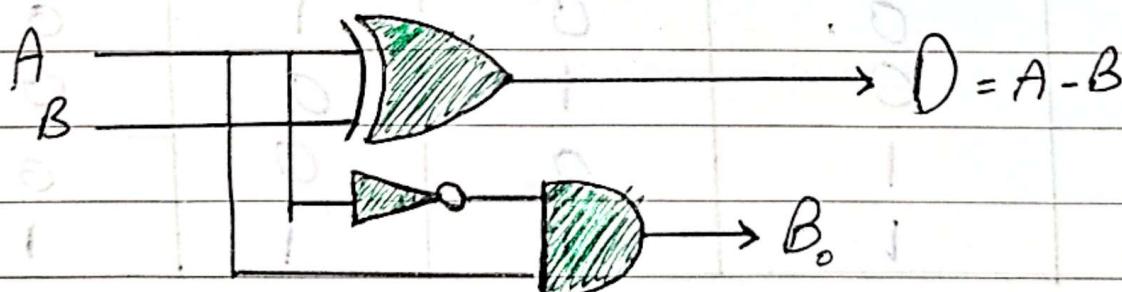

## F-3.4 Full Subtractor


١٤١٥٢٠٢٥ التاریخ

الموضوع: Electronics

- \* a full Subtractor perform subtraction on two bits, a minuend and a subtrahend, & it also takes in consideration if a "1" was borrowed or not

Difference "D" =  $\bar{A}\bar{B}B_{in} + \bar{A}B\bar{B}_{in} + A\bar{B}\bar{B}_{in} + AB\bar{B}_{in}$

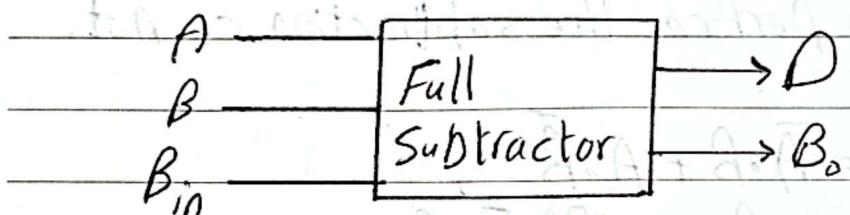Borrow "B\_o" =  $\bar{A}\bar{B}B_{in} + \bar{A}B\bar{B}_{in} + \bar{A}B\bar{B}_{in} + ABB_{in}$




Minuend A	Subtrahend B	Borrow in B <sub>in</sub>	Difference D	Borrow out B <sub>o</sub>
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$*D = \bar{A} \bar{B} B_o + \bar{A} B \bar{B}_o + A \bar{B} \bar{B}_o + A B B_o$$

$$\star B_0 = \bar{A} \cdot B + \bar{A} \cdot B_{in} + B \cdot B_{in}$$

## "Simplified version"

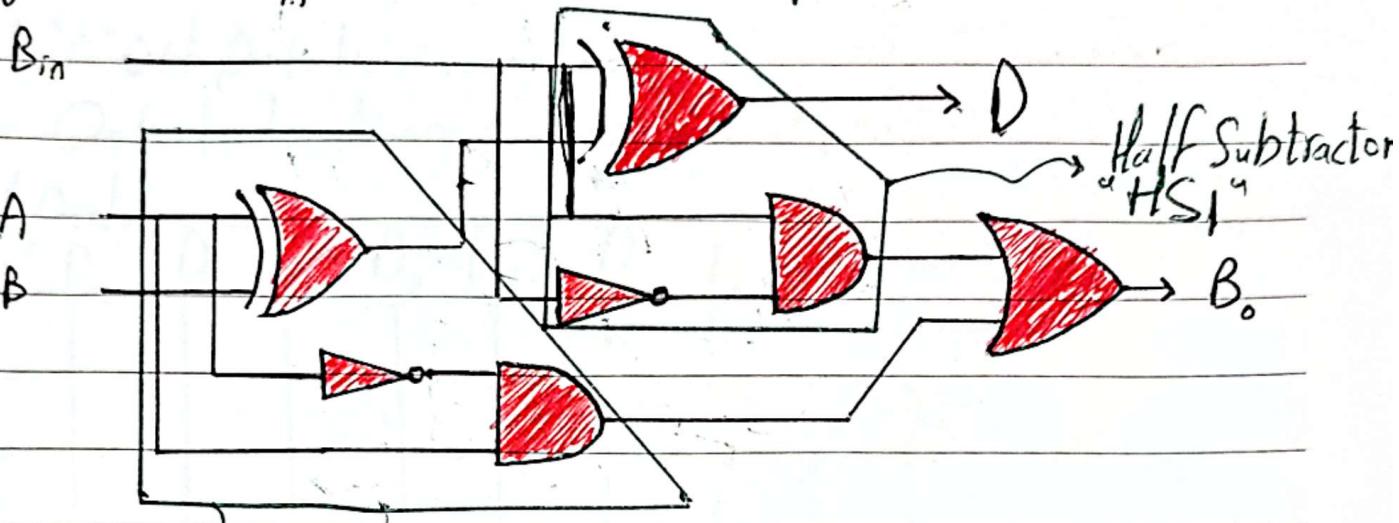

## Half Subtractor

- HSIIJII+

يحسب الفرق على  $|A - B| \leftarrow B - A$  "Borrow" في  $C - A$ .

HSI

- يحسب الفرع ما ينت "B<sub>11</sub>" ← (و فيه "Borrow" من الرّابع الذي قيلوا "A-B-B<sub>1</sub>) ← (B<sub>1</sub> A (الفرع ما ينت ولا لا) و الناتج من "HSI" (الفرع ما ينت ولا لا).
- يحسب (و فيه "Borrow" ما ينت ولا لا).

## 8-2 Encoders


١٤ ١٥ ٢٠٢٥ التاريخ

Electronics: إبراهيم

→ An encoder is a multiplexer without its single output line, it's a combinational logic function that has "2<sup>n</sup>" or fewer input lines & "n" output lines.

\* Ex. Octal to Binary Encoder - it has 3 inputs & three outputs

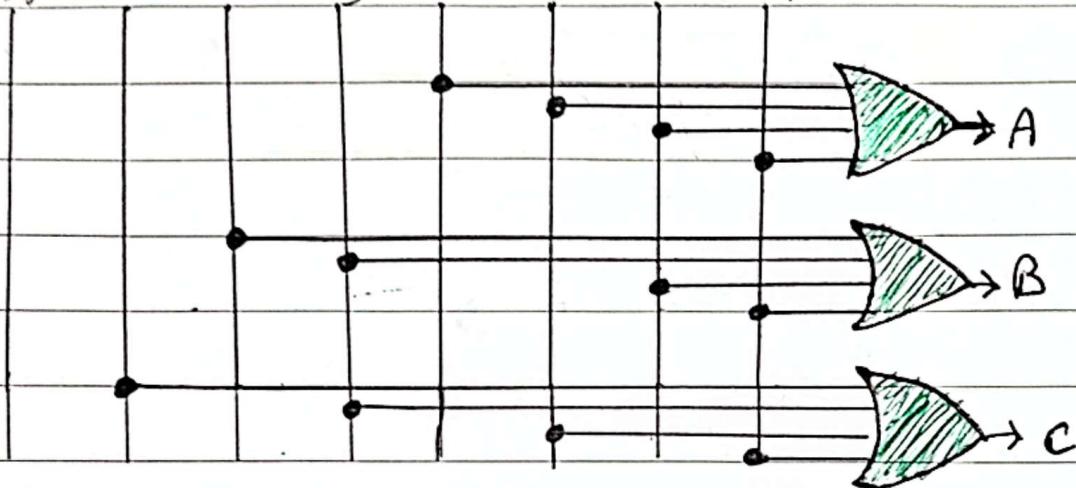$D_0$   $D_1$   $D_2$   $D_3$   $D_4$   $D_5$   $D_6$   $D_7$



$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	A	B	C
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1